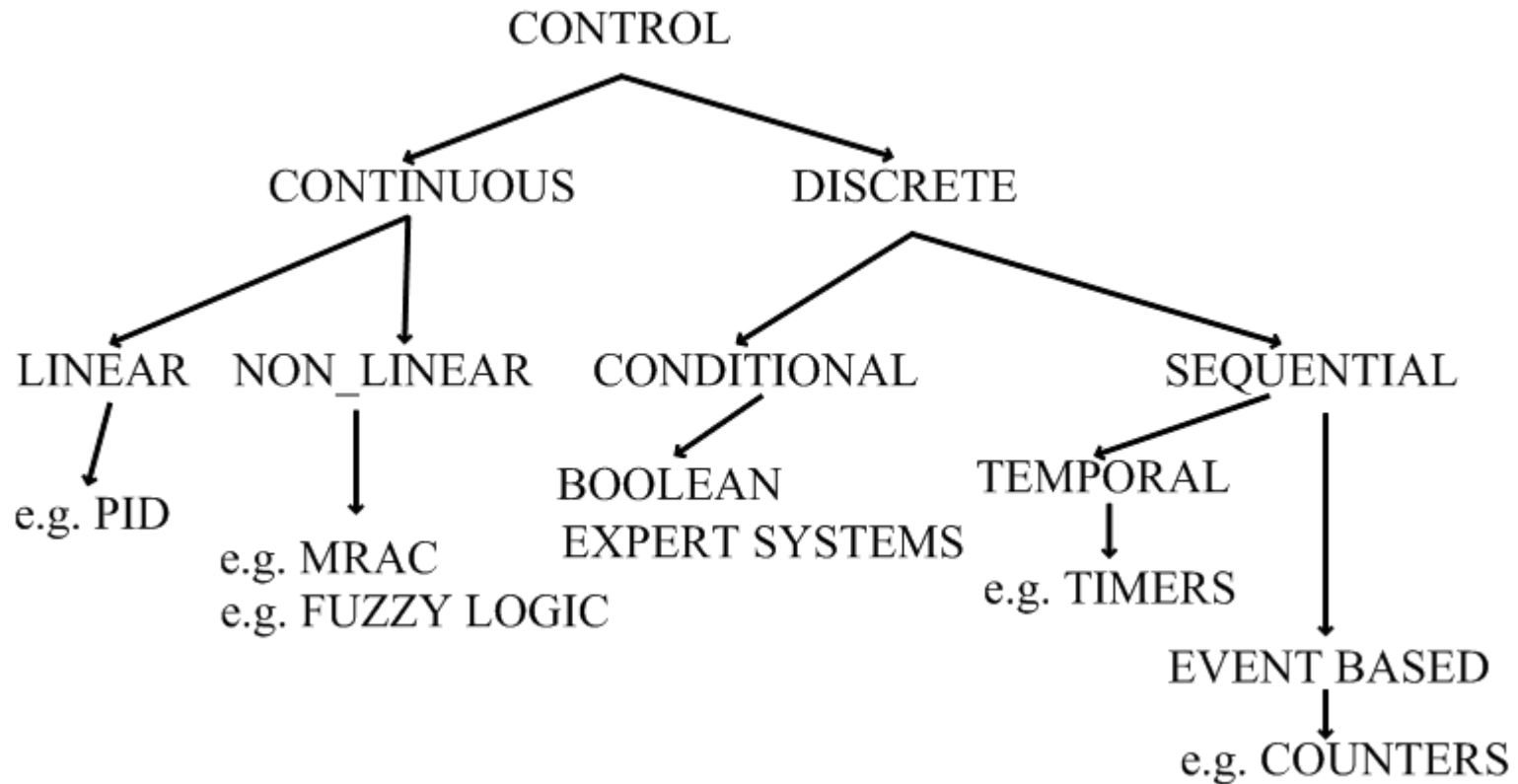


Lecture 3

PLC programming

Basic categories of control systems



- Continuous - The values to be controlled change smoothly. e.g. the speed of a car.
- Discrete (Logical) - The value to be controlled are easily described as on-off. e.g. when the power is turned on, the press closes
- Linear - Can be described with a simple differential equation.
- Non linear - It involves more than one variable in more complex relations
- Sequential - A logical controller that will keep track of time and previous events.

Example: Control concerns in an elevator:

Logical:

1. The elevator must move towards a floor when a button is pushed.
2. The elevator must open a door when it is at a floor.
3. It must have the door closed before it moves.

Linear:

1. If the desired position changes to a new value, accelerate quickly towards the new position.
2. As the elevator approaches the correct position, slow down.

Non-linear:

1. Accelerate slowly to start.
2. Decelerate as you approach the final position.
3. Allow faster motion while moving.
4. Compensate for cable stretch, and changing spring constant, etc.


Migration from relays to PLC

- electricity has been used for control and early electrical control was based on relays.
- These relays allow power to be switched on and off without a mechanical switch.
- It is common to use relays to make simple logical control decisions.
- The development of low cost computer has brought the most recent revolution, the Programmable Logic Controller (PLC).
- The advent of the PLC began in the 1970s, and has become the most common choice for manufacturing controls.

- PLCs have been gaining popularity on the factory floor and will probably remain predominant. Most of this is because of the advantages they offer.
 1. Cost effective for controlling complex systems.
 2. Flexible and can be reapplied to control other systems quickly and easily.
 3. Computational abilities allow more sophisticated control.
 4. Trouble shooting aids make programming easier and reduce downtime.
 5. Reliable components make these likely to operate for years before failure.

Ladder logic


- Ladder logic is the main programming method used for PLCs.
- ladder logic has been developed to mimic relay logic.
- By selecting ladder logic as the main programming method, the amount of training needed for engineers and trades people was greatly reduced.
- Modern control systems still include relays, but these are rarely used for logic.
- A relay is a simple device that uses a magnetic field to control a switch, as shown below.

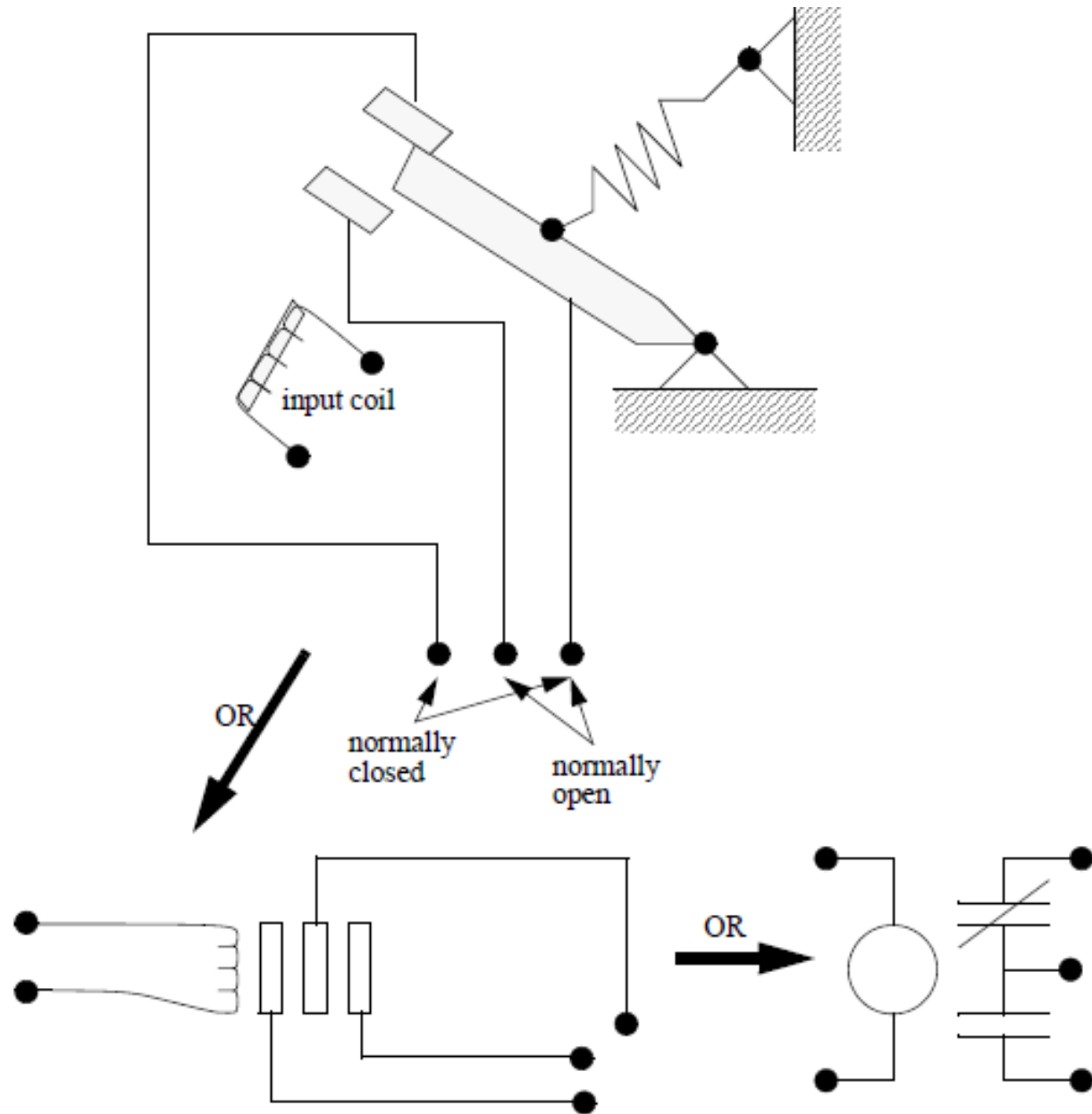


Relay layout and schematics

- When a voltage is applied to the input coil, the resulting current creates a magnetic field. The magnetic field pulls a metal switch (or reed) towards it and the contacts touch, closing the switch.
- The contact that closes when the coil is energized is called normally open.
- The normally closed contacts touch when the input coil is not energized.
- Relays are normally drawn in schematic form using a circle to represent the input coil.
- The output contacts are shown with two parallel lines. Normally open contacts are shown as two lines, and will be open (non-conducting) when the input is not energized.
- Normally closed contacts are shown with two lines with a diagonal line through them. When the input coil is not energized the normally closed contacts will be closed (conducting).

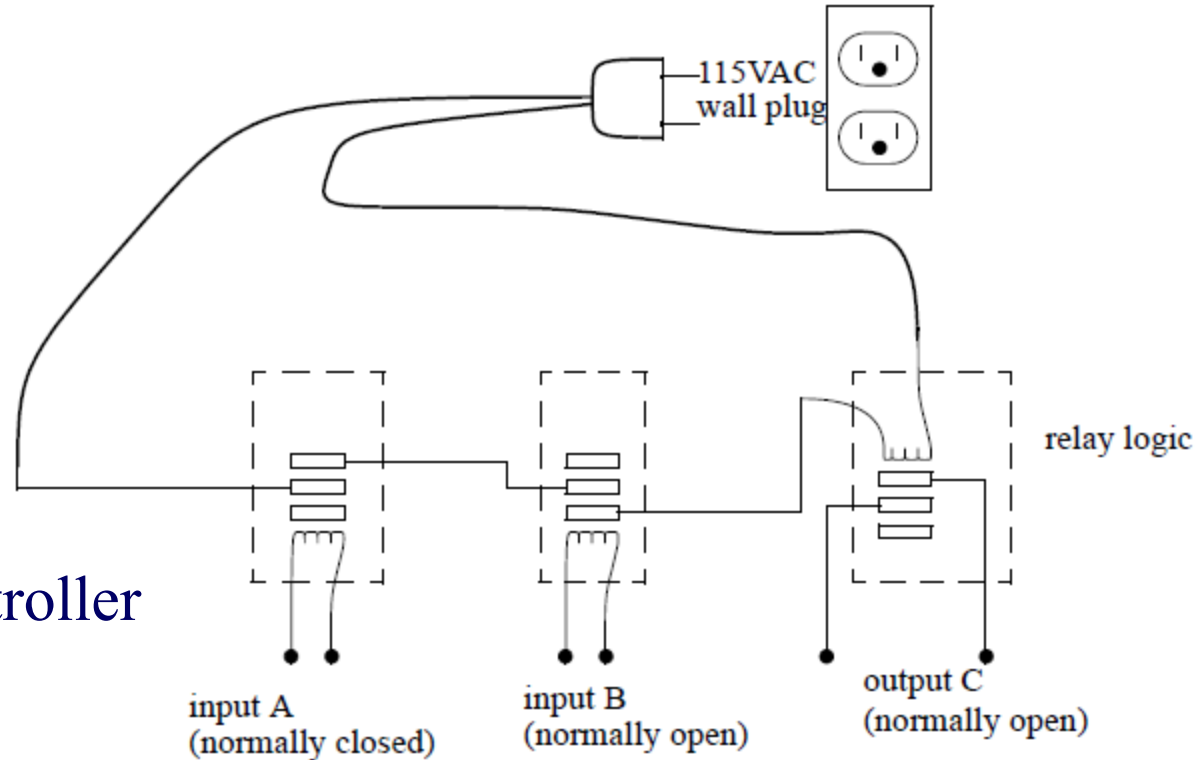- Relays are used to let one power source close a switch for another (often high current) power source, while keeping them isolated As shown below.




A simple relay controller

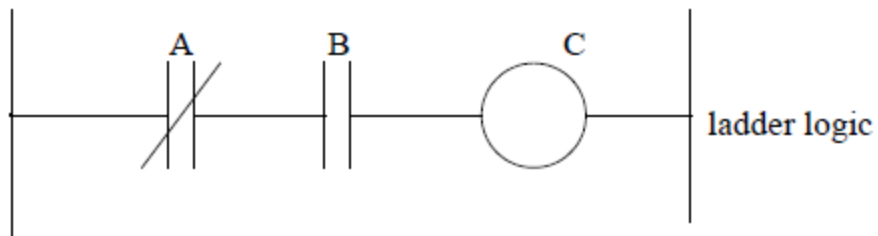

- In this system the first relay on the left is used as normally closed, and will allow current to flow until a voltage is applied to the input A.
- The second relay is normally open and will not allow current to flow until a voltage is applied to the input B.
- If current is flowing through the first two relays then current will flow through the coil in the third relay, and close the switch for output C.
- This circuit would normally be drawn in the ladder logic form.
- This can be read logically as C will be on if A is off and B is on.

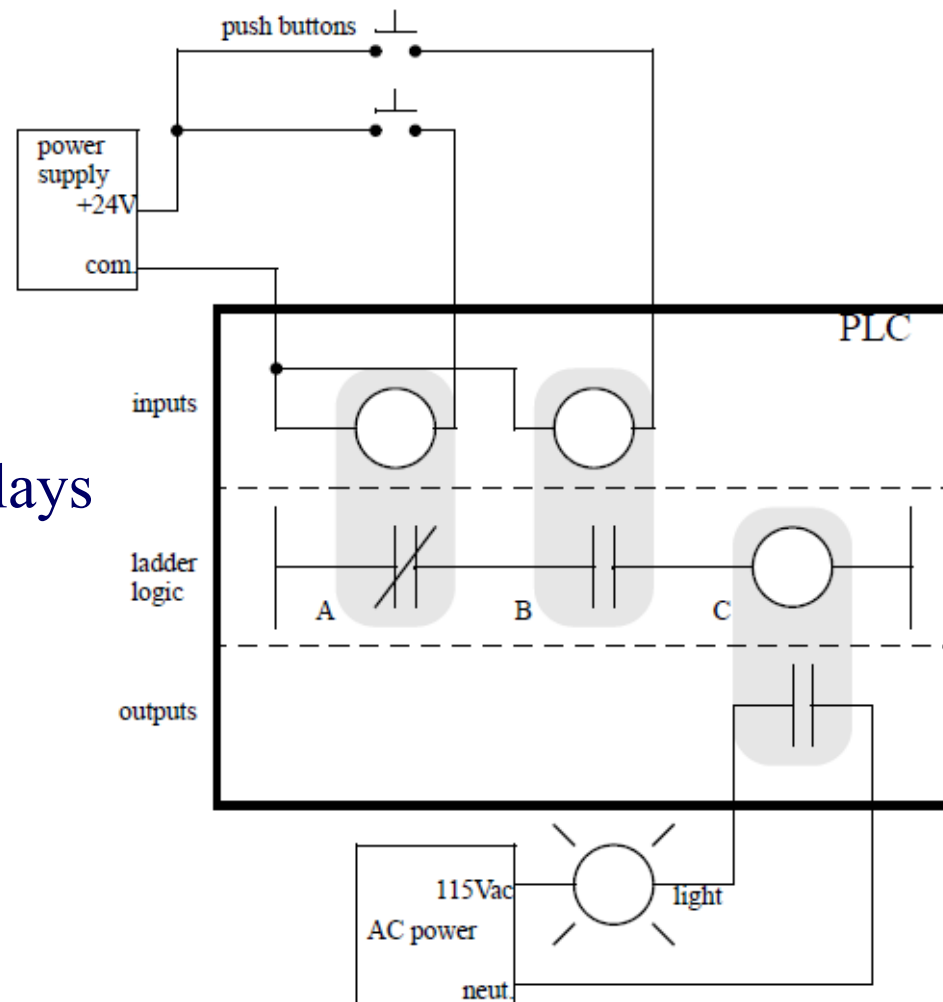- The example above does not show the entire control system, but only the logic. When we consider a PLC there are inputs, outputs, and the logic. The figure below shows a complete representation of the PLC.



A PLC illustrated with relays

- There are two inputs from push buttons.
- The inputs as activating 24V DC relay coils in the PLC.
- This in turn drives an output relay that switches 115V AC, that will turn on a light.
- In actual PLCs inputs are never relays, but outputs are often relays.
- The ladder logic in the PLC is actually a computer program that the user can enter and change.
- Notice that both of the input push buttons are normally open, but the ladder logic inside the PLC has one normally open contact, and one normally closed contact.


- The ladder logic in the PLC don't need to match the inputs or outputs.
- Many relays have multiple outputs (throws) and this allows an output relay to also be an input simultaneously.
- The circuit shown below is an example of this, it is called a **seal in circuit**.
- When A is pushed, the output B will turn on, and the input B will also turn on and keep B on permanently until power is removed.



- In this circuit the current can flow through either branch of the circuit, through the contacts labelled A or B.
- The input B will only be on when the output B is on.
- If B is off, and A is energized, then B will turn on.
- If B turns on then the input B will turn on, and keep output B on even if input A goes off.
- After B is turned on the output B will not turn off.

Programming:

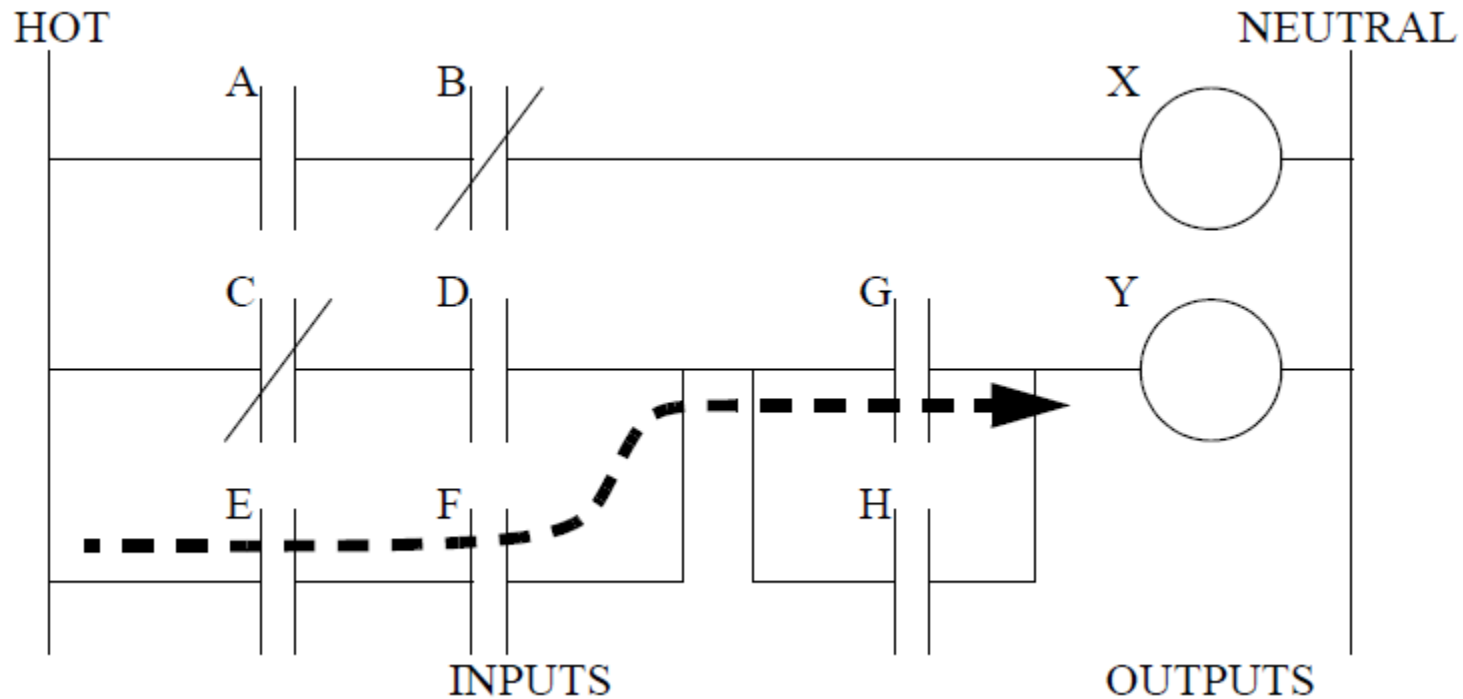- An example of ladder logic is shown below.



Power needs to flow through some combination of the inputs (A,B,C,D,E,F,G,H) to turn on outputs (X,Y).

- To interpret this diagram imagine that the power is on the vertical line on the left hand side, we call this the hot rail.
- On the right hand side is the neutral rail.
- In the figure there are two rungs, and on each rung there are combinations of inputs (two vertical lines) and outputs (circles).
- If the inputs are opened or closed in the right combination the power can flow from the hot rail, through the inputs, to power the outputs, and finally to the neutral rail.
- An input can come from a sensor, switch, or any other type of actuators.

- An output will be some device outside the PLC that is switched on or off, such as lights or motors.
- In the top rung the contacts are normally open and normally closed. Which means if input A is on and input B is off, then power will flow through the output and activate it.
- Any other combination of input values will result in the output X being off.
- The second rung is more complex, there are multiple combinations of inputs that will result in the output Y turning on.
- On the left most part of the rung, power could flow through the top if C is off and D is on.

- Power could also (and simultaneously) flow through the bottom if both E and F are true. This would get power half way across the rung, and then if G or H is true the power will be delivered to output Y.

Other methods of programming PLC's

Mnemonic instructions

- These instructions can be derived directly from the ladder logic diagrams and entered into the PLC through a simple programming terminal. An example of mnemonics is shown below


- In this example the instructions are read one line at a time from top to bottom.
- The first line 00000 has the instruction LDN (input load and not) for input A. This will examine the input to the PLC and if it is off it will remember a 1, if it is on it will remember a 0.

```

00000 LDN  A
00001 LD   B
00002 AND  C
00003 LD   D
00004 AND  D
00005 AND
00006 OR
00007 ST   X
00008 END

```

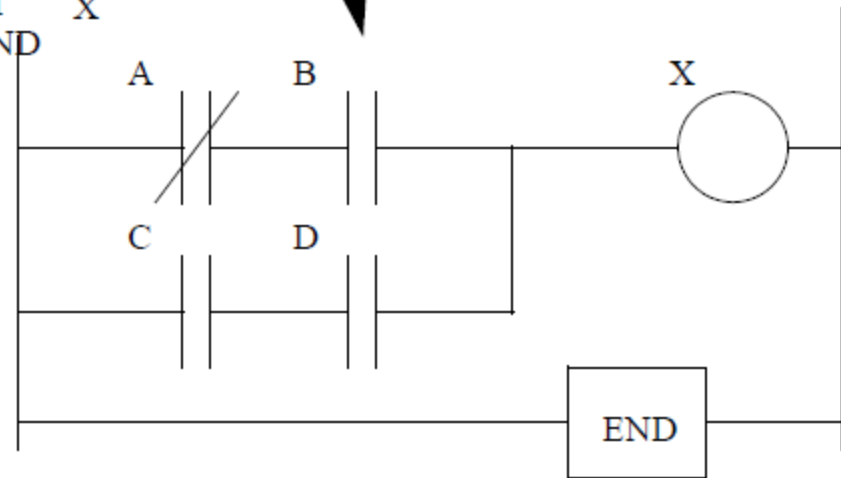the mnemonic code is equivalent to the ladder logic below



- The next line uses an LD (input load) statement to look at the input. If the input is off it remembers a 0, if the input is on it remembers a 1.

- The `AND` statement recalls the last two numbers remembered and if they are both true the result is a 1, otherwise the result is a 0.
- This result now replaces the two numbers that were recalled, and there is only one number remembered.
- The process is repeated for lines 00003 and 00004, but when these are done there are now three numbers remembered. The oldest number is from the `AND`, the newer numbers are from the two `LD` instructions.
- The `AND` in line 00005 combines the results from the last `LD` instructions and now there are two numbers remembered.


- The OR instruction takes the two numbers now remaining and if either one is a 1 the result is a 1, otherwise the result is a 0. This result replaces the two numbers, and there is now a single number there.
- The last instruction is the ST (store output) that will look at the last value stored and if it is 1, the output will be turned on, if it is 0 the output will be turned off.

- The notation shown above is not standard Allen-Bradley notation. The program to the right would be the A-B equivalent
- The ladder logic program in is equivalent to the mnemonic program.
- Even if you have programmed a PLC with ladder logic, it will be converted to mnemonic form before being used by the PLC.
- In the past mnemonic programming was the most common, but now it is uncommon for users to even see mnemonic programs.

SOR
BST
XIC A
XIO B
NXB
XIO C
XIO D
BND
OTE X
EOR
END

Sequential Function Charts (SFCs)

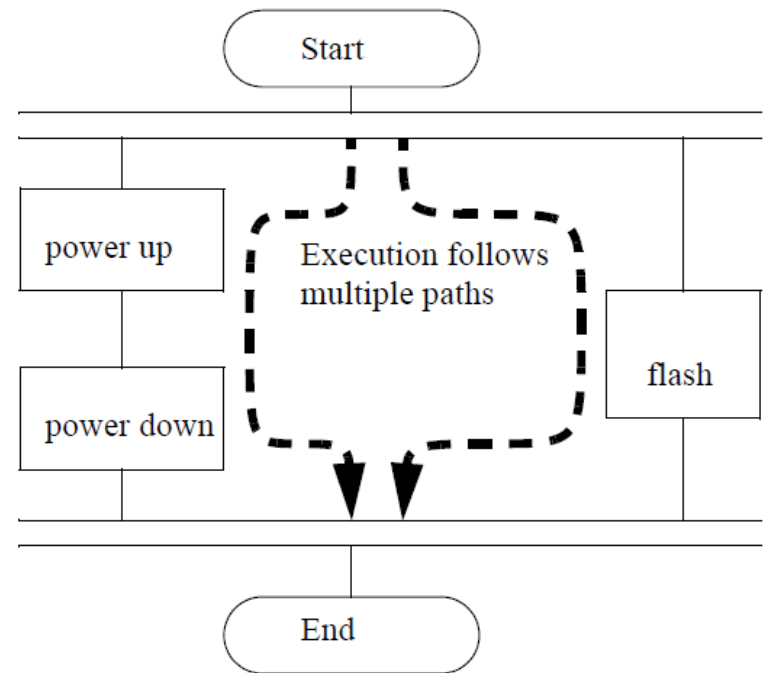- It have been developed to accommodate the programming of more advanced systems.
- The example seen is doing two different things.
- To read the chart, start at the top where is says start.
- Below this there is the double horizontal line that says follow both paths.
- As a result the PLC will start to follow the branch on the left and right hand sides at the same time.



- On the left there are two functions the first one is the power up function. This function will run until it decides it is done, and the power down function will come after.
- On the right hand side is the flash function, this will run until it is done.
- These functions look unexplained, but each function, such as power up will be a small ladder logic program.
- This method is much different from flowcharts because it does not have to follow a single path through the flowchart.

Structured Text programming

- It has been developed as a more modern programming language.
- It is quite similar to languages such as BASIC.
- A simple example is shown below.

```
i := 0;
```

```
REPEAT
```

```
i := i + 1;
```

```
UNTIL i >= 10
```


```
END_REPEAT;
```

- This example uses a PLC memory location i. This memory location is for an integer.


- The first line of the program sets the value to 0. The next line begins a loop, and will be where the loop returns to.
- The next line recalls the value in location i , adds 1 to it and returns it to the same location.
- The next line checks to see if the loop should quit.
- If i is greater than or equal to 10, then the loop will quit, otherwise the computer will go back up to the REPEAT statement continue from there.
- Each time the program goes through this loop i will increase by 1 until the value reaches 10.

PLC connections

- When a process is controlled by a PLC it uses inputs from sensors to make decisions and update outputs to drive actuators, as shown in Figure below.
- The process is a real process that will change over time. Actuators will drive the system to new states (modes of operation).
- This means that the controller is limited by the sensors available, if an input is not available, the controller will have no way to detect a condition.

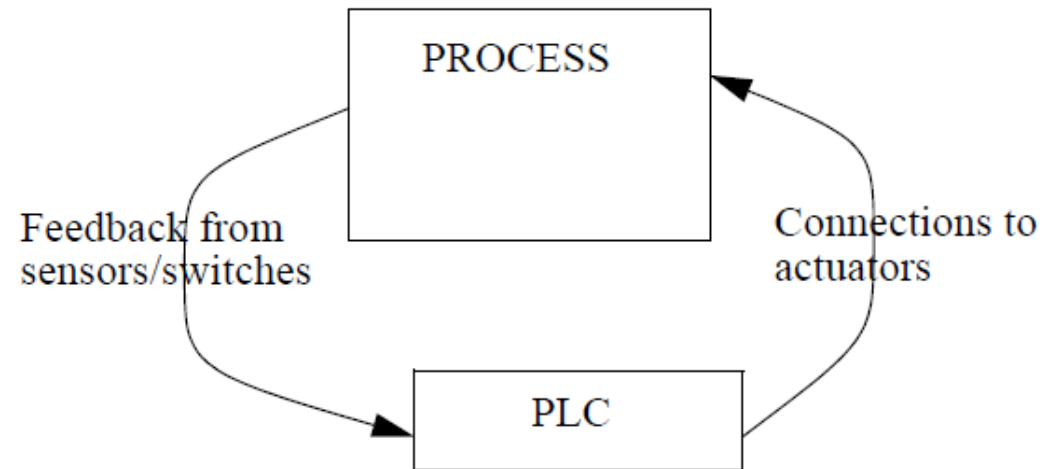

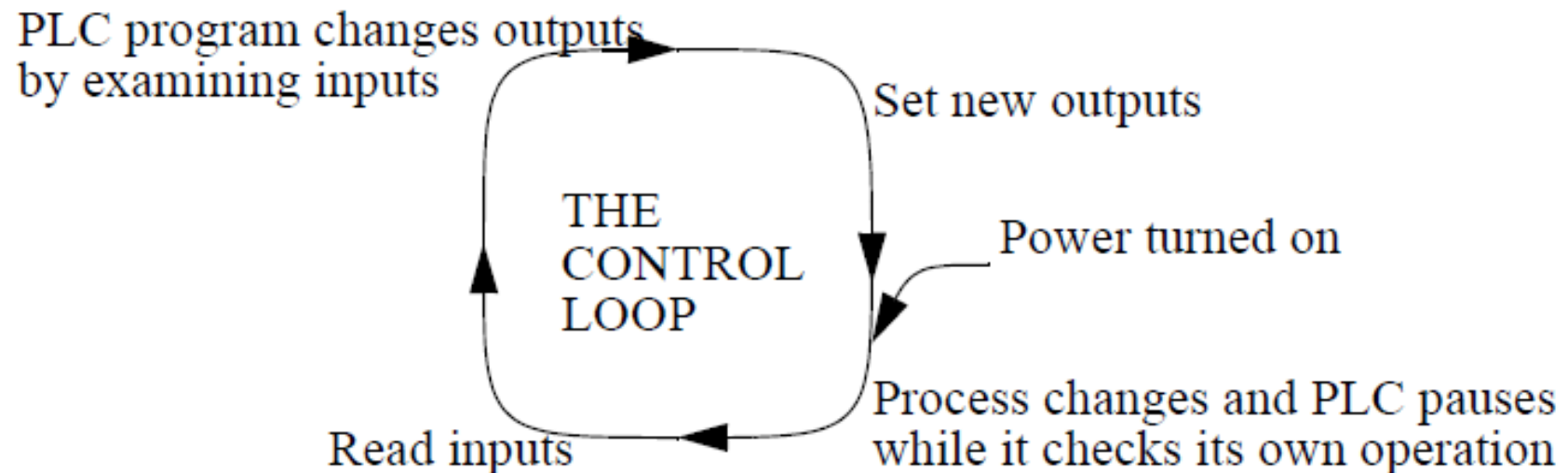- The control loop is a continuous cycle of the PLC reading inputs, solving the ladder logic, and then changing the outputs.
- Like any computer this does not happen instantly. The figure below shows the basic operation cycle of a PLC



- When power is turned on initially the PLC does a quick sanity check to ensure that the hardware is working properly.
- If there is a problem the PLC will halt and indicate there is an error. For example, if the PLC power is dropping and about to go off this will result in one type of fault.
- If the PLC passes the check it will then scan (read) all the inputs.
- After the inputs values are stored in memory the ladder logic will be scanned (solved) using the stored values (not the current values). This is done to prevent logic problems when inputs change during the ladder logic scan.

- When the ladder logic scan is complete the outputs will be scanned (the output values will be changed).
- After this the system goes back to do a sanity check, and the loop continues indefinitely.
- Unlike normal computers, the entire program will be run every scan.
- Typical times for each of the stages is in the order of milliseconds.