

EXP. No. (4)

Three- Phase Transformer Connections

Object:

To study the connection of polarity for 3-phase operation of transformer.

Theory:

For 3-phase operation, we can use a single 3-phase transformer or a bank of three 1-phase transformers. The single unit of 3-phase transformer may cost about 15% less than a bank and will occupy much less space. There is little difference in reliability, but it is cheaper to carry spare for 1-phase than 3-phase transformers, if only one installation is concerned. The usual 3-phase connections are Y-Y, Δ - Δ , Y- Δ , Δ -Y.

Procedure:

Part 1: Checking for polarities of 3-phase transformer coils when the transformer does not connect to supply.

- 1- Make the connection as shown in fig. (1).
- 2- Connect the terminals A2 & B2.
- 3- Apply voltage on the two terminals A1 & B1, and read the voltage on coils C (i.e. C1 & C2), if its read zero or nearly zero the connection (i.e. two terminals A2 & B2) are symmetrical, otherwise the connection is unsymmetrical.
- 4- Repeat 2 and 3 for terminals A2 & B1, terminals A2 & C2, and terminals A2 & C1.

Part 2:

Checking for Y and Δ connections of secondary side of 3-phase transformer when primary side connected to 3-phase supply.

- 1- Make the connection as shown in fig. (2).
- 2- Connect the three terminals a4 b4 c4.
- 3- Apply voltage on primary side Y connected and read the voltmeter across the two terminals a1 b1, the two terminals a1 c1, and the two terminals b1 c1, if three voltages are equals and equals to $\sqrt{3}$ Vph, the three points a4 b4 c4 are

symmetrical and the secondary Y connection is true, otherwise the three points are unsymmetrical and Y connection is fail.

- 4- Repeat 2 and 4 for connections a4 b4 c1, a4 b1 c4, and a4 b1 c1.
- 5- Connect the coil terminal a4 to the coil terminal b1 and b4 to c1.
- 6- Apply voltage on primary side Y connections and read the voltmeter across the two terminals a1 c4, a1b4 and a4c4 , if the voltage across a1c4 is zero, and the voltage across a1b4 and a4c4 are equals and equal to phase voltage, the Δ connection on secondary side is true, otherwise the Δ connection on secondary side is fail.
- 7- Repeat 5 and 6 for connections (a4b1 and b4c4), (a4b4 and b1c1) and (a4b4 and b1c4).

Discussion:

- 1- Draw the phasor diagram of all cases in part 2.
- 2- Compare the advantage and disadvantage of a 3-phase transformer with a bank of three single phase transformer.
- 3- What is connection? Where the connection is used?

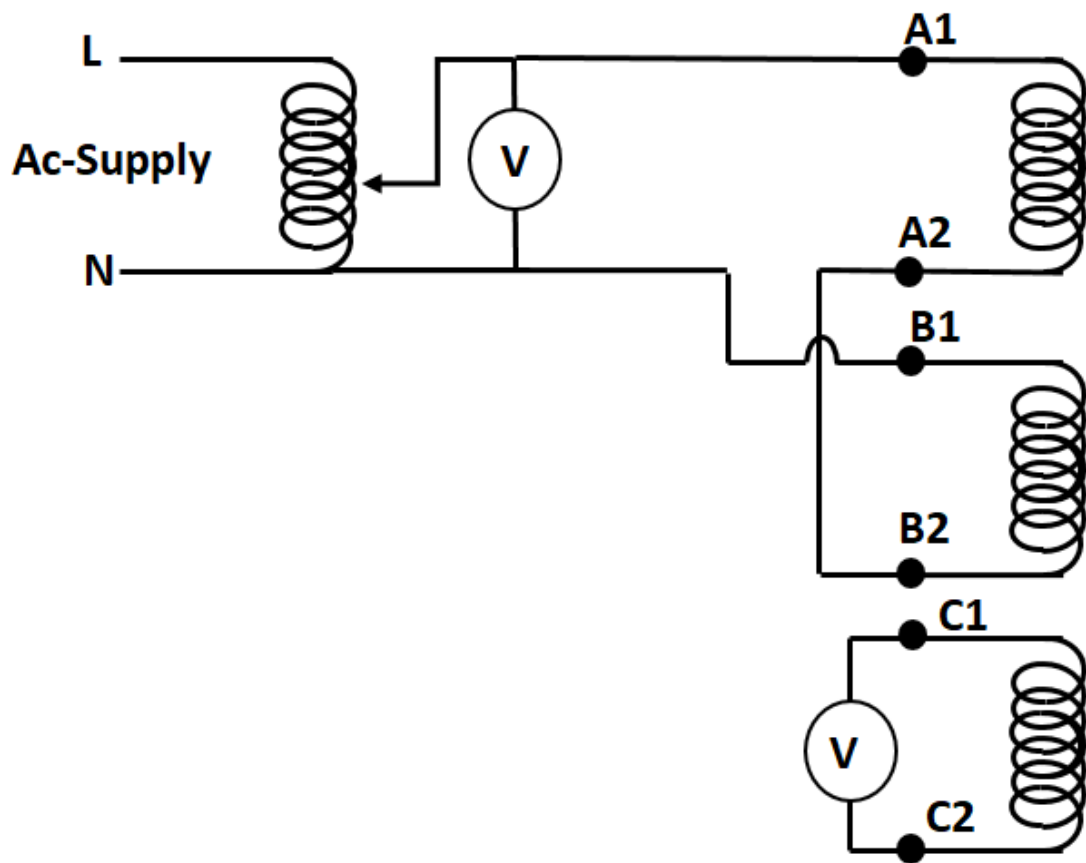


Fig.(1)

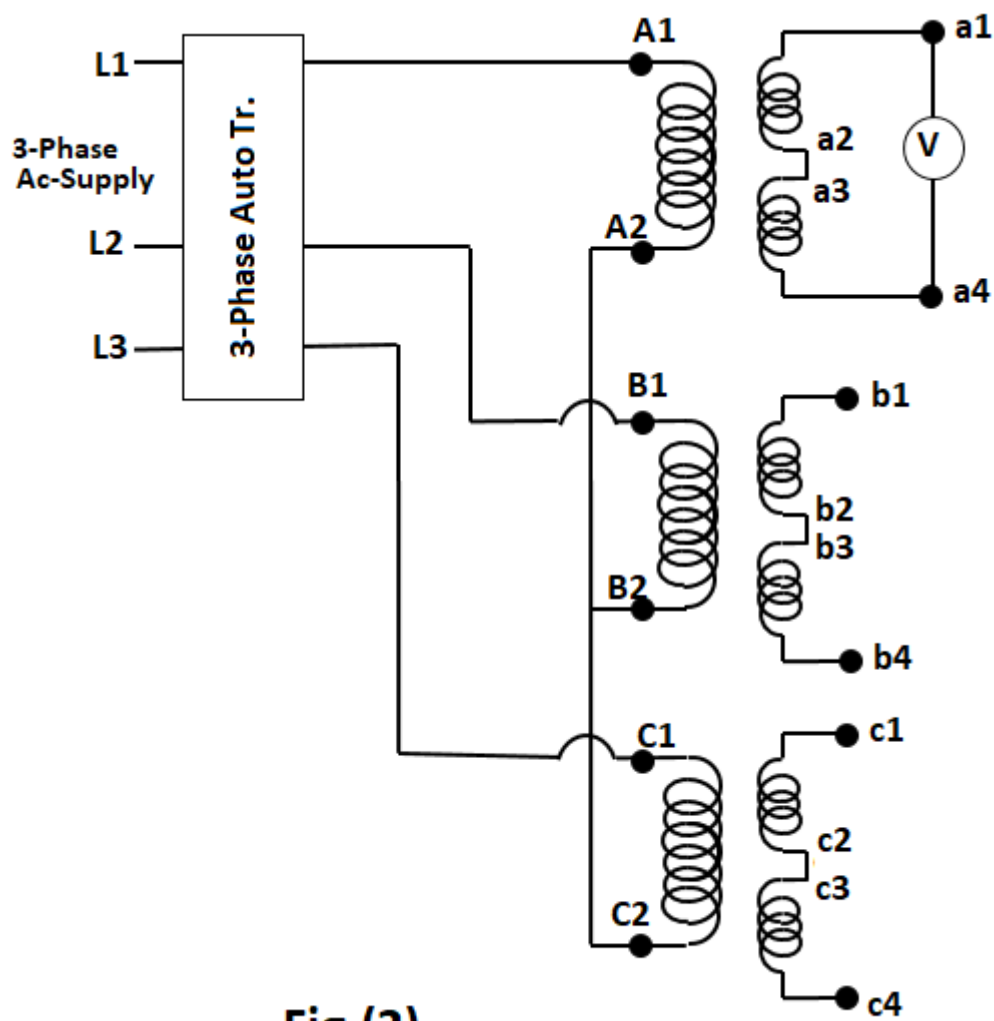


Fig.(2)