

## EXP. No. (1)

### Short Transmission Line

#### **Introduction:**

The effect of capacitance can be neglected in short line in overhead of lines a length of 50 Km to 60 Km in short, but in cables the distance is considerably less before capacitance has an appreciable effect.

So, a short single –phase transmission line may be represented by the equipment circuit shown in fig (1).

#### **Apparatus:**

3 voltmeters, 2 watt meters, 1 ammeter, molded line and suitable variable load.

#### **Object:**

The aim of the experiment is:

1-To determine the parameters of the line (R and  $X_L$ ) as:

$$Z = \frac{|\Delta V|}{|I_r|} \dots \dots \dots (1)$$

$$P_{loss} = P_s - P_r \dots \dots \dots (2)$$

$$P_{loss} = I^2 \cdot R$$

$$X_L = \sqrt{Z^2 - R^2} \dots \dots \dots (3)$$

2- To study the characteristics of the short line ( $\eta$  and  $\mathcal{E}$ )

$\eta$  is the efficiency and  $\mathcal{E}$  is the voltage regulation.

3-To plot the phasor diagram at lag, unity and lead power factor.

#### **Procedure:**

1-Connect the circuit as shown in fig. (1).

2-Set the sending voltage to 100 V, then record  $I_s$ ,  $V_r$ ,  $P_s$ ,  $P_r$  and  $V_d$  at unity power factor.


3-Repeat several times by varying the value of load.


4-Repeat step 2 and 3 at 0.86 lagging and 0.86 leading power factor.

**Report:**


- 1-Plot the phasor diagram at unity, lagging and leading P.F.
- 2-Calculate the ( $\eta\%$ ) and ( $\varepsilon\%$ ).
- 3- Determine the short transmission line parameters( $R$  and  $X_L$ ).

$V_s$ (v)	$I_s$ (A)	$P_s$ (W)	$P_r$ (W)	$V_r$ (v)	$V_D$ (v)	$\eta\%$	$\varepsilon\%$
100							

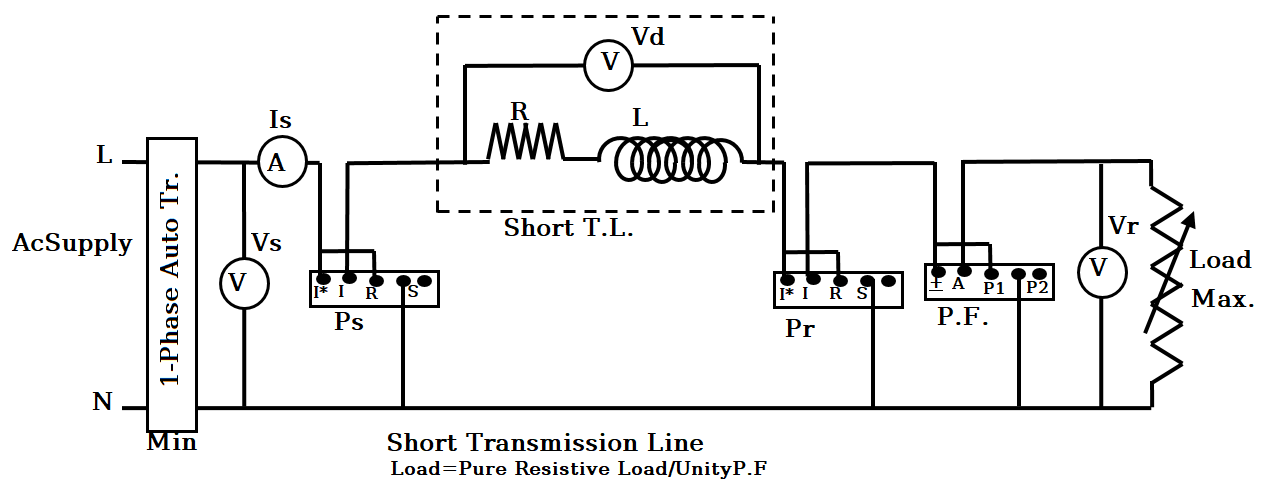

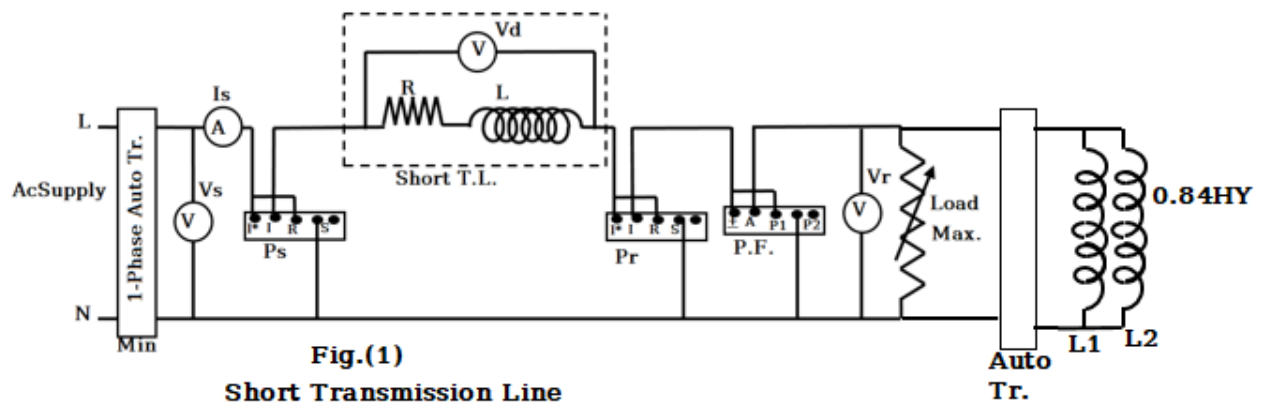

**Fig.(1)**  
**Short Transmission Line**  
**Load=Inductive Load/0.86 Lagging P.F**

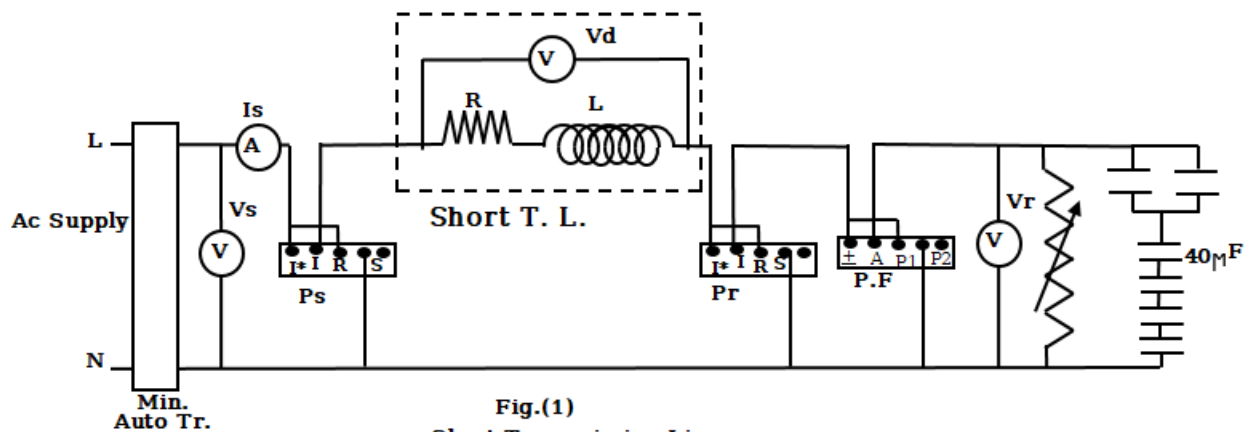

**Fig.(1)**  
**Short Transmission Line**  
**Load=Capacitive Load/0.86 Leading P.F**