



Final (Theoretical/Practical) Exam – 2nd Semester (2023-2024)

(


ناوت به زمانی کوردی)

Q1/Choose the right answer:

(4 marks)

A) The density of this cylinder is:

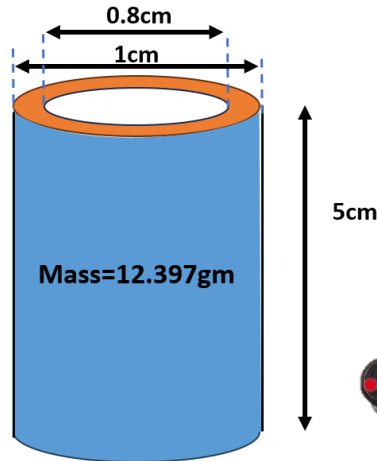- a) 7.78g/cm³
- b) 8.77 g/cm³
- c) 43.84 g/cm³
- d) 34.84g/cm³



B) This physics instrument is called:

- a) Fixed Microscope
- b) Travelling Microscope
- c) Spectrometer
- d) Spectroscope



C) A wire is 1.0 m long and its cross-sectional area is 0.0314 mm² with a resistance of 10 Ω. The resistivity of this material is:

- a) 3.0 × 10⁻⁸ Ω.m
- b) 3.14 × 10⁻⁷ Ω.m
- c) 30 × 10⁻⁸ Ω. m
- d) 314 × 10⁻⁷ Ω.m

D) A sample of oxygen gas has a volume of 225 mL when its pressure is 1.12 atm. What will the volume of the gas be at a pressure of 0.98 atm if the temperature remains constant?

- a) 25.71 mL
- b) 257.1 mL
- c) 19.68 mL
- d) 196.8 mL

Q2/ Write the Ohms law statement, and find the equivalent resistance of circuit consists of R₁=100Ω, R₂=100Ω and R₃=50Ω connected in parallel. (5 marks)


Ohms law: At constant temperature, the electric current flowing in a conducting material is directly proportional to the applied voltage.

R_{eq} (write the solution): $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} =$

∴ R_{eq} = Ω

R ₁ (Ω)	R ₂ (Ω)	R ₃ (Ω)	R _{eq} (Ω)
100	100	50	25
200	200	100	50
100	50	50	20

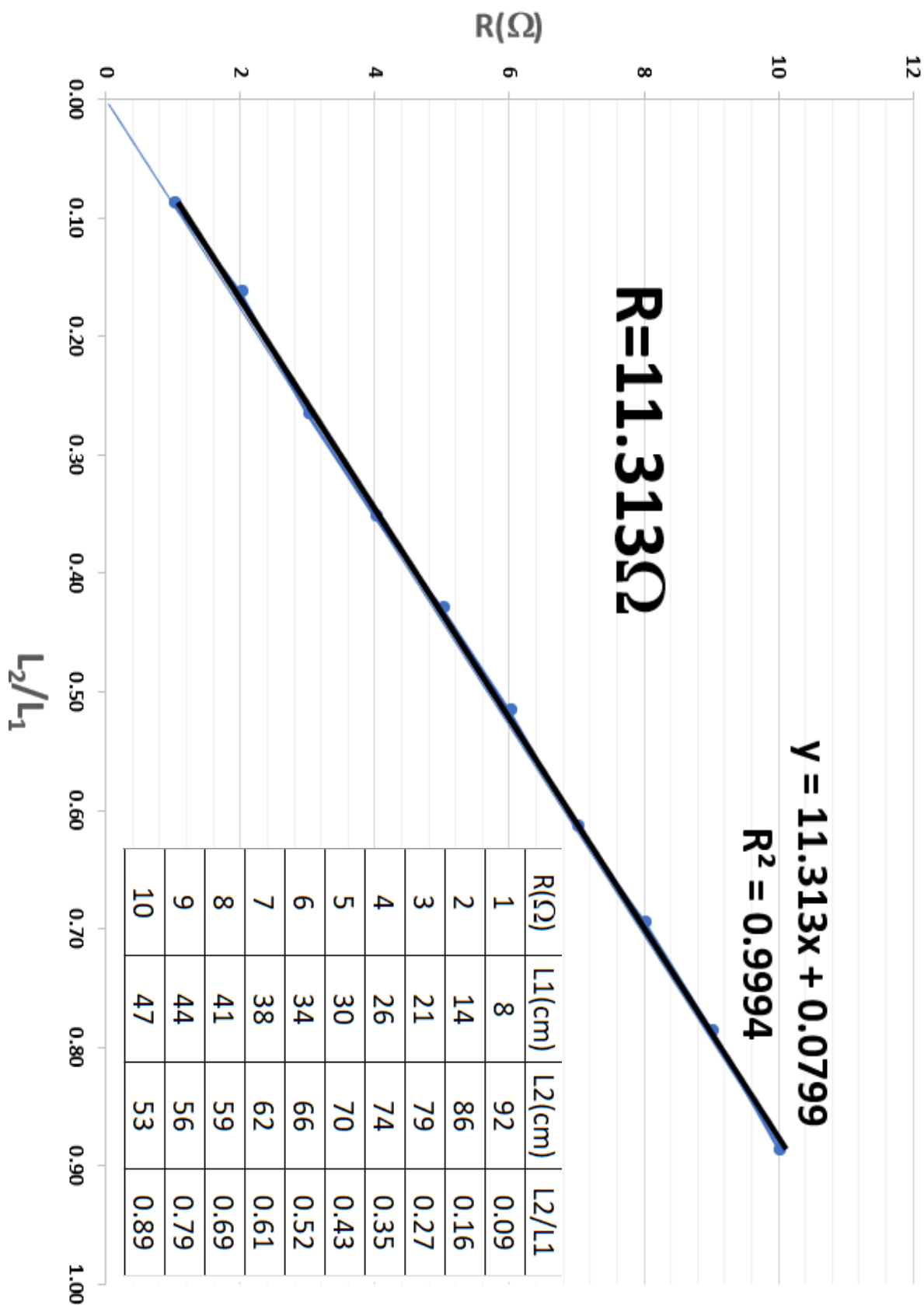Q3/ From **Wheatstone bridge**, use the following data to determine the value of the unknown resistance: **(6 marks)**



Staff of the Instrumentation Physics Lab.: 1. Dr. Kasim Fawzy Ahmed 2. Dr. Diyar Ali Rasool

3. Dr. Kadhim Qasim Jabbar 4. Mrs. Khadija Najmdeen Abdulla