


..... :ناو

1) The galvanometer has following applications:

A- It is used for detecting the of current flows in the circuit.

B- It is used for measuring the

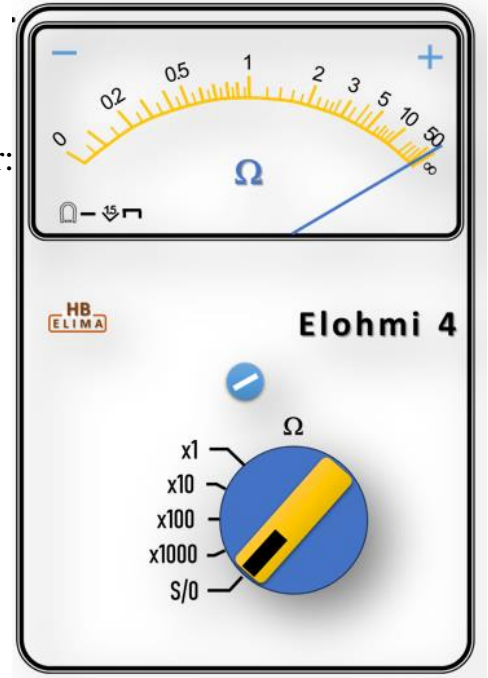2) Write the electrical circuit of the following Ohmmeter:



..... :ناو

1) The galvanometer has following applications:

A- It is used for detecting the of current flows in the circuit.

B- It is used for measuring the

2) Write the electrical circuit of the following Ohmmeter:

