

Exp. No. 1: Half and Full Adder


Maha George Zia

Assistant professor

Electrical Engineering department


Binary addition

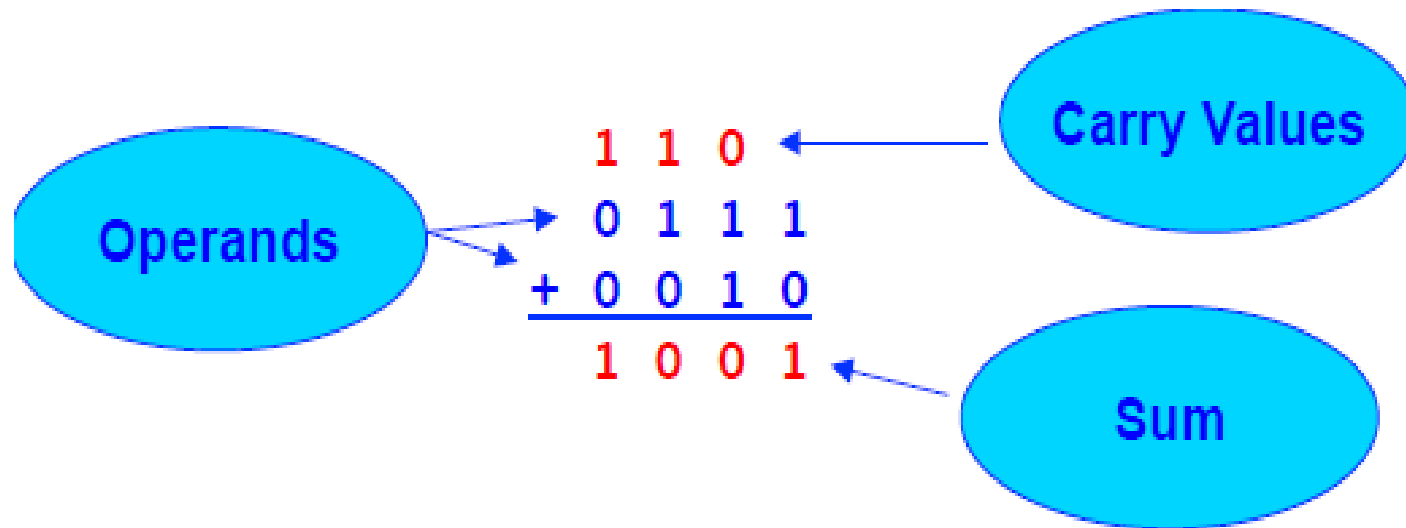- $0 + 0$ is a sum of 0 with a carry of 0
- $1 + 0$ is a sum of 1 with a carry of 0
- $0 + 1$ is a sum of 1 with a carry of 0
- $1 + 1$ is a sum of 0 with a carry of 1




Half adder Circuit

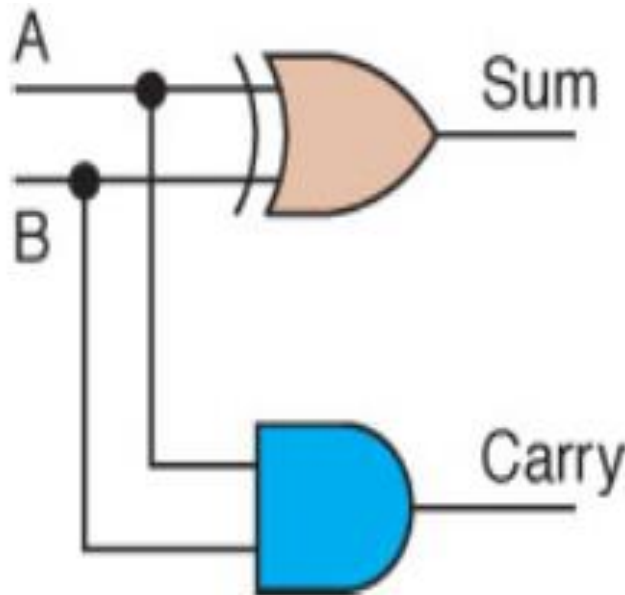Is a combinational circuit that adds two bits




$$\text{Sum} = A \text{ XOR } B$$
$$\text{Carry} = A \text{ AND } B$$

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

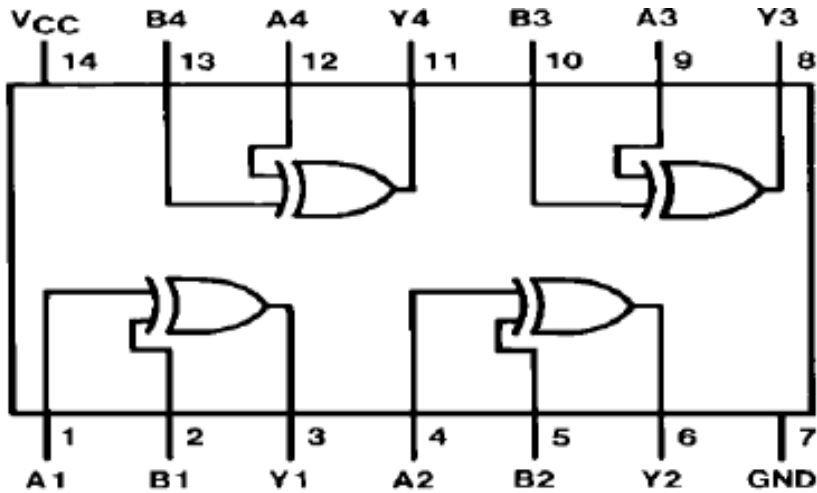

Pin diagram of 7486 XOR

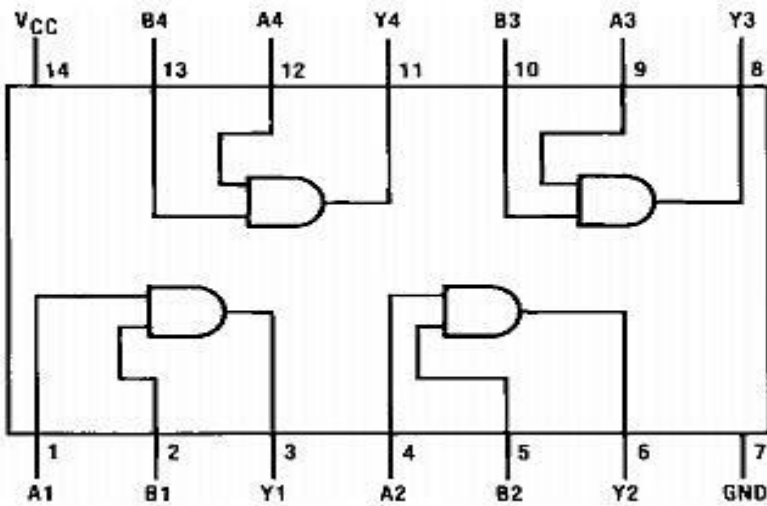


Pin diagram of 7408 Quad 2-input AND gates

Full adder circuit

- Is a combinational circuit that adds three bits (A, B, Carry-in (C_i))

The **full adder** takes 3 inputs:



- A, B, and a **carry-in** value

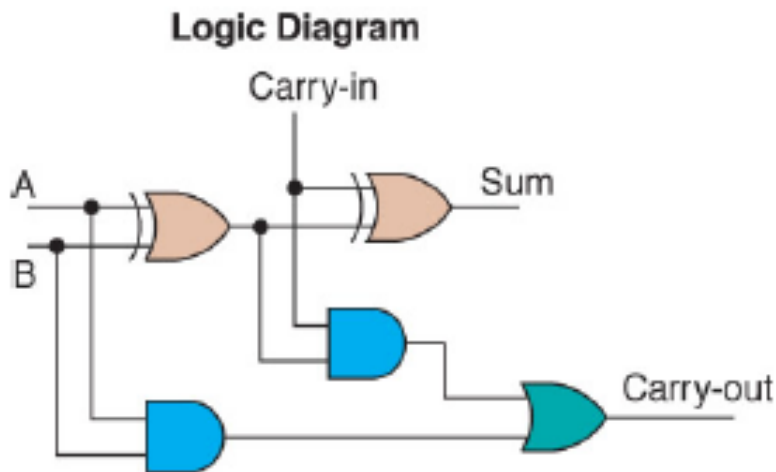

Truth Table

A	B	Carry-in	Sum	Carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

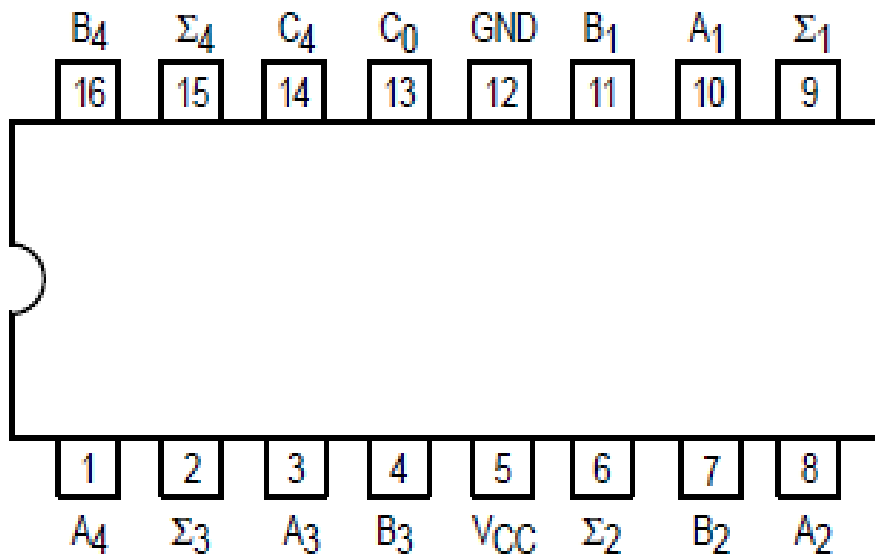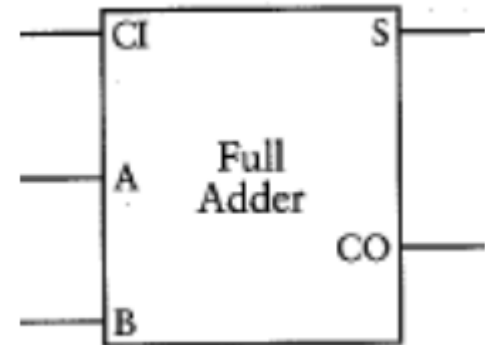- inputs are A, B, and CI.
- outputs are S and CO




Pin diagram of 7483 4-bit Full adder

$A_1 - A_4$
 $B_1 - B_4$
 C_0
 $\Sigma_1 - \Sigma_4$
 C_4

Operand A Inputs
 Operand B Inputs
 Carry Input
 Sum Outputs
 Carry Output

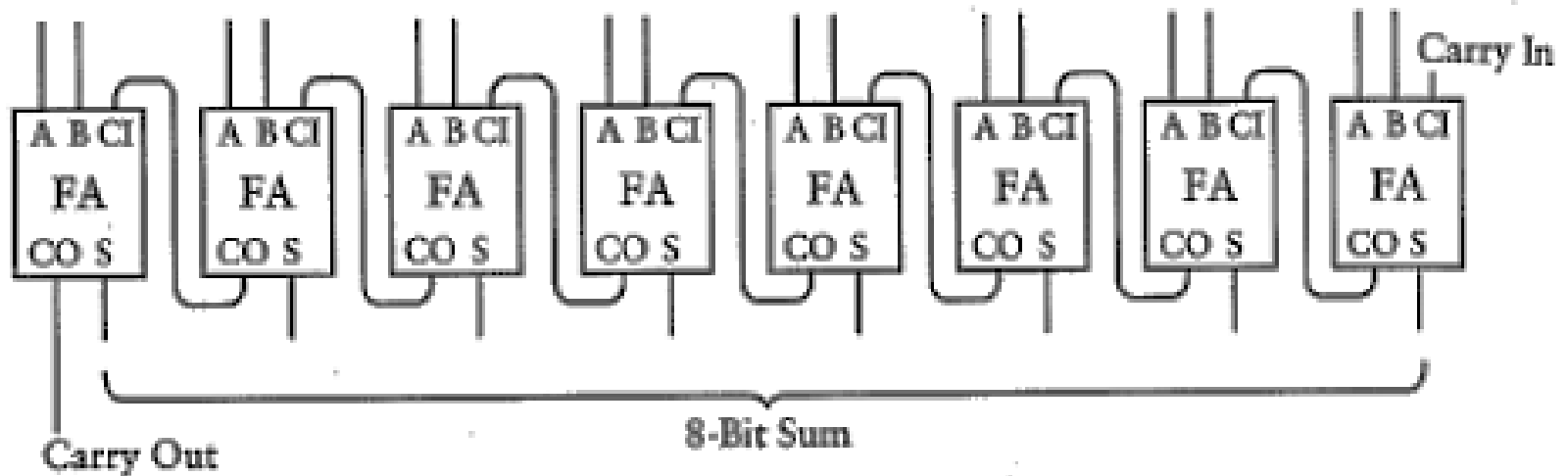- Example: Add two 8-bit binary numbers
- Solution: we need an 8-bit adder



Notice how the carry out from one bit's adder becomes the carry-in to the next adder

