

# Exp. No. 10 Encoding / Decoding and Displaying

# Encoders

- An encoder is a digital circuit that performs the inverse operation of a decoder. An encoder has  $2^n$  (or fewer) input lines and  $n$  output lines.
- The output lines, generate the binary code corresponding to the input value. An example of an encoder is the octal-to-binary encoder whose truth table is given below:

*Truth Table of an Octal-to-Binary Encoder*


Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

- According to the truth table, the outputs are:


$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

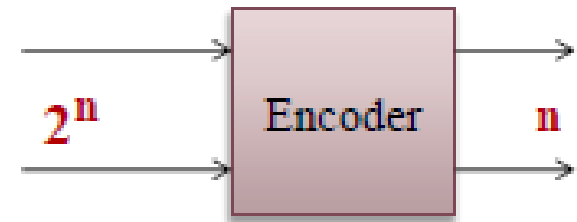

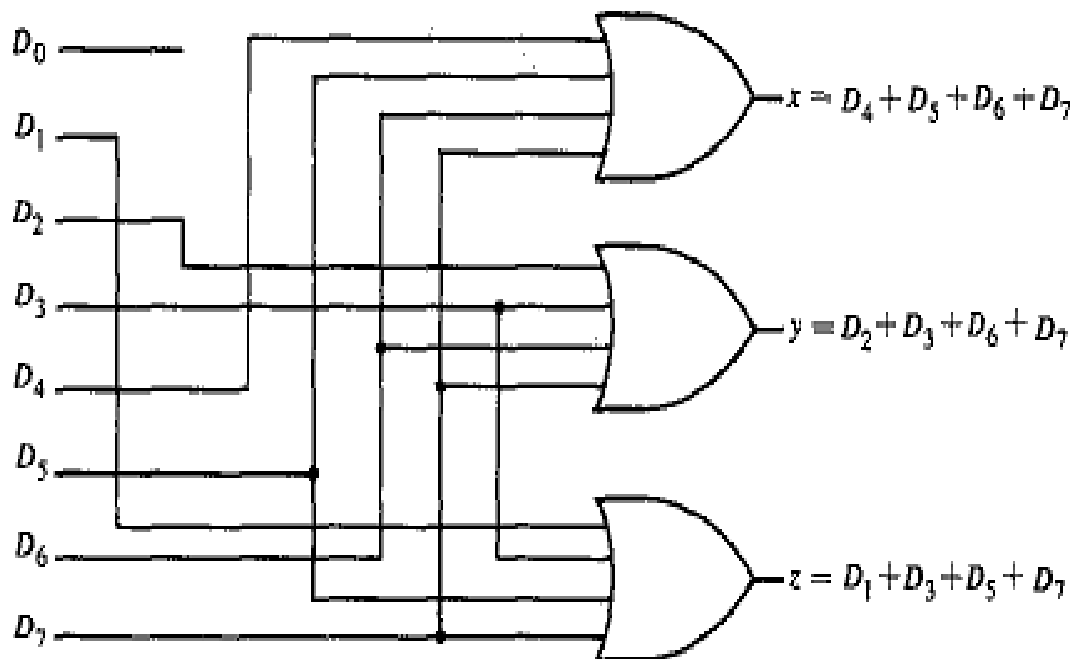
- The encoder can be implemented with three OR gates



8-to-3 line encoder
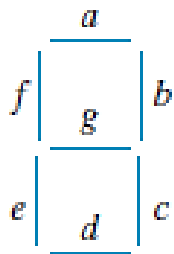
# Decoder

- A *decoder* is a combinational circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines. If the  $n$ -bit coded information has unused combinations, the decoder may have fewer than  $2^n$  outputs.
- **The name *decoder* is also used in conjunction with other code converters, such as a BCD-to-seven-segment decoder.**



(a) Segment designation





(b) Numerical designation for display

Consider the three-to-eight-line decoder circuit of Figure below. A particular application of this decoder is binary-to-octal conversion

*Truth Table of a Three-to-Eight-Line Decoder*

Inputs			Outputs							
$x$	$y$	$z$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

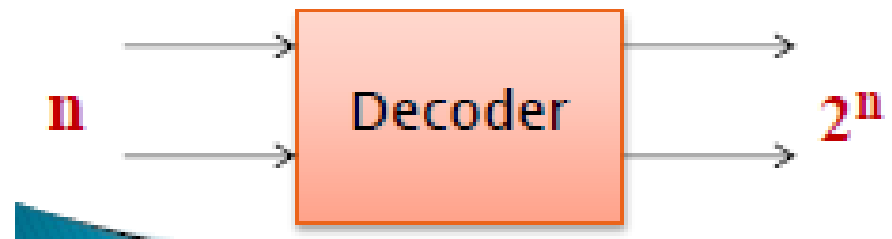


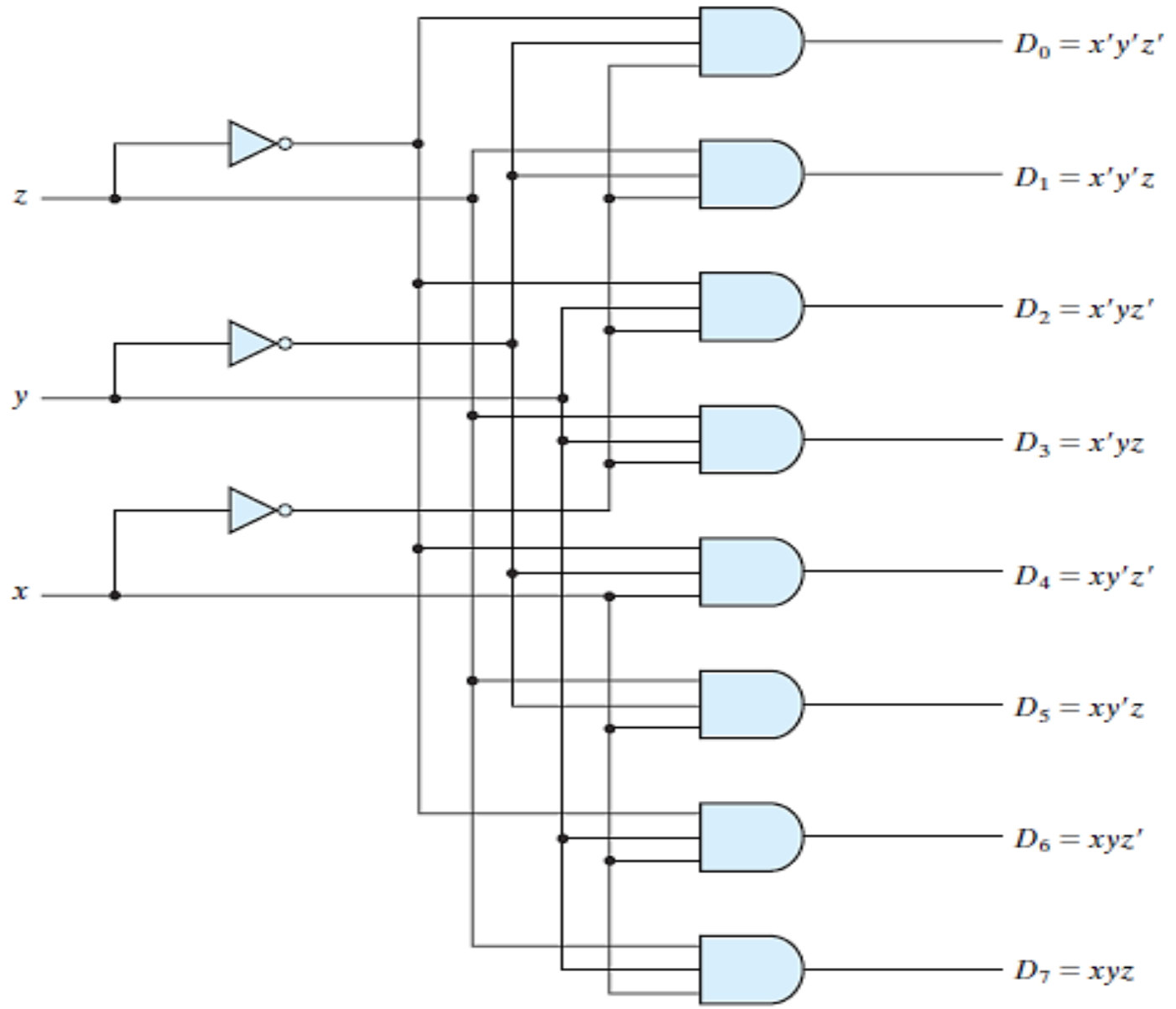

# Common Cathode and Common Anode Format

Two important types of 7-segment LED digital display.

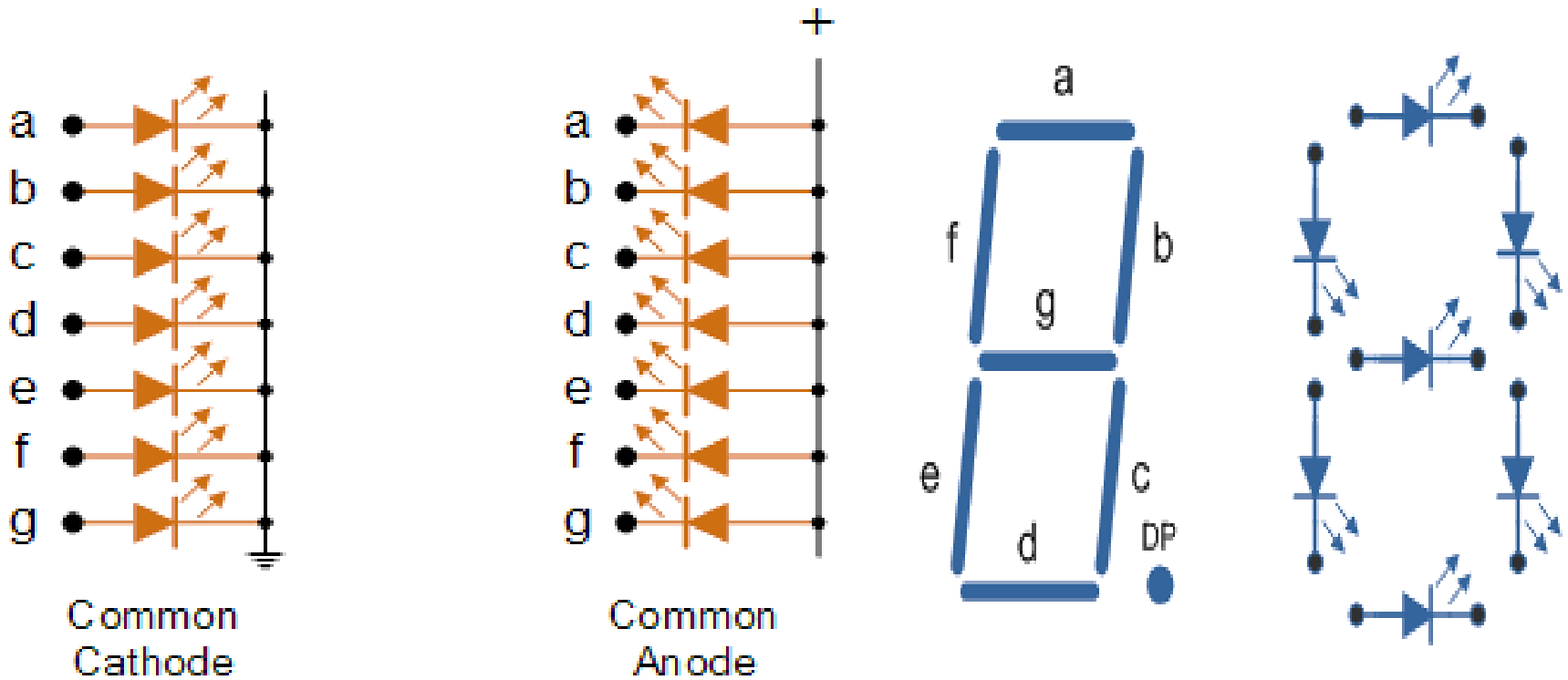- 1. **The Common Cathode Display (CCD)** – In the common cathode display, all the cathode connections of the LED's are joined together to logic “0” or ground. The individual segments are illuminated by application of a “HIGH”, logic “1” signal to the individual Anode terminals.
- 2. **The Common Anode Display (CAD)** – In the common anode display, all the anode connections of the LED's are joined together to logic “1” and the individual segments are illuminated by connecting the individual Cathode terminals to a “LOW”, logic “0” signal.



Electrical connection of the individual diodes for a common cathode display and a common anode display and by illuminating each light emitting diode individually, they can be made to display a variety of numbers or characters.






So in order to display the number 3 for example, segments a, b, c, d and g would need to be illuminated. **Truth Table for a 7-segment display**

Individual Segments							Display
a	b	c	d	e	f	g	
×	×	×	×	×	×		0
	×	×					1
×	×		×	×		×	2
×	×	×	×			×	3
	×	×			×	×	4
×		×	×		×	×	5
×		×	×	×	×	×	6
×	×	×					7

Individual Segments							Display
a	b	c	d	e	f	g	
x	x	x	x	x	x	x	8
x	x	x	x		x	x	9
x	x	x		x	x	x	A
		x	x	x	x	x	b
x			x	x	x		C
	x	x	x	x		x	d
x			x	x	x	x	E
x				x	x	x	F

- it can be seen that to display any single digit number from 0 to 9 in binary or letters from A to F in hexadecimal, we would require 7 separate segment connections plus one additional connection for the LED's "common" connection.
- 
- Also as the segments are basically a standard light emitting diode, **the driving circuit would need to produce up to 20mA of current to illuminate each individual segment** and to display the number 8, all 7 segments would need to be lit resulting a total current of nearly 140mA, (8 x 20mA).
- Obviously, the use of so many connections and power consumption is impractical for some electronic or microprocessor based circuits and **so in order to reduce the number of signal lines required to drive just one single display, display decoders such as the BCD to 7-Segment Display Decoder and Driver IC's are used instead.**

# BCD to 7-Segment Display Decoders

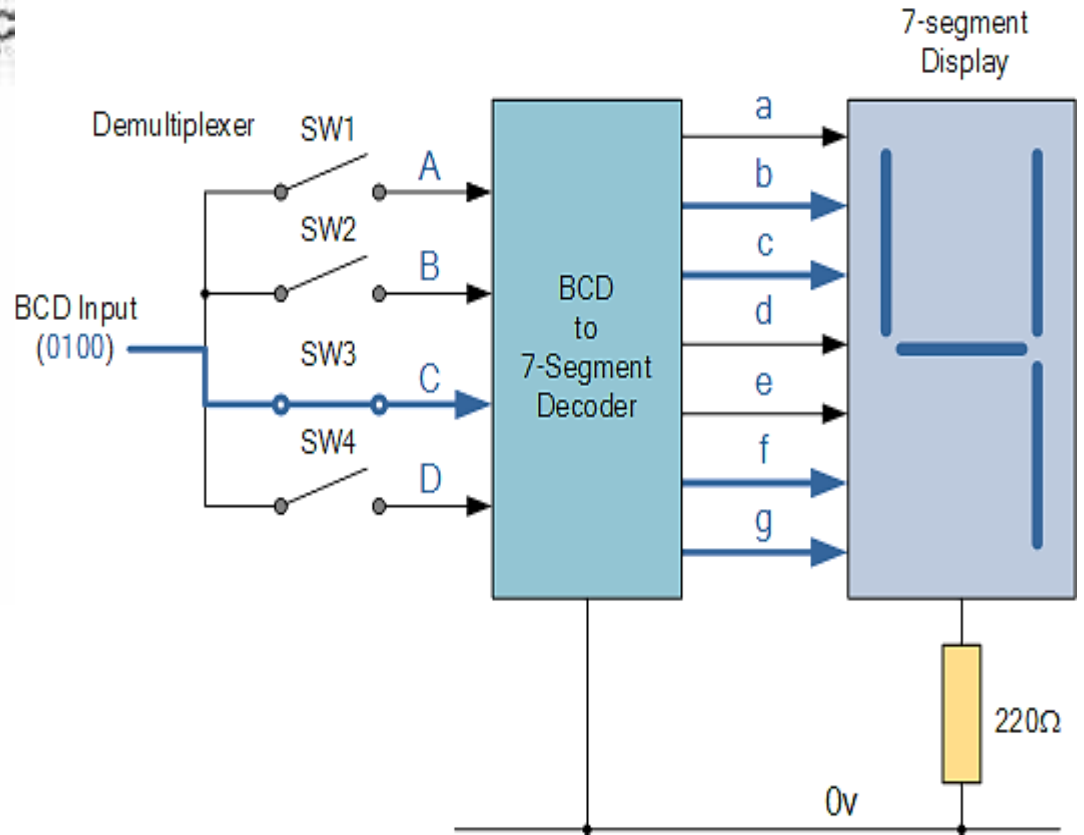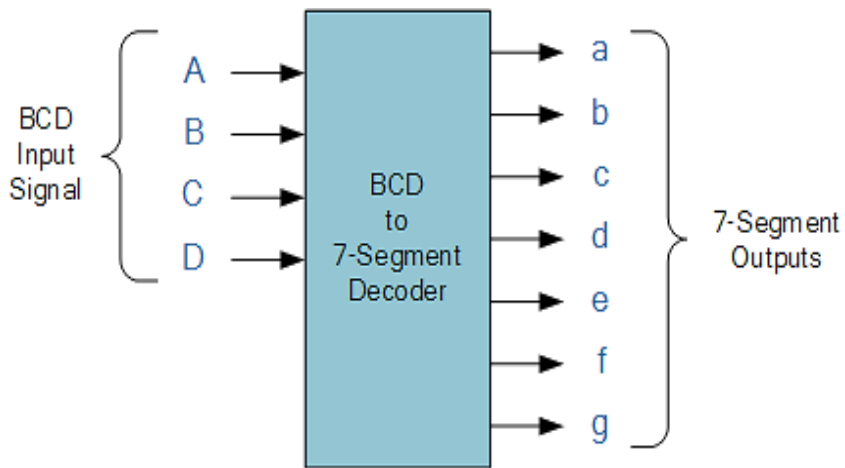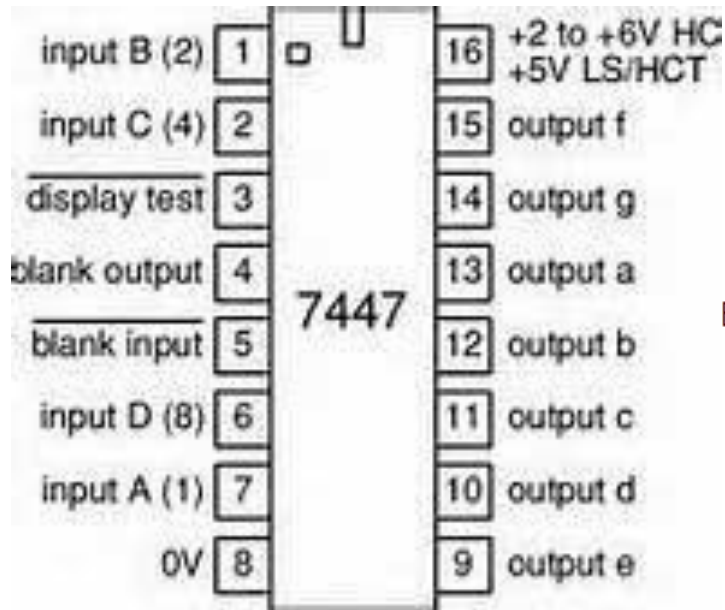

An example of the 4-bit BCD input ( 0100 ) representing the number 4