


# Exp. No. 3 Parity generator- checker and controlled inverter

- ❖ **One important application of the use of an Exclusive-OR gate is to generate parity.**
- ❖ Parity is used to detect errors in transmitted data caused by noise or other disturbances.
- ❖ **A parity bit is an extra bit that is added to a data word and can be either odd or even parity.**
- ❖ **In an even parity system, the sum of all the bits (including the parity bit) is an even number**
- ❖ **In an odd parity system the sum of all the bits must be an odd number.**

- ❖ The circuit that creates the parity bit at the transmitter is called the parity generator.
- ❖ The circuit that determines if the received data is correct is the parity checker.
- ❖ **Parity is good for detecting a single bit error only.**
- ❖ The parity generator and the parity checker can both be built using Exclusive-OR gates.
- ❖ *In even parity bit scheme, the parity bit is '0' if there are even number of 1s in the data stream and the parity bit is '1' if there are odd number of 1s in the data stream.*

- ❖ In odd parity bit scheme, the parity bit is '1' if there are **even number of 1s** in the data stream and the parity bit is '0' if there are **odd number of 1s** in the data stream.

## 7486 XOR

 

# Even Parity Generator

- The total number of 1s must be **even**, to generate the even parity bit P.


$$P = \bar{A} \bar{B} C + \bar{A} B \bar{C} + A \bar{B} \bar{C} + A B C$$

$$= \bar{A} (\bar{B} C + B \bar{C}) + A (\bar{B} \bar{C} + B C)$$

$$= \bar{A} (B \oplus C) + A (\overline{B \oplus C})$$

$$P = A \oplus B \oplus C$$

3-bit message			Even parity bit generator (P)
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

# Odd Parity Generator

- The total number of 1s must be **odd**, to generate the even parity bit P.

3-bit message			Odd parity bit generator (P)
A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

	BC	00	01	11	10
A		0	1	3	2
00		1	0	1	0
01		0	1	0	1


H.W: find the expression of odd parity generator from k-map and plot its logic circuit

# Even Parity Checker

The below table shows the truth table for the even parity checker in which **parity error check (PEC) = 1** if the error occurs, i.e., the four bits received have odd number of 1s and *PEC = 0* if no error occurs, i.e., if the 4-bit message has even number of 1s.

4-bit received message				Parity error check $C_p$
A	B	C	P	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0


$$\begin{aligned}
 PEC &= \bar{A} \bar{B} (\bar{C} D + \underline{C} \bar{D}) + \bar{A} B (\bar{C} \bar{D} + CD) + A B (\bar{C} D + C \bar{D}) + A \bar{B} (\bar{C} \bar{D} + CD) \\
 &= \bar{A} \bar{B} (C \oplus D) + \bar{A} B (\overline{C \oplus D}) + A B (C \oplus D) + A \bar{B} (\overline{C \oplus D}) \\
 &= (\bar{A} \bar{B} + A B) (C \oplus D) + (\bar{A} B + \underline{A} \bar{B}) (\overline{C \oplus D}) \\
 &= (A \oplus B) \oplus (C \oplus D)
 \end{aligned}$$

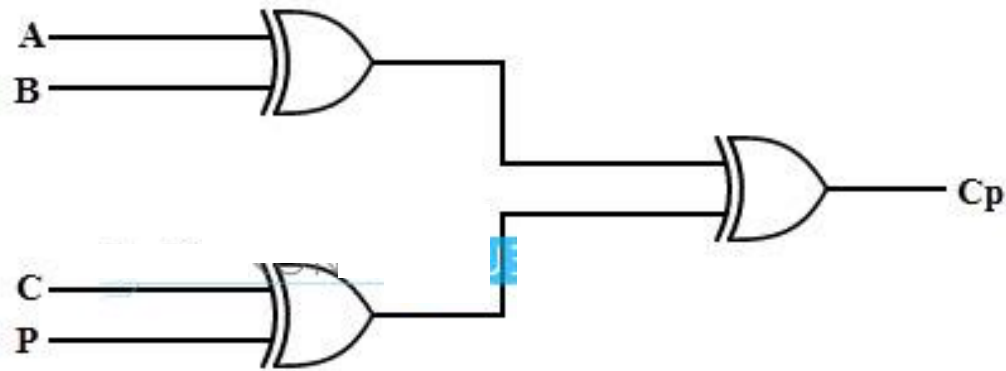



 
# Controlled inverter

It can be seen from the figure and the accompanying truth table that **XOR gate works as NOT (inverter) gate** when its one input is held high, *and as a buffer when the same input is pulled low.*



ICI (A1-A2) = 74LS 86

 



TRUTH TABLE I  
XOR Gate

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

A=1,  
then  
B'=Y  
and  
B=Y'

B=1, then A=Y' and  
A'=Y

XOR gate as controlled inverter

 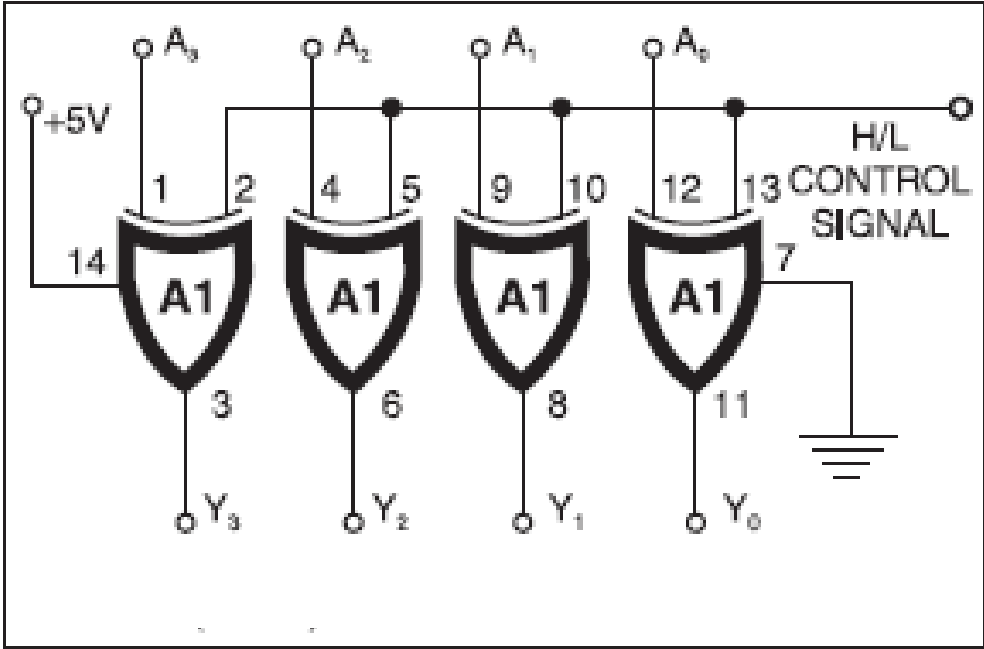

7486 XOR

