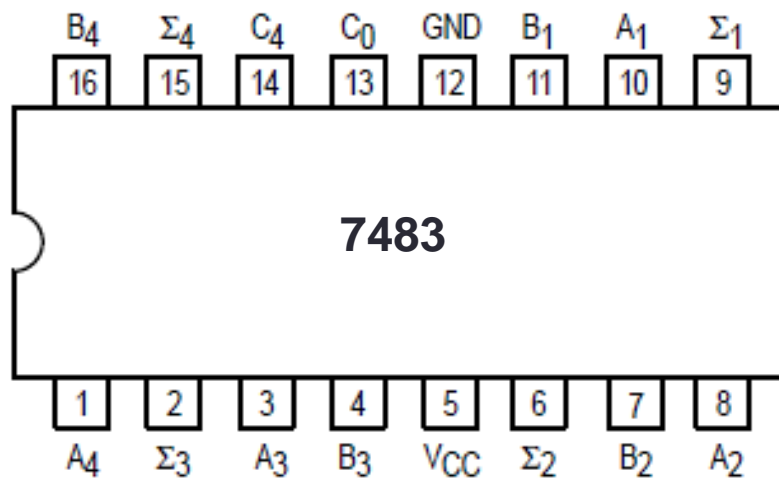


EXP. NO. 5

2'S COMPLEMENT ADDER-SUBTRACTOR


Full-Adder IC 7483

- inputs are A, B, and CI.
- outputs are S and CO



A₁–A₄
 B₁–B₄
 C₀
 Σ₁–Σ₄
 C₄

 Operand A Inputs
 Operand B Inputs
 Carry Input
 Sum Outputs (Note b)
 Carry Output (Note b)




Addition and subtraction operations


Using XOR gate properties:

- 1- **Mode M=1** : $x \oplus 1 = \bar{x}$, the carry in (C_i) =1, and the
• **output = A + (2's complement of B)**, we have **subtraction operation**
- 2- **Mode M=0** : $x + 0 = x$, the carry in (C_i) =0, and the
• **output = A + B**, we have ***addition operation***

four bit binary parallel adder

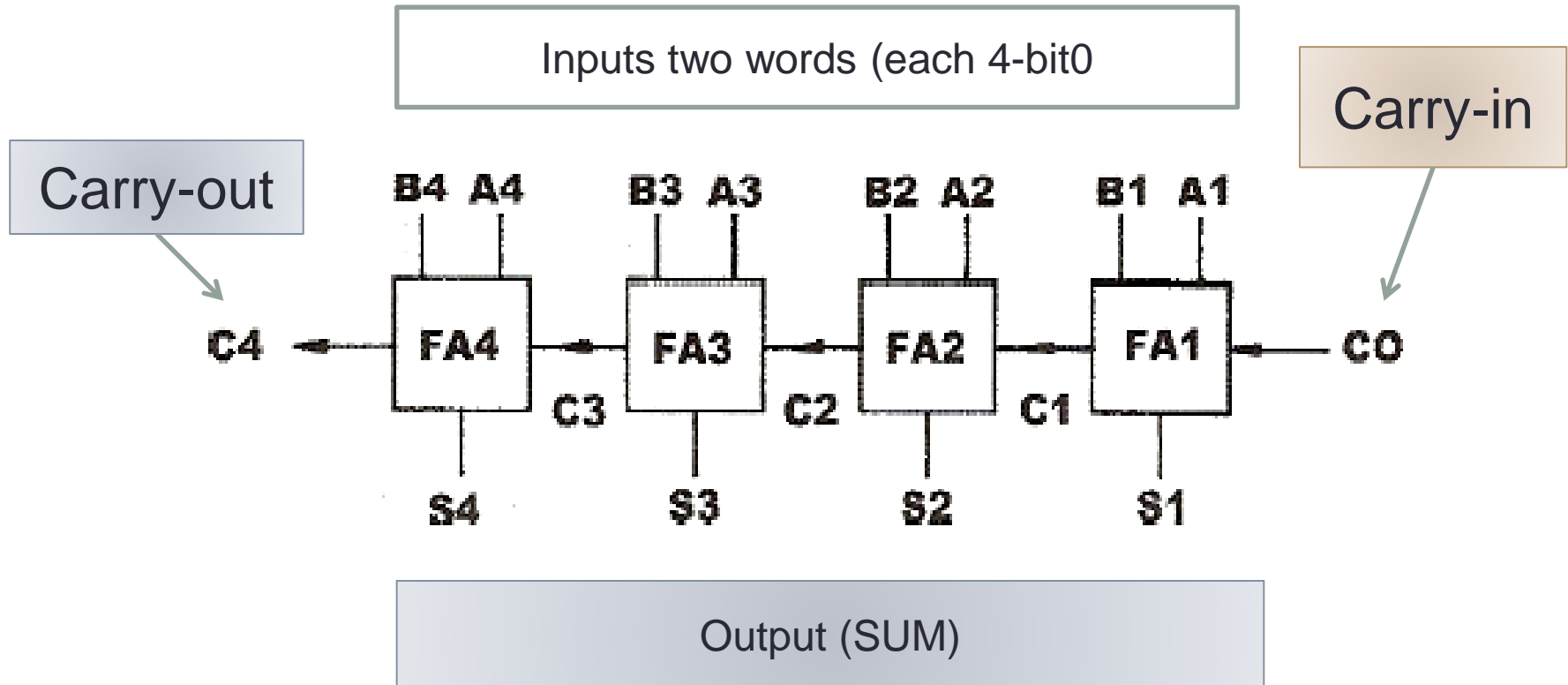

Adder-Subtractor using IC 7483

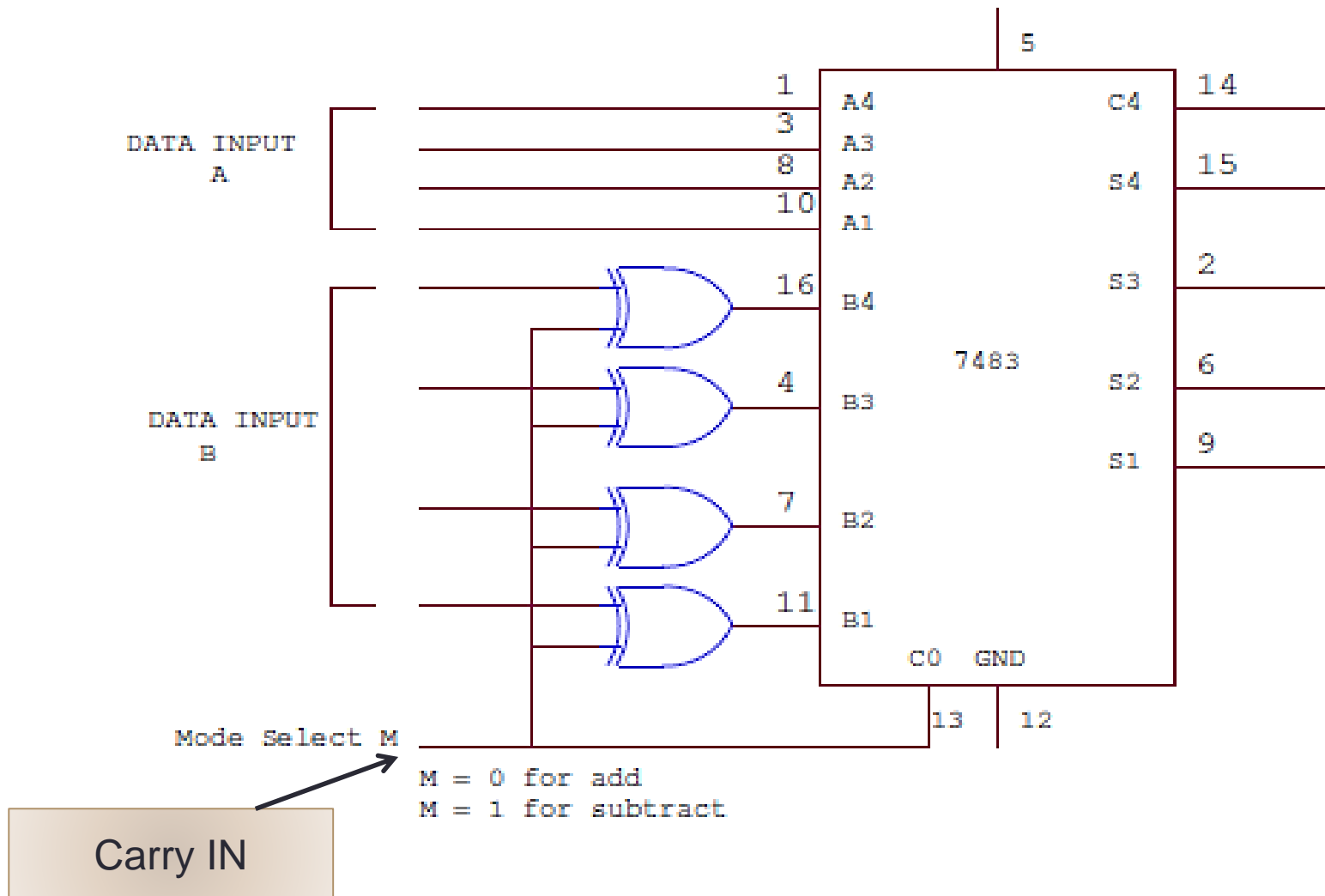

Example: Given the two binary numbers $X = 1010100$ and $Y = 1000011$, perform the subtraction (a) $X - Y$ and (b) $Y - X$ **using 1's complements**

$$(a) X - Y = 1010100 - 1000011$$

$$\begin{array}{r}
 X = \quad \quad \quad 1010100 \\
 \text{1's complement of } Y = \quad + \underline{0111100} \\
 \text{Sum} = \quad \quad \quad 10010000 \\
 \text{End-around carry} \quad \quad \quad \rightarrow + 1 \\
 \text{Answer: } X - Y = \quad \quad \quad \underline{0010001}
 \end{array}$$


$$(b) Y - X = 1000011 - 1010100$$

$$\begin{array}{r}
 Y = \quad \quad \quad 1000011 \\
 \text{1's complement of } X = \quad + \underline{0101011} \\
 \text{Sum} = \quad \quad \quad 1101110
 \end{array}$$

There is no end carry.

$$\text{Answer: } Y - X = -(1\text{'s complement of } 1101110) = -0010001$$

Circuit for 1's complement (4-bit)

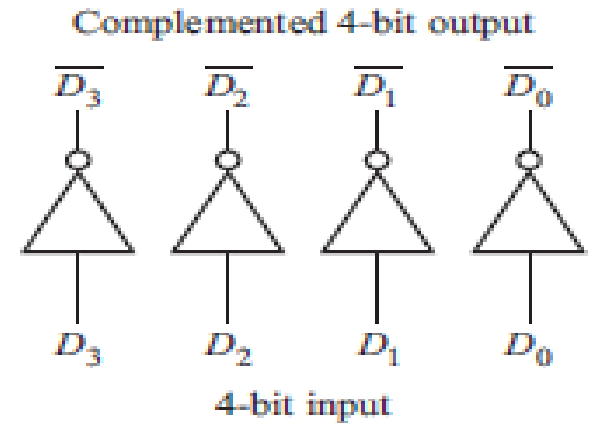

Subtractor circuit

