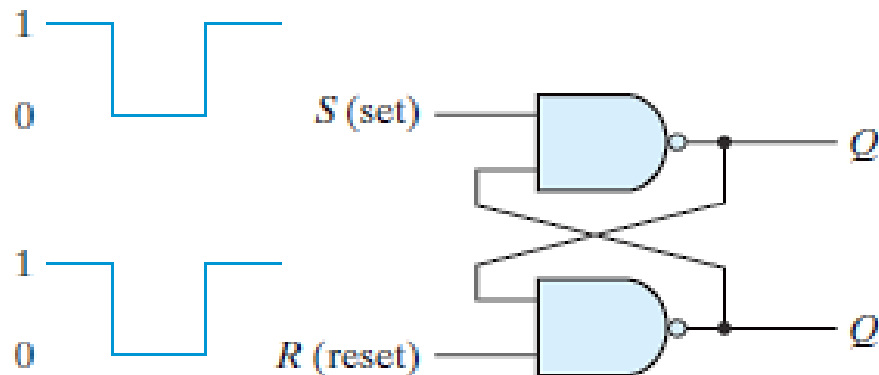



Exp. No.6 Flip-Flops

SR- Latch (without clock)

- ❑ Storage elements that operate with signal levels (rather than signal transitions) are referred to as latches ; **those controlled by a clock transition are flip-flops .**
- ❑ Latches are said to be level sensitive devices; **flip-flops are edge-sensitive devices.**




(a) Logic diagram

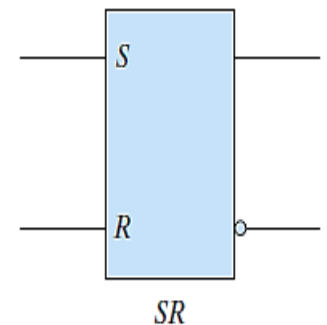

(b) SR Latch block diagram

 (a) SR latch with NAND gates

- **Note: Each flip flop is a binary cell capable of storing one bit of information. For example to store 4-bits we need 4 flip-flops.**



S	R	Q	Q'	
1	0	1	0	
0	0	1	0	(after $S = 1, R = 0$)
0	1	0	1	
0	0	0	1	(after $S = 0, R = 1$)
1	1	0	0	(forbidden)

(b) Function table

SR latch with NOR gates



(a) Response to positive level




(b) Positive-edge response




(c) Negative-edge response

 
(a) response in latch and (b,c) clock applied to flip-flop



Pin diagram of 7400N NAND

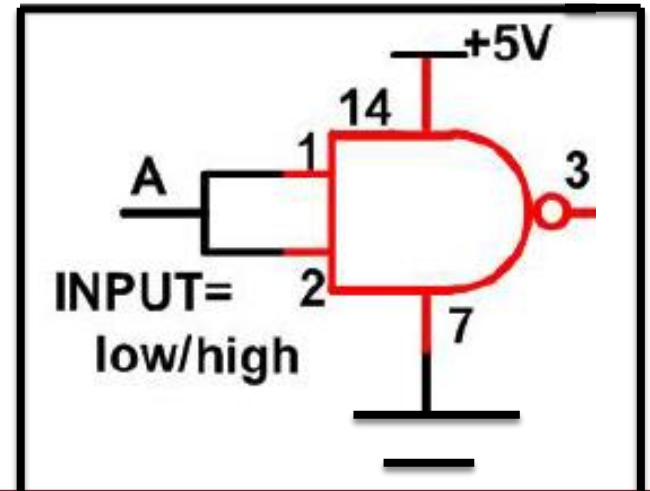


NAND gate connected as NOT gate

 

Pin diagram of 7486 XOR

SR Flip-Flop

 - flip-flops are edge-sensitive devices and controlled by clock(clk , cp , En , Enable)




(a) Logic diagram

En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate


(b) Function table

SR Flip - Flop


D Flip-Flop

 

(a) Positive-edge

 

(a) Negative-edge

 

(a) Logic diagram




D Flip-Flop

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state


(b) Function table

JK Flip-Flop

$$D = JQ' + K'Q$$

 

(a) Circuit diagram

 


(b) Graphic symbol

JK Flip-Flop Characteristic Tables

JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement


7472 IC (JK FF)

(TOP VIEW)

 


$$D = JQ' + K'Q$$

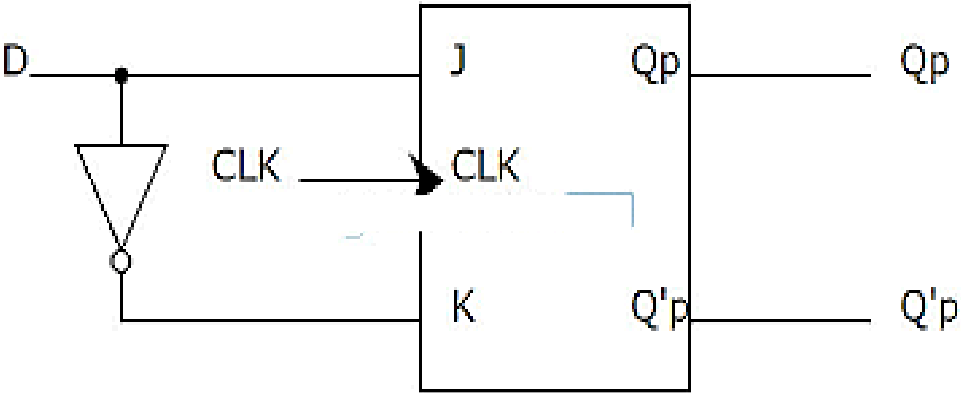If $K = D'$, and $J = D$ then $D = DQ' + DQ = D$ and the JK flip flop is connected as D Flip flop.



- T Flip Flop (Toggle)**

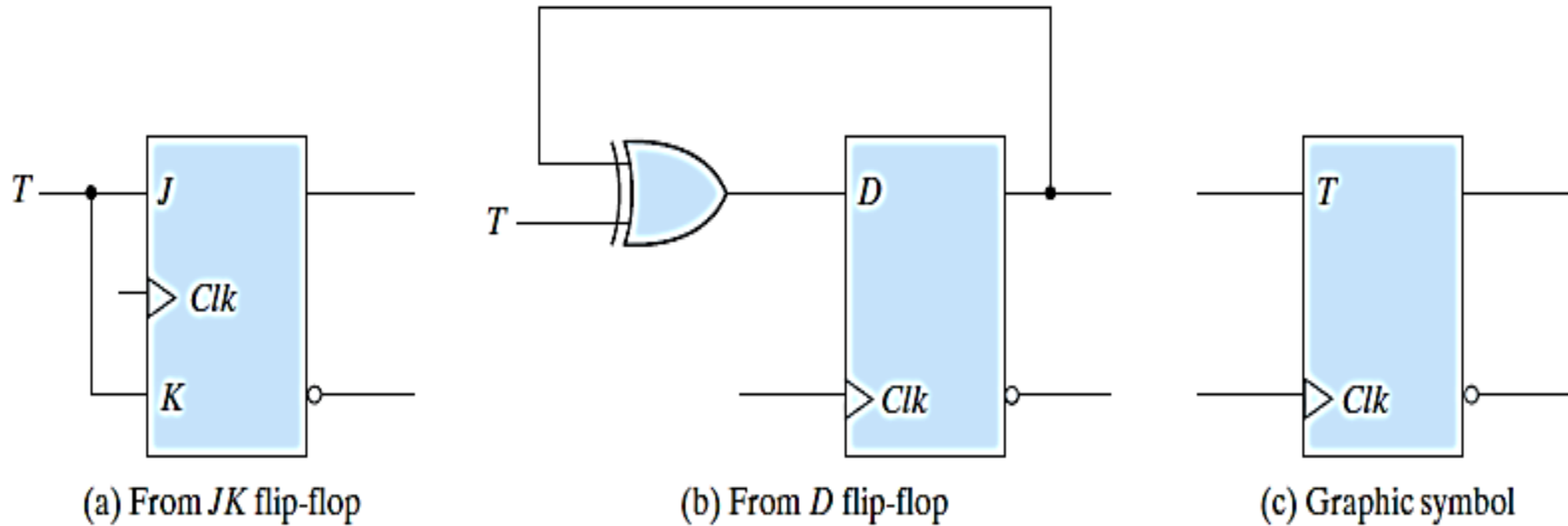


If $T = 0$ ($J = K = 0$), a clock edge does not change the output. When $T = 1$ ($J = K = 1$), a clock edge complements the output

T Flip-Flop


T	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Master-Slave JK Flip Flop

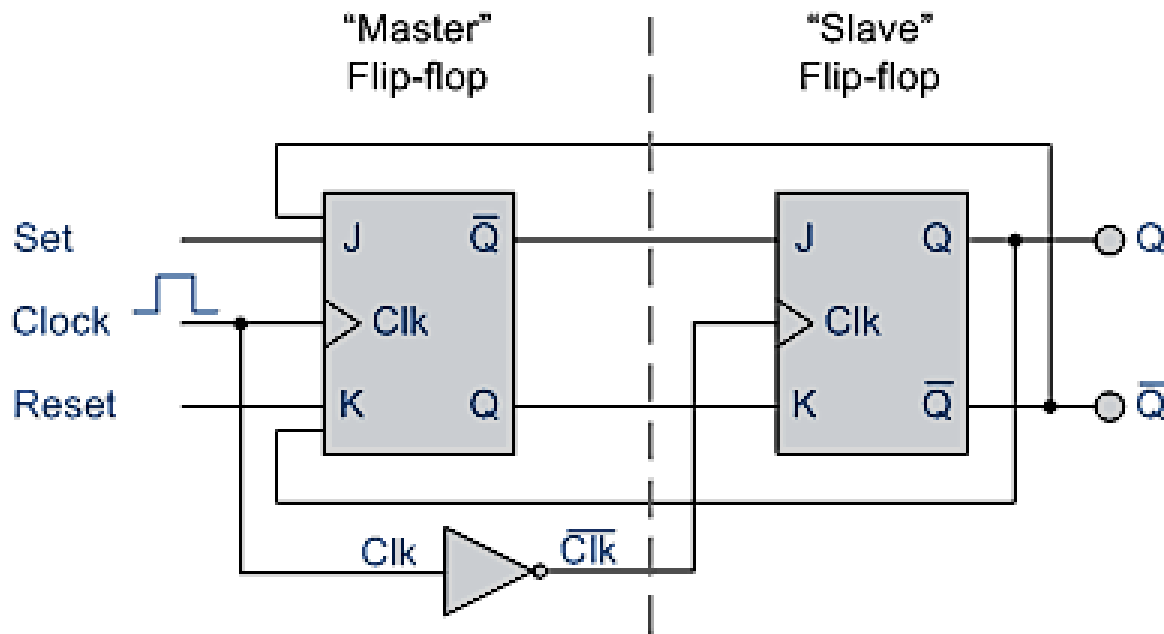
Master-slave flip flop is designed using two separate flip flops. Out of these, one acts as the master and the other as a slave.



- From the above figure you can see that both the J-K flip flops are presented in a series connection. The output of the master J-K flip flop is fed to the input of the slave J-K flip flop. The output of the slave J-K flip flop is given as a feedback to the input of the master J-K flip flop. The clock pulse [Clk] is given to the master J-K flip flop and it is sent through a NOT Gate and thus inverted before passing it to the slave J-K flip flop.
- Here the master flip-flop is triggered by the external clock pulse train while the slave is activated at its inversion i.e. if the master is positive edge-triggered, then the slave is negative-edge triggered and vice-versa.

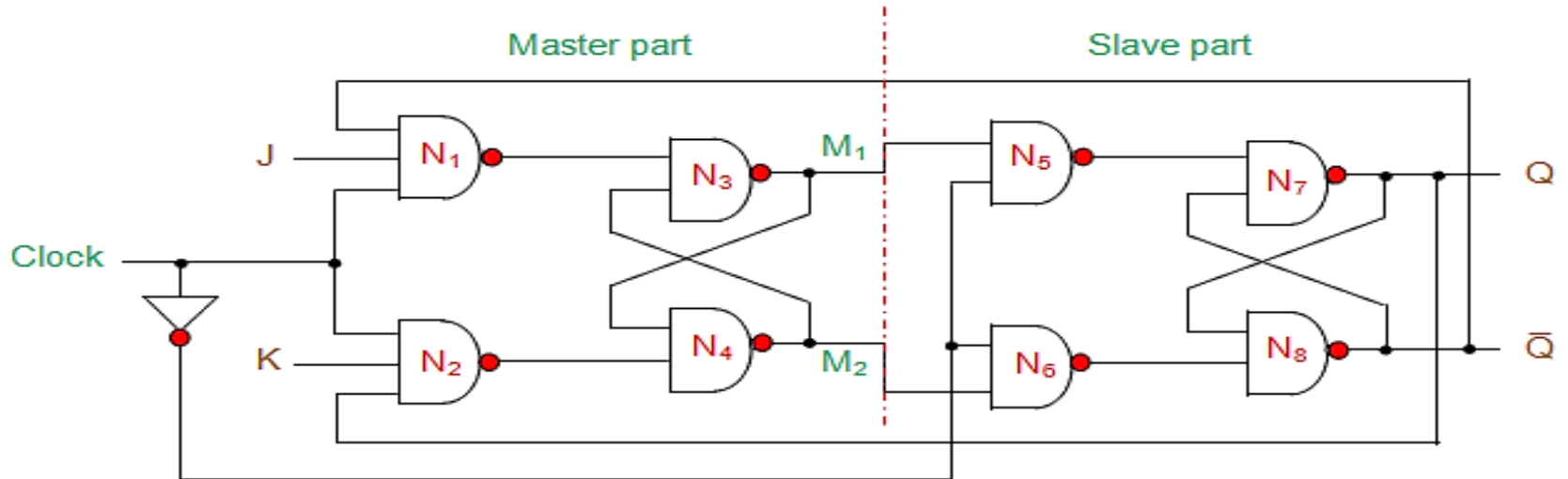

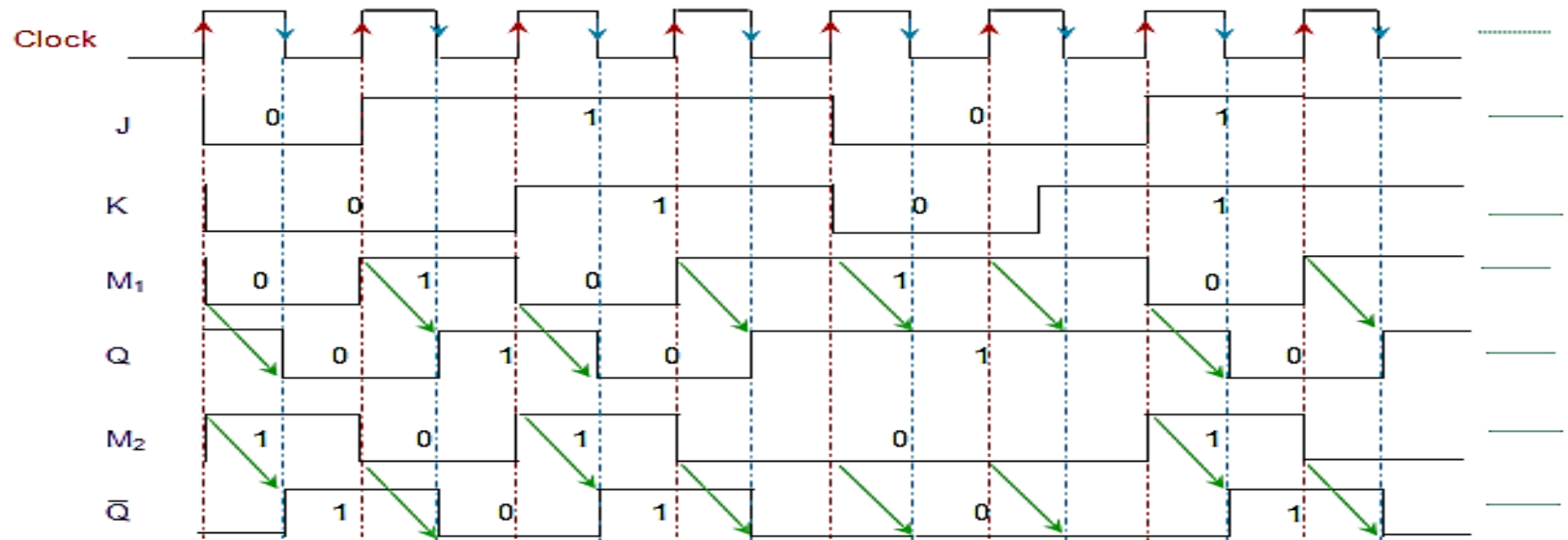Master-Slave JK flip-flop realized using NAND gates and an inverter



Timing diagram for master-slave JK flip-flop