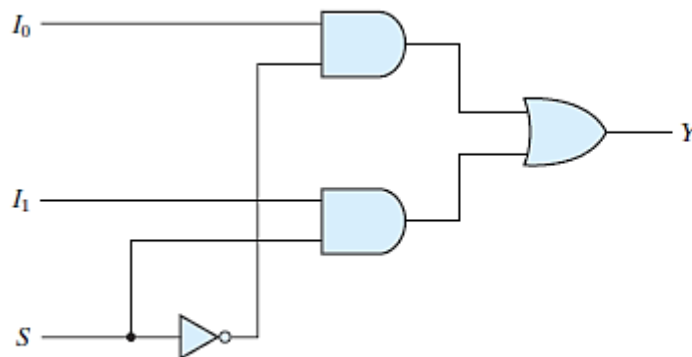



Exp. No.8 Multiplexer (MUX) and Demultiplexer(DEMUX)

Multiplexer

- A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line.
- The selection of a particular input line is controlled by a set of selection lines. Normally, there are 2^n input lines and n selection lines whose bit combinations determine which input is selected.



(a) Logic diagram

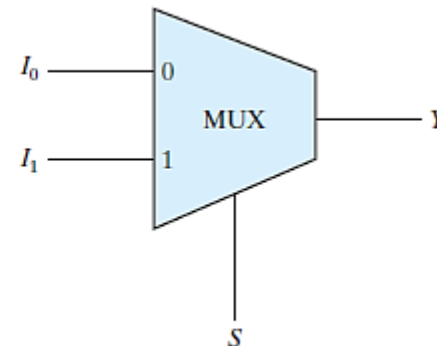


(b) Block diagram

Two-to-one-line multiplexer

- $Y = I_0 \cdot \bar{S} + I_1 \cdot S$

- When the select line, $S=0$, the output of the lower AND gate is zero, but the upper AND gate is I_0 . Thus, the output generated by the OR gate is equal to I_0 .
- Similarly, when $S=1$, the output of the upper AND gate is zero, but the output of lower AND gate is I_1 . Therefore, the output of the OR gate is I_1 .
- Thus, the Boolean expression for the output becomes I_0 when $S=0$ and output is I_1 when $S=1$.

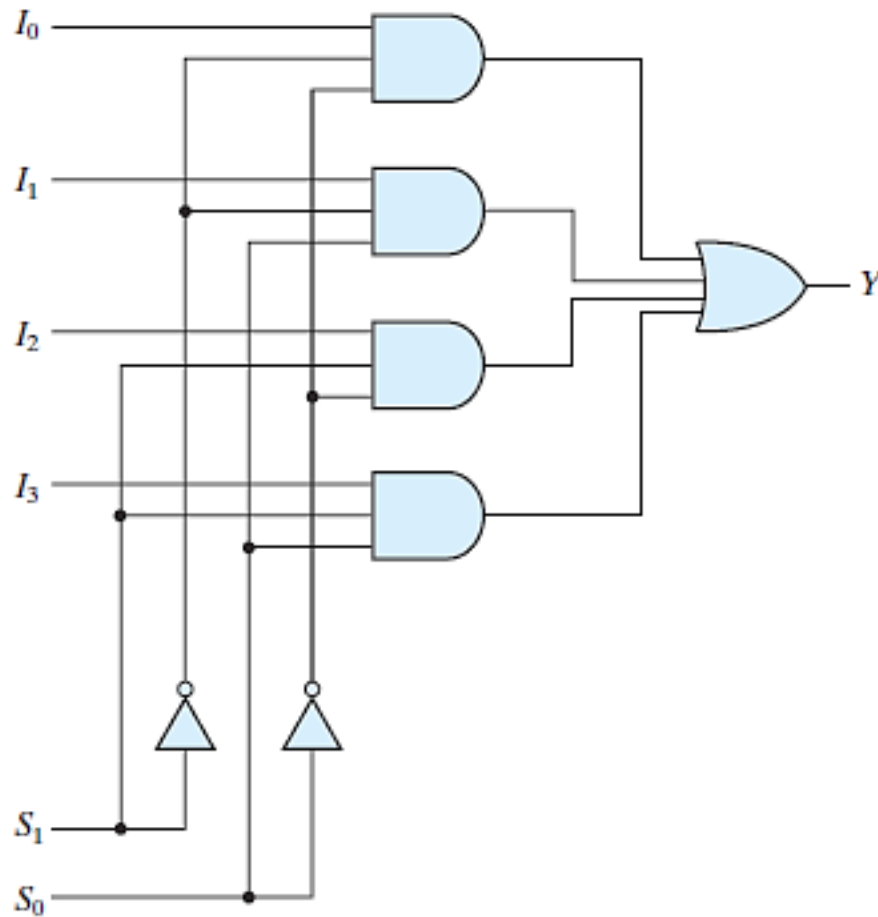

(a) Logic diagram


H.W Find the equation of Y of 4-to-1 line MUX

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


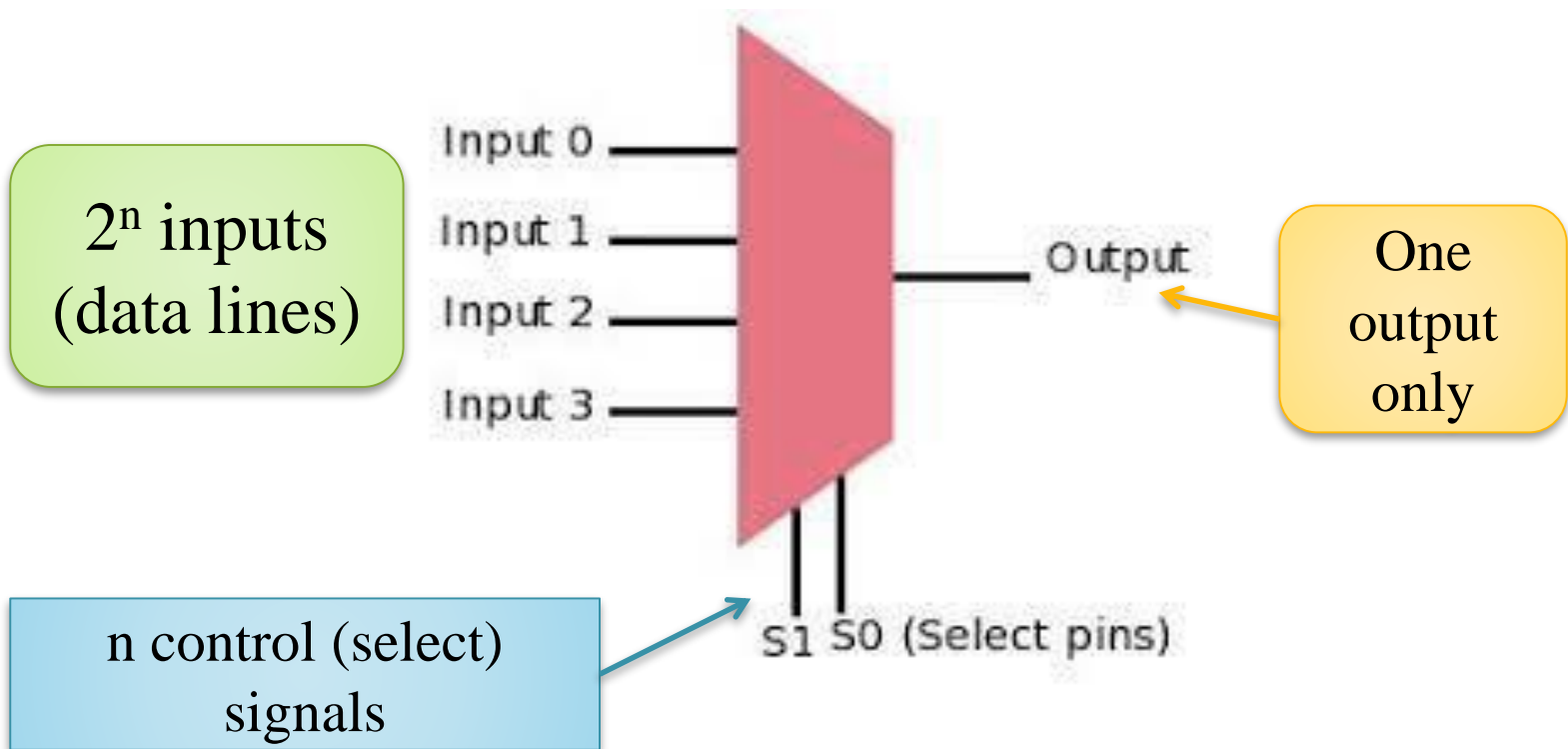
(b) Function table

Four-to-one-line multiplexer

- The size of a multiplexer is specified by the number 2^n of its data input lines and the single output line. The n selection lines are implied from the 2^n data lines.




4-to-1 Multiplexer Waveforms

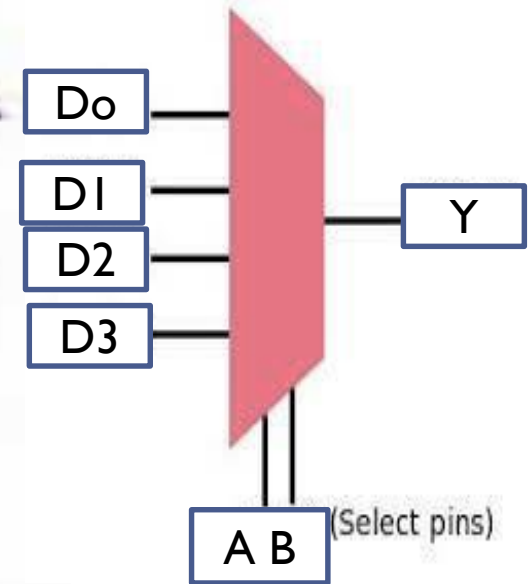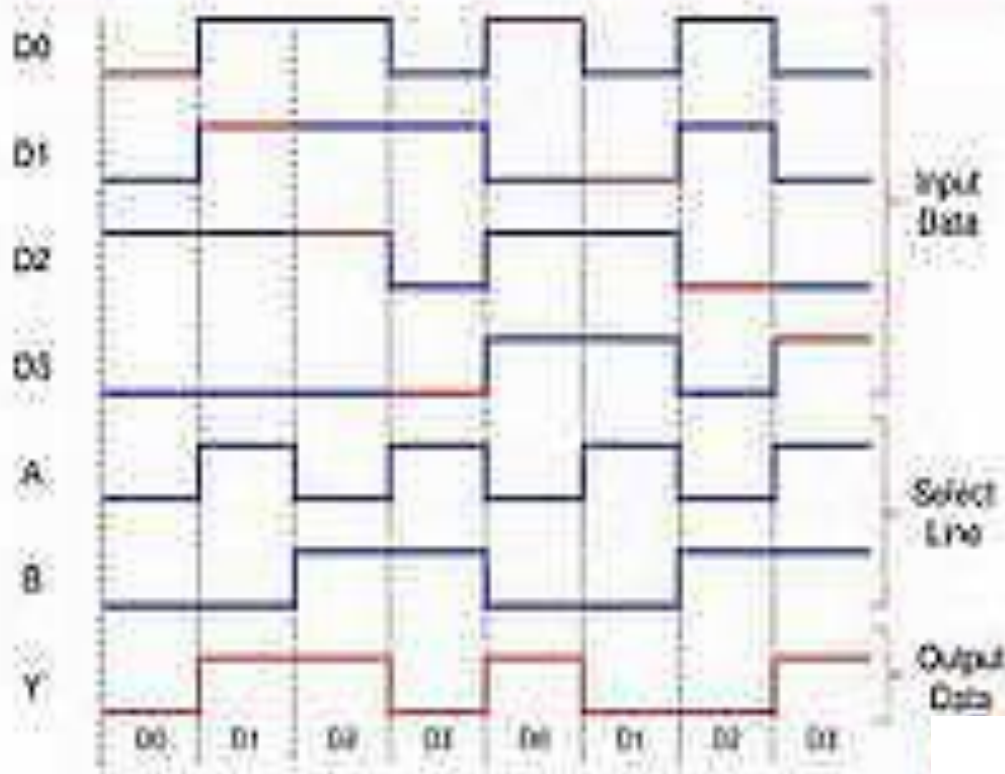


A	B	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3


8-to-1 line MUX

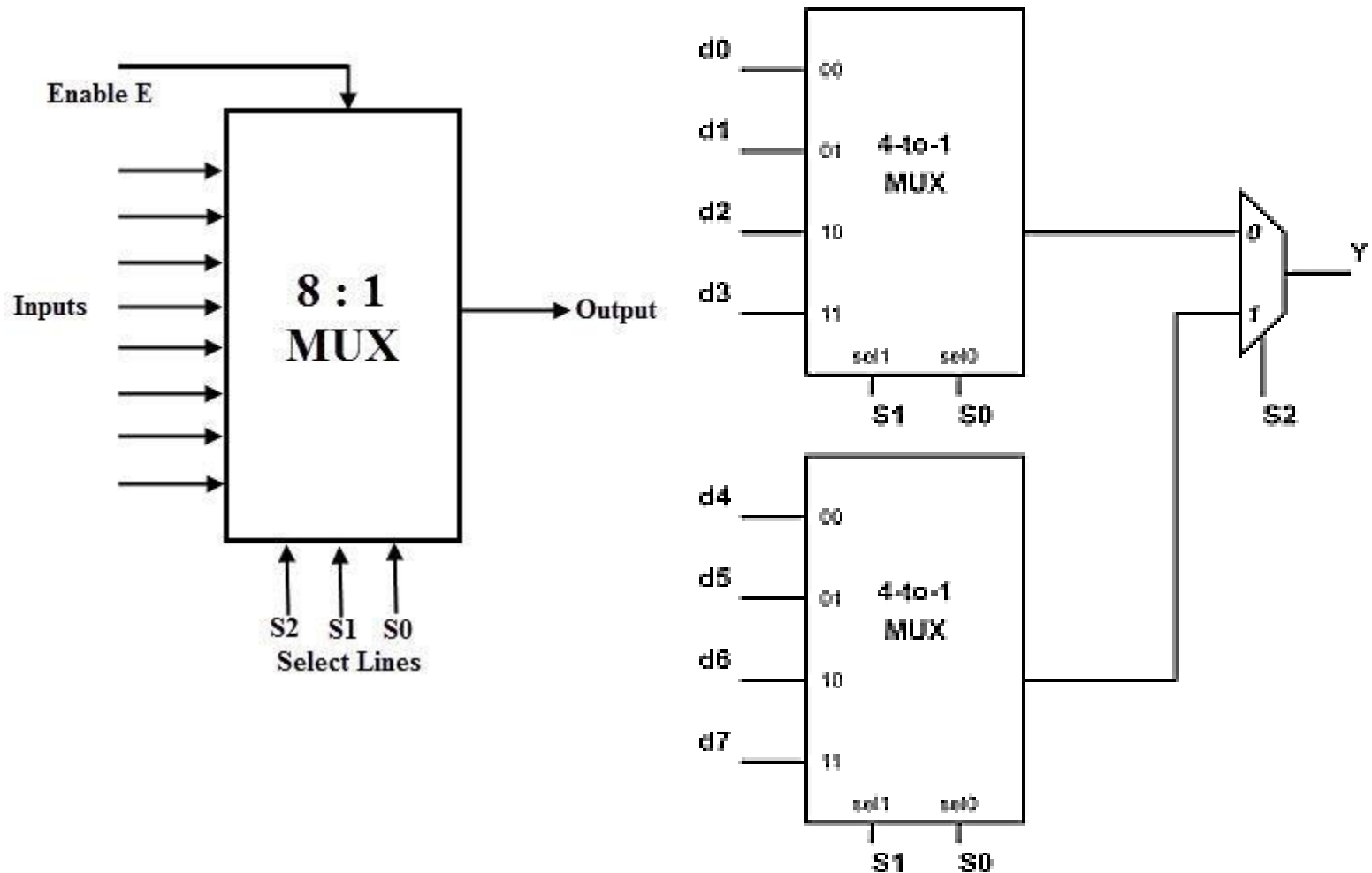

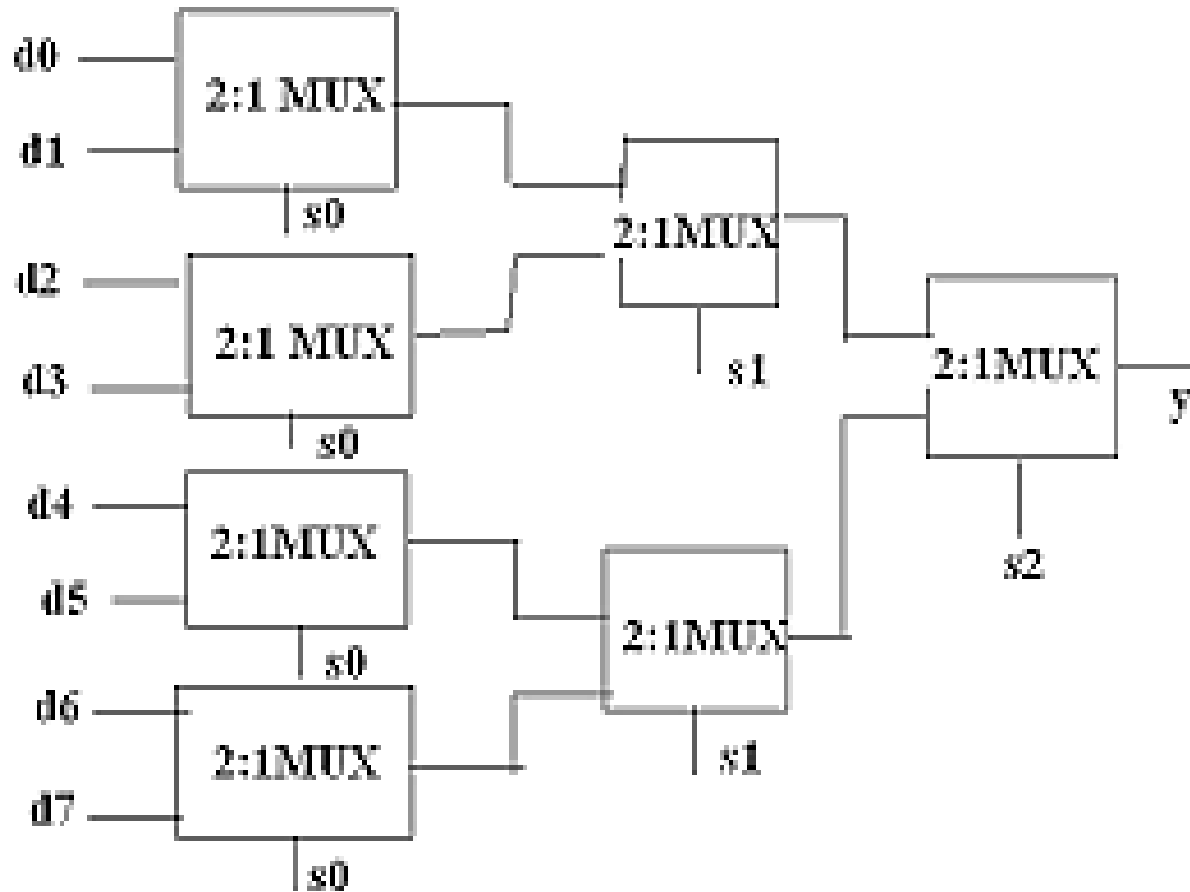
8-to-1 line MUX using 4-to-1 MUX and 2-to-1 MUX



8-to-1 line MUX using 2-to-1 MUX

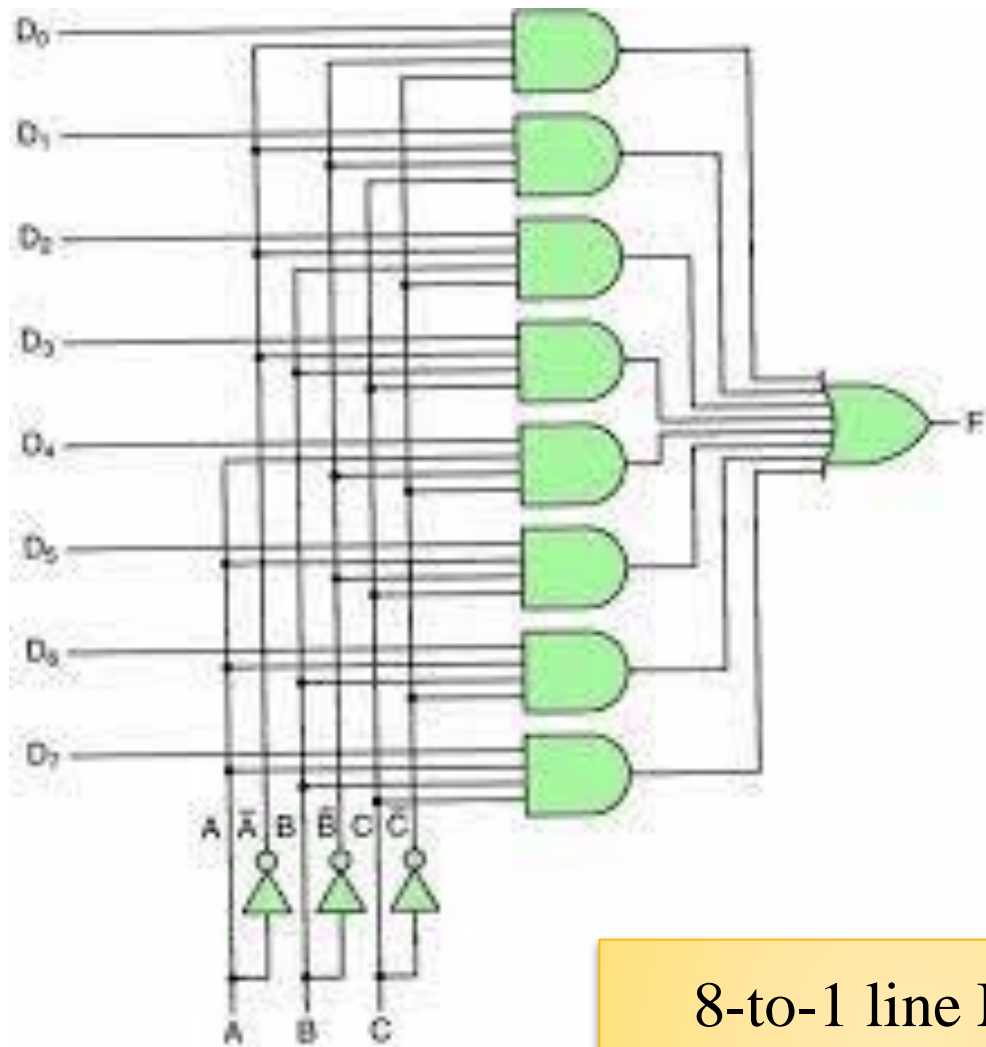


8-to-1 line MUX
using logic gates

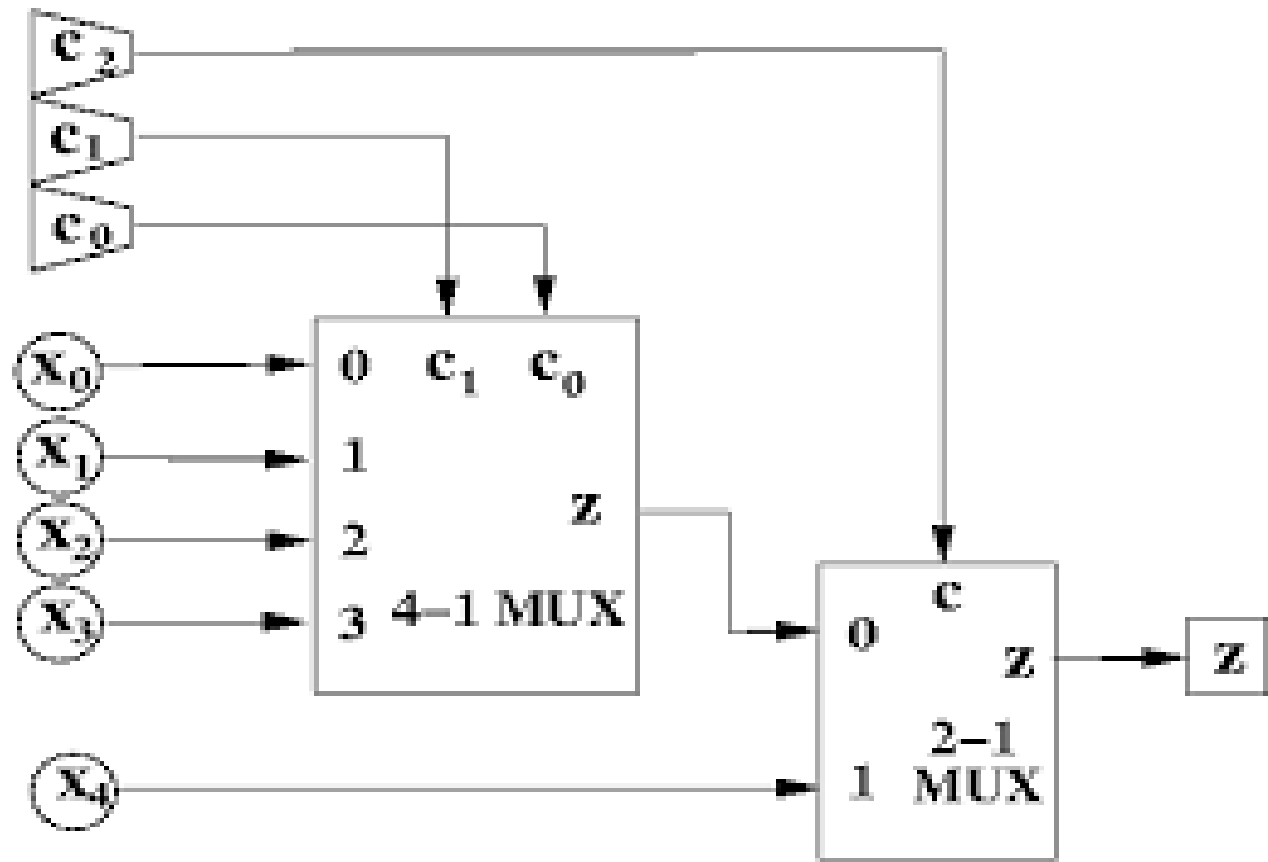

5-to-1 line MUX using 4-to-1 MUX and 2-to-1 MUX


Demultiplexer

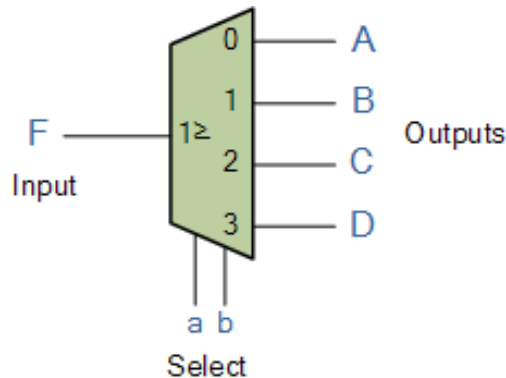- ❖ The demultiplexer takes one single input data line and then switches it to any one of a number of individual output lines one at a time.
- ❖ The demultiplexer converts a serial data signal at the input to a parallel data at its output lines.



a	b	o/p
0	0	A
0	1	B
1	0	C
1	1	D

1 – to- 4 line Demultiplexer

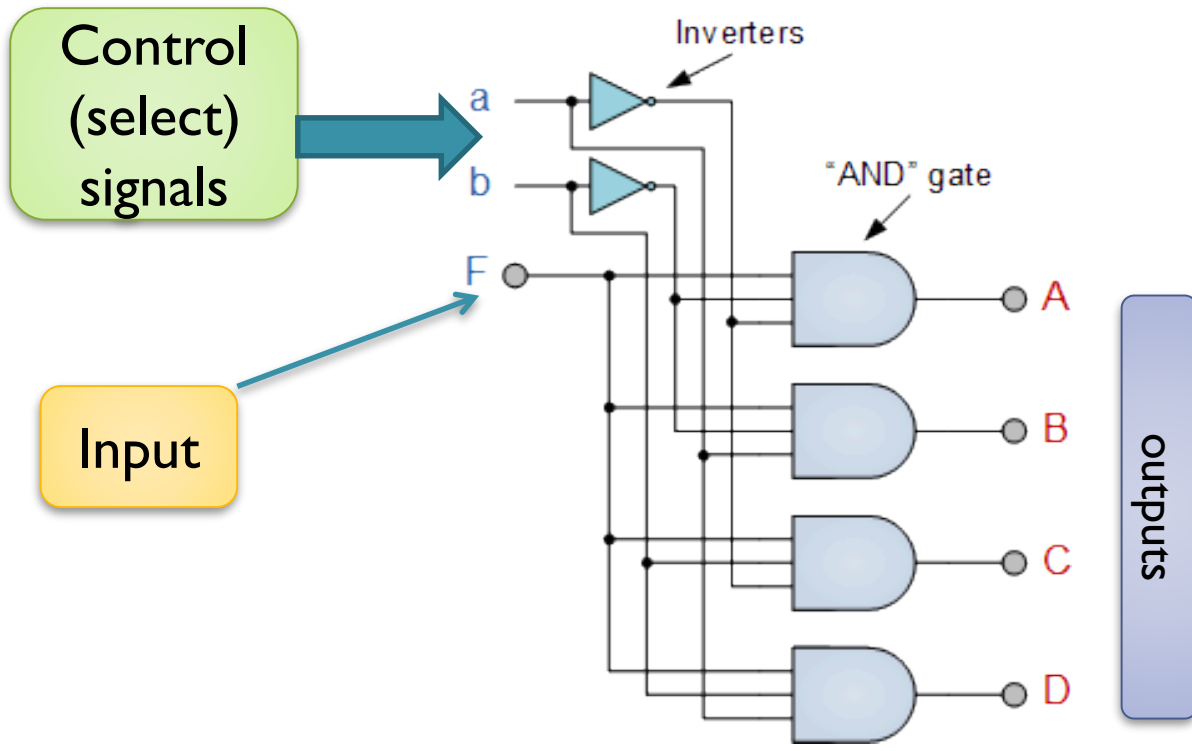

1 – to- 4 line Demultiplexer logic diagram

1-to-4 De-Multiplexer Waveforms

