

Advance Electricity Lab

Exp. (1):

- 1) Define Resonance?
- 2) Define Quality Factor?
- 3) Define Band Width?
- 4) Prove $f_0 = \frac{1}{2\pi\sqrt{LC}}$

Exp. (1):

- 1) What is Effective Current?
- 2) Define Capacitive Reactance(X_C)?
- 3) Define Inductive Reactance(X_L)?
- 4) How series resonance occurs?

Exp. (1):

- 1) Sketch the electrical circuit for series resonance?
- 2) What do you mean by RLC circuit?
- 3) Is $V_C = V_L$ in series resonance circuit?
- 4) Is the circuit current reaching its maximum (I_{Max}) in series resonance circuit?

Exp. (1):

- 1) Is $Z = R$ reach its minimum at resonance, in series resonance circuit?
- 2) Mention six characteristics of series resonance circuit?
- 3) How Quality Factor changes when the resistor is increased?
- 4) How Band Width changes when the resistor is increased?

Exp. (1):

- 1) What is the relation between Quality factor and Band width?
- 2) Is $X_L > X_C$ above the resonance, in series resonance circuit?
- 3) Draw the circuit diagram (inductance part)?
- 4) Is $X_L > X_C$ below the resonance, in series resonance circuit?

Exp. (1):

- 1) Mention six characteristics of series resonance circuit?
- 2) Sketch the electrical circuit for series resonance?
- 3) Define Quality Factor?
- 4) Define Capacitive Reactance(X_C)?

Exp. (2):

- 1) Define High Pass Filter Frequency?
- 2) Define Low Pass Filter Frequency?
- 3) Define Band Pass Filter Frequency?
- 4) Define Band Stop Pass Filter Frequency?

Exp. (2):

- 1) Define Cut Off frequency?
- 2) Write an equation for Cut Off frequency in Low Pass Filter Frequency?
- 3) Write an equation for Cut Off frequency in High Pass Filter Frequency?
- 4) What is the unit of Cut Off frequency?

Exp. (2):

- 1) Prove that $f_c = \frac{R}{2\pi L}$?
- 2) Prove that $f_c = \frac{1}{2\pi RC}$?
- 3) Compare High Pass Filter Frequency and Low Pass Filter Frequency?
- 4) Compare Band Pass Filter Frequency and Band Stop Pass Filter Frequency?

Exp. (2):

- 1) Sketch the electrical circuit for High Pass Filter Frequency?
- 2) Sketch the electrical circuit for Low Pass Filter Frequency?
- 3) Define Cut Off frequency?
- 4) Write an equation for Cut Off frequency in Low Pass Filter Frequency?

Exp. (2):

- 1) Define Low Pass Filter Frequency?
- 2) Define Band Pass Filter Frequency?
- 3) Sketch the electrical circuit for High Pass Filter Frequency?
- 4) Define Cut Off frequency?

Exp. (2):

- 1) Compare High Pass Filter Frequency and Low Pass Filter Frequency?
- 2) Compare Band Pass Filter Frequency and Band Stop Pass Filter Frequency?
- 3) What is the unit of Cut Off frequency?
- 4) Prove that $f_c = \frac{R}{2\pi L}$?

Exp. (3):

- 1) Define inductance?
- 2) Define Capacitance?
- 3) On what factor does the inductance of inductor depend?
- 4) On what factor does the capacitance of a capacitor depend?

Exp. (3):

- 1) Define phasor diagram?
- 2) Write an equation for r in Capacitance part?
- 3) What is phase angle?
- 4) Does current lag or lead in a purely resistive circuit?

Exp. (3):

- 1) Does current lag or lead in a purely inductive circuit?
- 2) Does current lag or lead in a purely capacitive circuit?
- 3) Sketch the electrical circuit for Investigation of Capacitance and Inductance in A.C Circuit.
- 4) Define inductance?

Exp. (3):

- 1) On what factor does the inductance of inductor depend?
- 2) Define Capacitance?
- 3) Write an equation for r in Capacitance part?
- 4) What is phase angle?

Exp. (3):

- 1) Does current lag or lead in a purely resistive circuit?
- 2) On what factor does the inductance of inductor depend?
- 3) Define inductance?
- 4) Define Capacitance?

Exp. (3):

- 1) What is phasor diagram?
- 2) Write an equation for r in Capacitance part?
- 3) What is phase angle?
- 4) Sketch the electrical circuit for Investigation of Capacitance and Inductance in A.C Circuit.

Exp. (4):

- 1) Define Resistance?
- 2) Define Phase Shift?
- 3) Define Power?
- 4) How many type of electrical power do we have? Count them?

Exp. (4):

- 1) Define Reactive Power?
- 2) Define Apparent Power?
- 3) State Real Power Equation in your experiment?
- 4) State Apparent Power Equation in your experiment?

Exp. (4):

- 1) State Reactive Power Equation in your experiment?
- 2) Does current lag or lead in a purely resistive circuit?
- 3) Define Resistance?
- 4) Define Phase Shift?

Exp. (4):

- 1) What are the differences between Reactive Power and Apparent Power?
- 2) What are the differences between Real Power and Apparent Power?
- 3) State Reactive Power Equation in your experiment?
- 4) Does current lag or lead in a purely resistive circuit?

Exp. (4):

- 1) Define Reactive Power?
- 2) Define Apparent Power?
- 3) Define Real (true, active) Power?
- 4) Does current lag or lead in a purely capacitive circuit?

Exp. (4):

- 1) What are the differences between Reactive Power and Apparent Power?
- 2) Define Phase Shift?
- 3) Does current lag or lead in a purely capacitive circuit?
- 4) State Apparent Power Equation in your experiment?

Exp. (5):

- 1) Define Thevenin's theorem?
- 2) Why theoretical value and practical value of R_{Th} doesn't match with each other?
- 3) What is Resistance?
- 4) On what factor does the resistance of a resistor depend?

Exp. (5):

- 1) On what factor does the resistance of a resistor depend?
- 2) Write all steps that you apply to simplify a complex circuit by using Thevenin's theory?
- 3) How do you get V_{Th} practically? Write its steps?
- 4) Write an equation for I_L ?

Exp. (5):

- 1) Define Thevenin's theorem?
- 2) Write all steps that you apply to simplify a complex circuit by using Thevenin's theory?
- 3) Write an equation for I_L ?
- 4) Draw the circuit diagram?

Exp. (5):

- 1) How do you get V_{Th} practically? Write its steps?
- 2) Define Thevenin's theorem?
- 3) Define Resistance?
- 4) On what factor does the resistance of a resistor depend?

Exp. (5):

- 1) Write all steps that you apply to simplify a complex circuit by using Thevenin's theory?
- 2) Draw the circuit diagram?
- 3) On what factor does the resistance of a resistor depend?
- 4) Write an equation for I_L ?

Exp. (5):

- 1) Define Thevenin's theorem?
- 2) Draw the circuit diagram?
- 3) Write an equation for I_L ?
- 4) Define Resistance?

Exp. (6):

- 1) Define electrical damping?
- 2) How many types of electrical damping do we have?
- 3) What is the role of the capacitor in this experiment?
- 4) What is the role of the inductor (coil) in this experiment?

Exp. (6):

- 1) Define electrical resonance?
- 2) Write an equation for damping factor (b)?
- 3) Write an equation for error ratio ?
- 4) Define time period?

Exp. (6):

- 1) What is the role of the capacitor in this experiment?
- 2) Write an equation for damping factor (b)?
- 3) How many types of electrical damping do we have?
- 4) Draw the circuit diagram?

Exp. (6):

- 1) Draw the circuit diagram?
- 2) How many types of electrical damping do we have?
- 3) What is the role of the capacitor in this experiment?
- 4) Write an equation for error ratio ?

Exp. (6):

- 1) What is electrical damping?
- 2) How many types of electrical damping do we have?
- 3) Draw the circuit diagram?
- 4) Write an equation for damping factor (b)?

Exp. (6):

- 1) What is the role of the capacitor in this experiment?
- 2) Draw the circuit diagram?
- 3) How many types of electrical damping do we have?
- 4) Write an equation for error ratio ?

Exp. (7):

- 1) Why is magnetic field at the center of solenoid coil higher than the magnetic field on its sides?
- 2) Define Biot-Savart Law?
- 3) What is the unit of magnetic field?
- 4) Write an equation for magnetic field?

Exp. (7):

- 1) Why we get some fixed value of magnetic field strength at the center of solenoid coil?
- 2) Define permeability?
- 3) What is the unit of permeability?
- 4) Define Biot-Savart Law?

Exp. (7):

- 1) If the circuit current is increased what will happen to the magnetic field?
- 2) What is the unit of magnetic field?
- 3) Write an equation for magnetic field?
- 4) Why is magnetic field at the center of solenoid coil higher than the magnetic field on its sides?

Exp. (7):

- 1) Define Biot-Savart Law?
- 2) Why we get some fixed value of magnetic field strength at the center of solenoid coil?
- 3) Draw the circuit diagram?
- 4) Write an equation for magnetic field?

Exp. (7):

- 1) Define Biot-Savart Law?
- 2) Why is magnetic field at the center of solenoid coil higher than the magnetic field on its sides?
- 3) Define Magnetic field?
- 4) What is the unit of permeability?

Exp. (7):

- 1) Draw the circuit diagram?
- 2) Write an equation for magnetic field?
- 3) Define Biot-Savart Law?
- 4) Define Magnetic field?

