
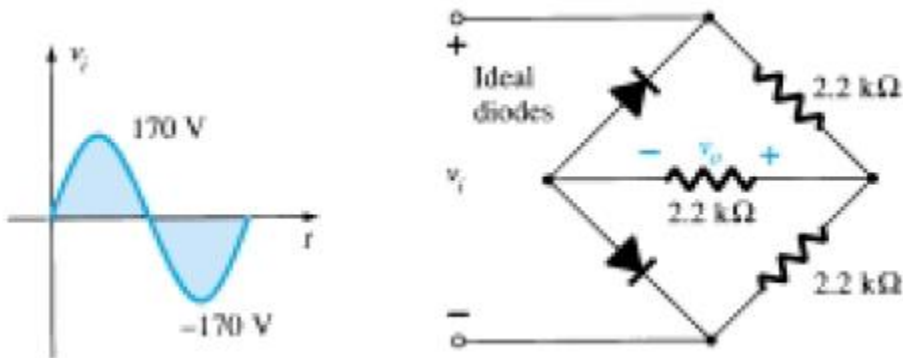


## Questions Bank of Circuit Analysis



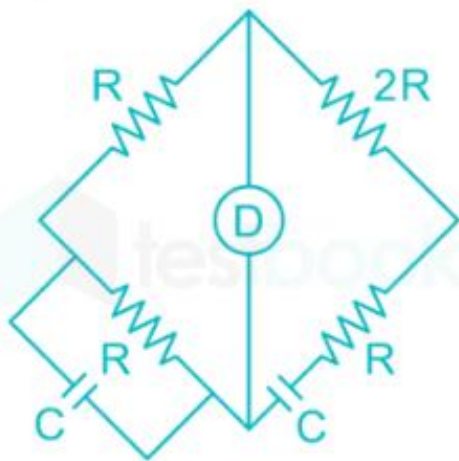
**Q1.** Sketch  $v_o$  for the network of Fig. and determine the dc voltage available.




**Q2.** In the AC bridge shown ( $R=10^3 \Omega$  and  $C=10^{-7} F$ ) if the bridge is balanced at a frequency  $f_0$ , then find  $f_0$ .



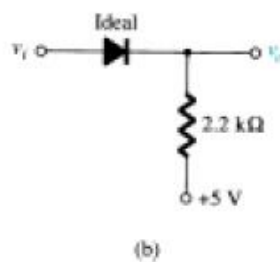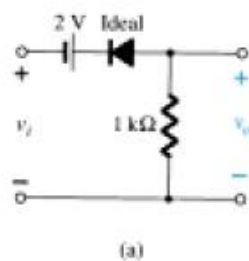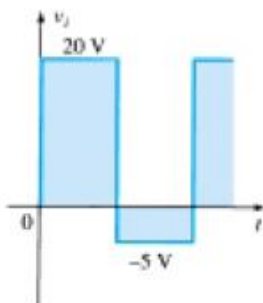**Q3.** Determine  $v_o$  for each network for the input shown.



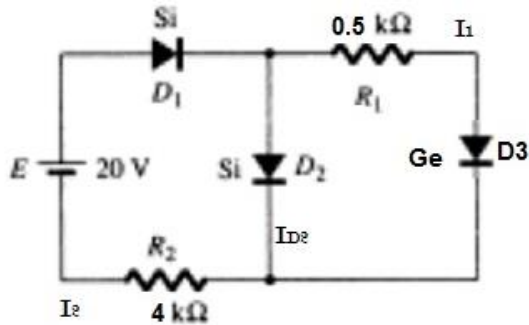**Q4.** Determine the currents  $I_1$ ,  $I_2$ , and  $I_{D2}$  for the network of the given circuit.



**Q5.** The arms of the four arm bridge (abcd), supplied with sinusoidal voltage, have the following values:

Arm (ab) : A resistance of ( $R_1=200 \Omega$ ) in parallel with a capacitance ( $C_1= 1 \mu\text{F}$ )

Arm (bc): Pure resistance ( $R_3=400 \Omega$ )

Arm (cd): Pure resistance ( $R_4=1000 \Omega$ )


Arm (da) : A resistance ( $R_2$ ) in series with a capacitor ( $C_2= 2 \mu\text{F}$ )

Determine the value of  $R_2$  and the frequency at which the bridge will balance .

The detector is connected between b and d, and supply voltage between a and c

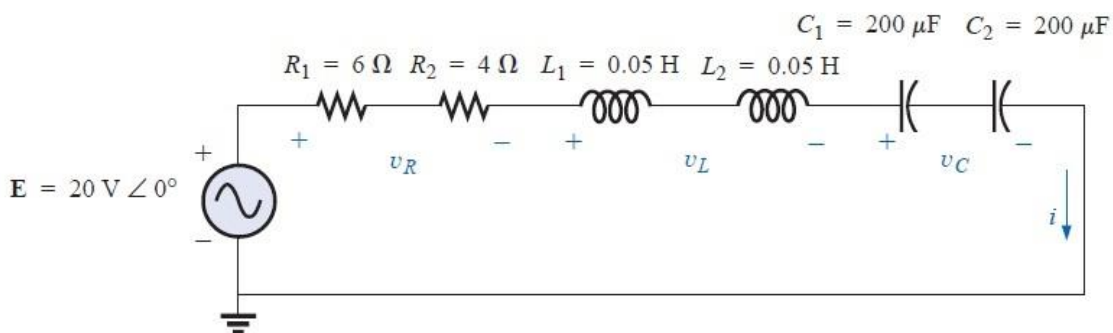**Q6.** For the circuit ( $277 \text{ rad/s}$ ) of Fig.


- Calculate  $\mathbf{I}$ ,  $\mathbf{V}_R$ ,  $\mathbf{V}_L$ , and  $\mathbf{V}_C$  in phasor form.
- Calculate the total power factor.
- Calculate the average power delivered to the circuit.
- Draw the phasor diagram.
- Obtain the phasor sum of  $\mathbf{V}_L$ , and  $\mathbf{V}_C$ .



**Q7.** Answer the following questions:

- 1- If the applied voltage lags the current in a series RLC circuit, is the frequency above or below resonance?
- 2- Draw the  $I_{\text{rms}}$  as function of  $\omega$  for RL, RC and Resistor only circuit.
- 3- At low frequencies the capacitive reactance considered as:  
a) Short circuit      b) open circuit      c) none of these
- 4- In the resonance circuit the larger resistance, the resonant current is -----.  
a) Smaller      b) larger      c) not affected
- 5- In an RLC circuit with an ac power source, the impedance is a minimum at -----  
--:  
a) Low frequency      b) high frequency      c) resonance frequency

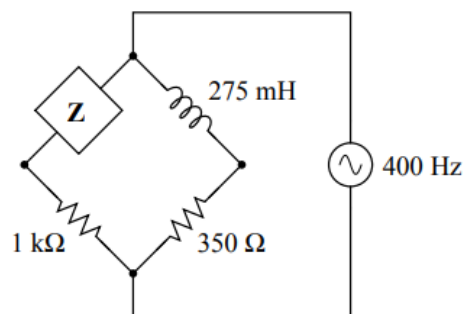**Q8.** Calculate the value of C or L in the unknown Z arm that is necessary to balance this AC bridge.




**Q9. Choose the correct answer:** **(12 marks)**

- 1- When the semiconductor has equal number of free electrons and holes, it is called.....  
(a- Doped semiconductor      b- intrinsic semiconductor  
c- extrinsic semiconductor      d- P-type semiconductor)
- 2- N-type semiconductor can be produced by introducing ----- into pure silicon crystal.  
(a- Arsenic      b- Gallium      c- Boron      d- indium )
- 3- The current and voltage in a ----- are not in phase, the voltage lags by  $90^\circ$ .  
(a- inductor      b- Resistor      c- Capacitor      d- Diode )
- 4- Half wave rectifier is an example of -----.  
(a- Clipper      b- amplifier      c- clamper      d- both a and c)
- 5- In the p-n junction of semiconductor you can see only ----- in the depletion region.  
(a- holes      b- free electrons      c- mobile charge carrier      d- ions )


- 6- If the applied voltage is in phase with the current in a series RLC circuit, then the frequency is-----.
- (a- below resonance    b- above resonance    c- zero    d- at resonance )
- 7- The forward current in the semiconductor diode is due to -----.
- (a- Resistance    b- majority carrier    c- minority carrier    d- capacitance at junction)
- 8- When the AC source, capacitor and inductor all are connected in parallel under high frequency limit, which of the following statement is true ?
- a- Inductor works like short circuit and capacitor works like open circuit.  
 b- Inductor works like open circuit and capacitor works like short circuit.  
 c- Both are work like open circuit.  
 d- Both are work like short circuit

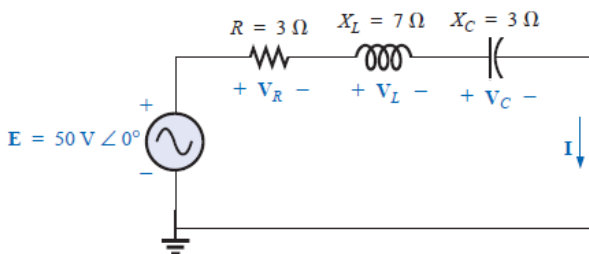**Q10.** For the given circuit, find  $V_R$ ,  $V_C$ ,  $V_L$  and  $I$  in vector notation and then draw the phasor diagram.



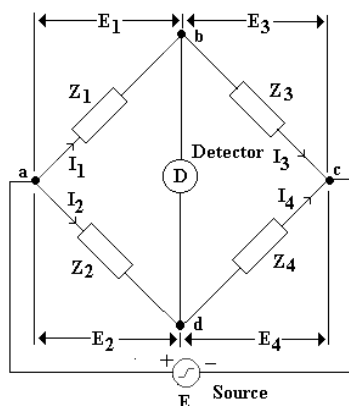**Q11.** An AC bridge is shown in figure, working at 1000 Hz. Arm (ab) is  $0.2 \mu\text{F}$  pure capacitance, arm (bc) is  $500 \Omega$  pure resistance, arm (cd) contains an unknown impedance and arm (da) has  $300 \Omega$  resistance in parallel with  $0.1 \mu\text{F}$  capacitor.


Find R and C or L constants of arm (cd) considering it as a series circuit.



**Q12.** For the given circuit determine:


a) Find  $\left(\frac{V_{2o}}{V_{1o}}\right)$ , the ratio of the maximum output voltage  $V_{2o}$  to the maximum input voltage  $V_{1o}$ .

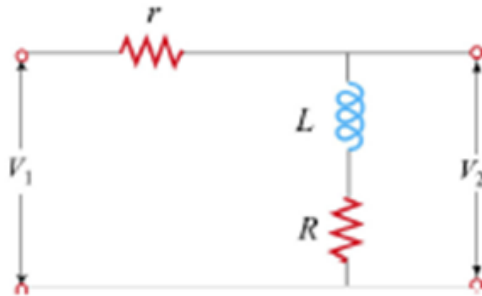b) Suppose  $r = 15 \Omega$ ,  $R = 10 \Omega$  and  $L = 250 \text{ mH}$ . Find the frequency at which  $\frac{V_{2o}}{V_{1o}} = \frac{1}{2}$





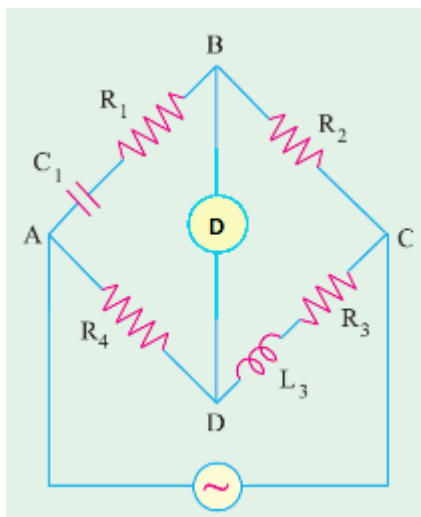**Q13.** For the given Hay's bridge at balance show that:

$$L_3 = \frac{C_1 R_2 R_4}{(1 + \omega^2 C_1^2 R_1^2)} \quad \text{and} \quad R_3 = \frac{\omega^2 C_1^2 R_1 R_2 R_4}{(1 + \omega^2 C_1^2 R_1^2)}$$



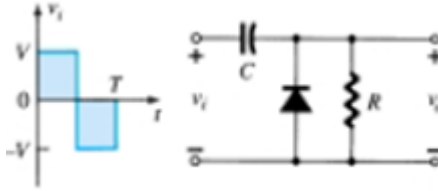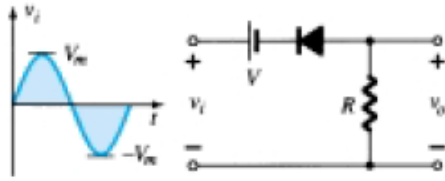**Q14.** Write the output wave form for the following circuits.



**Q15.** Use Thevenin's theorem to find the Voltage across the resistor  $R_2$  in the circuit below.

