

Salahaddin University-Erbil

COLLEGE OF ENGINEERING <<>>Electrical Eng. Department
2nd SEMESTER

«FINAL TERM EXAMINATIONS» First Attempted

TIME ALLOWED <<2 Hours>> Date << 6.5.2024>>

Lina N. Tofiq


Subject<<Analogue IC Design>>



QUESTION NO.1

[30 marks]

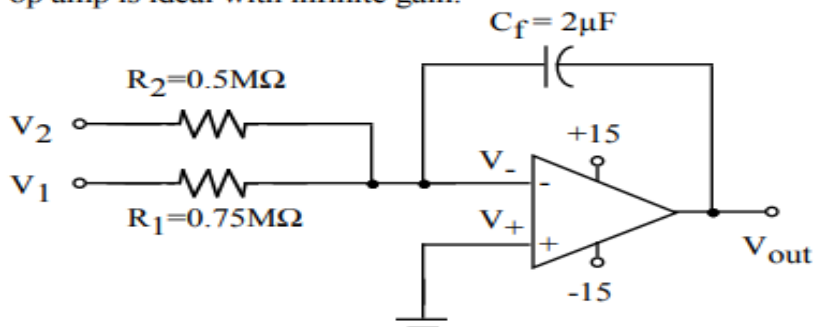
14. For the circuit shown below, $V_1 = 10\sin(200t)$ and $V_2 = 15\sin(200t)$. What is V_{out} ? The op amp is ideal with infinite gain.



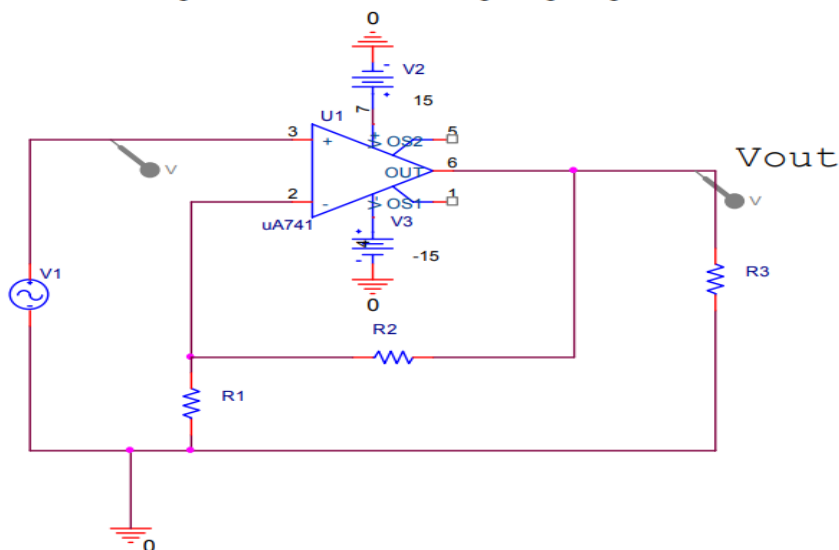QUESTION NO.2

[30 marks]

Below is a Capture schematic of an op-amp amplifier circuit that you should recognize.



1. What kind of amplifier is it?
2. What are the two "golden rules" of op-amp analysis?
3. Use these rules to derive an expression for V_{out} in terms of R_1 , R_2 and V_1 .
4. If $V_1=500\text{mV}$, $R_1=1\text{K}$ and $R_2=4\text{K}$, what is V_{out} ?
5. Find the current through the load resistor, R_3 , assuming the component values in part 4 and $R_3= 2\text{K}$ ohms.

QUESTION NO.3
[40 marks]

A.[20 marks]

«Find out the slew rate if an op-amp is necessary to amplify a signal through 4 volts of peak voltage at a 30kHz of frequency.»

B. [20 marks]

Design a phase-shift oscillator for a frequency of 800 Hz.The capacitors are to be 10 nF.

End