

University of Salahaddin – Erbil
College of Science
Physics Department



Laboratory Manual

Electricity and Magnetism

2nd Course

Assist. Lecturer. Safa Gh. Hameed



Safa.hameed@su.edu.krd

1Year – Physics
2021-2022




Experiment No. (1)

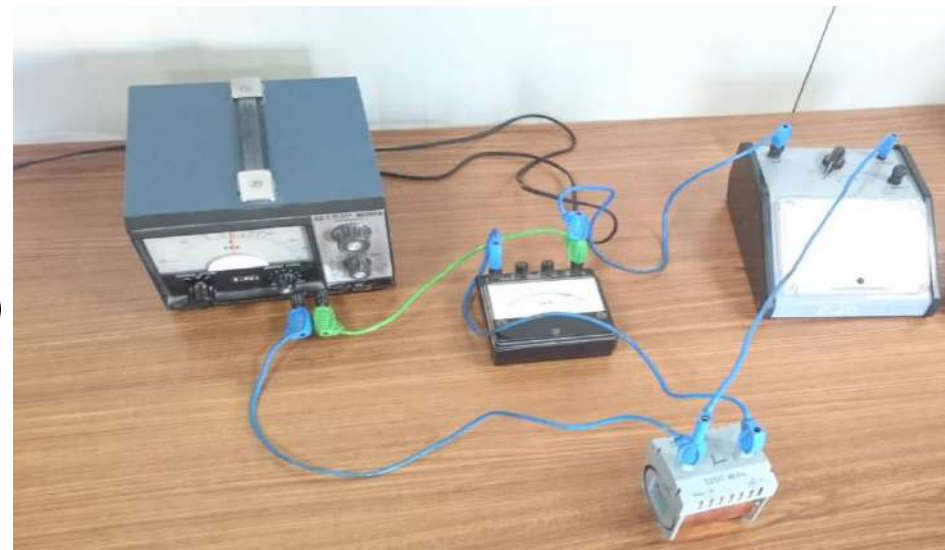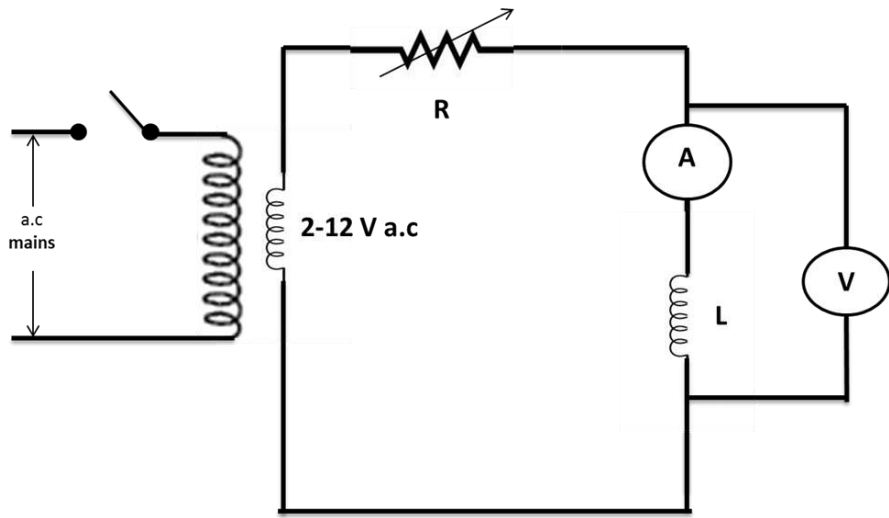To show that the behavior of an inductance in A.c. circuit is analogous to that of a resistor which obeys Ohm's law and hence to measure inductance



A.C Circuit

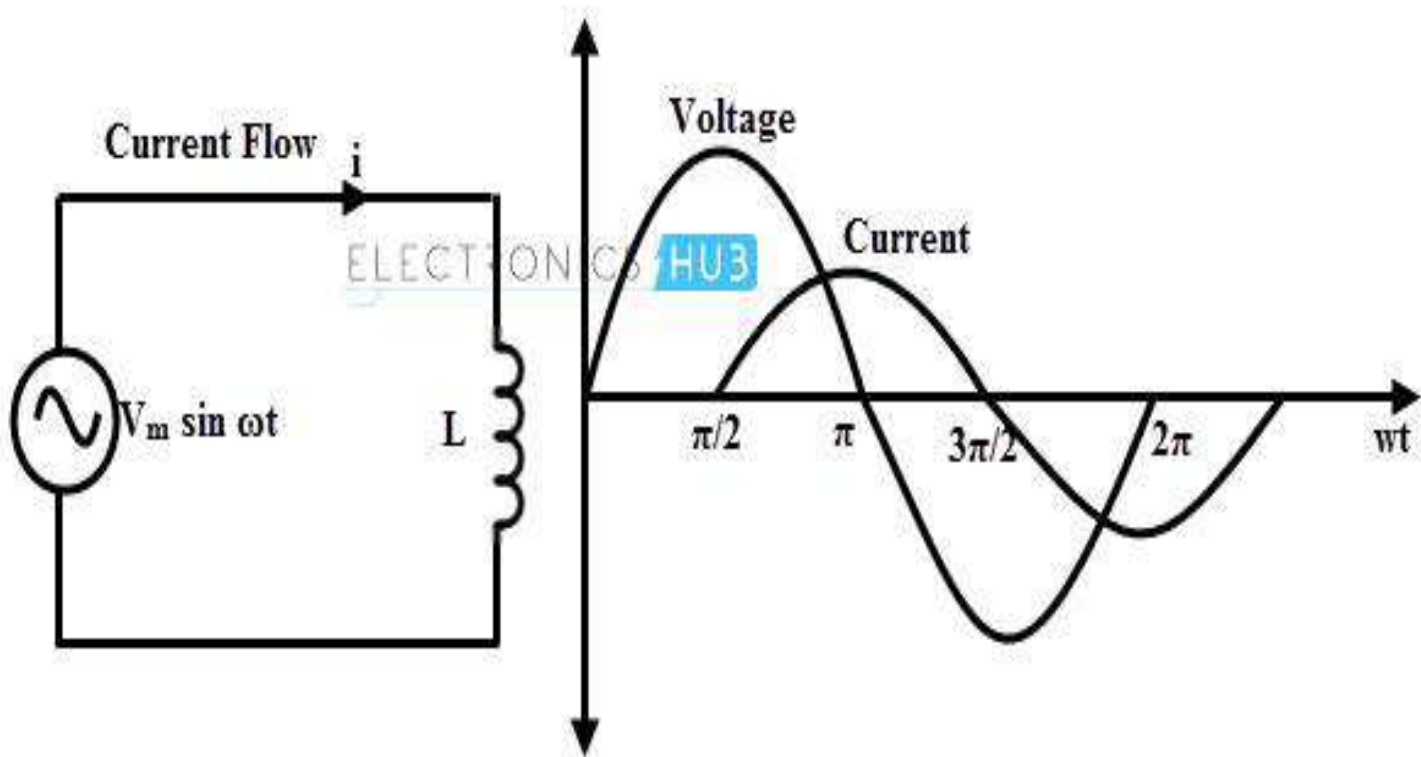

Experiment No. (1)

Data // part (1)

$$f = 1500 \text{ Hz}$$

$$L = 35 \text{ mH}$$

<i>V/ volt</i>	<i>I/A × 10⁻³</i>
<i>1</i>	
<i>1.5</i>	
<i>2</i>	
<i>2.5</i>	
<i>3</i>	
<i>3.5</i>	
<i>4</i>	
<i>4.5</i>	

Experiment No. (1)

Data // part (1)

$$L = 35 \text{ mH}$$


Theory value

$$X_L = 2\pi fL, \text{ where } f = 1500\text{Hz}$$

Graph & Calculation // part (1)/ Practically

$$\text{slop} = \frac{\Delta V}{\Delta I} = X_L$$

Practically
value

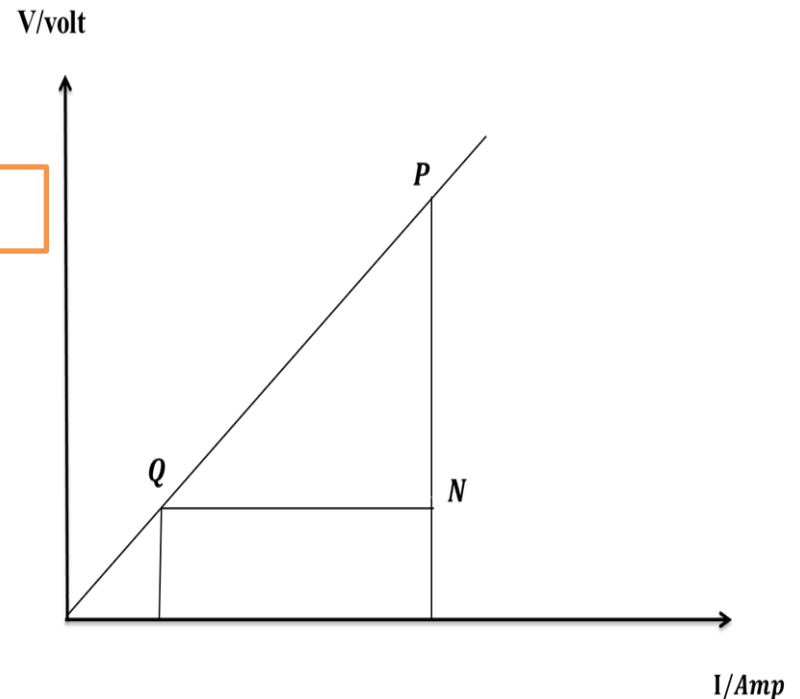

$$\text{Error ratio } (X_L) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

Experiment No. (1)

Data // part (2)

$$L = 35 \text{ mH}$$

<i>f</i> Hz	V/ volt	<i>I</i>/A × 10⁻³	$X_L = \frac{V}{I} / \Omega$
1000			
2000			
3000			
4000			
5000			
6000			
7000			
8000			
9000			

Experiment No. (1)

Data // part (2)

$L = 35 \text{ mH}$

Theory value


Graph & Calculation // part (2)/ Practically

$$\text{slop} = \frac{\Delta X_L}{\Delta f}$$

Practically value

$$X_L = 2\pi f L$$

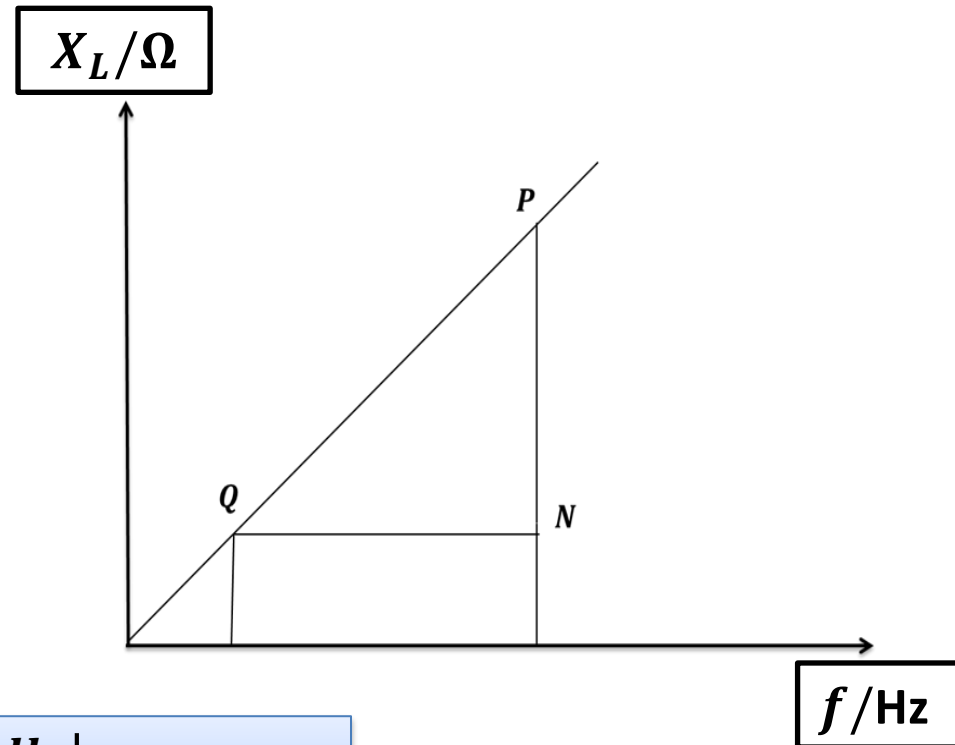
$$L = \frac{X_L}{2\pi f} = \frac{\text{slop}}{2\pi}$$










$$\text{Error ratio (L)} = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

Experiment No. (2)

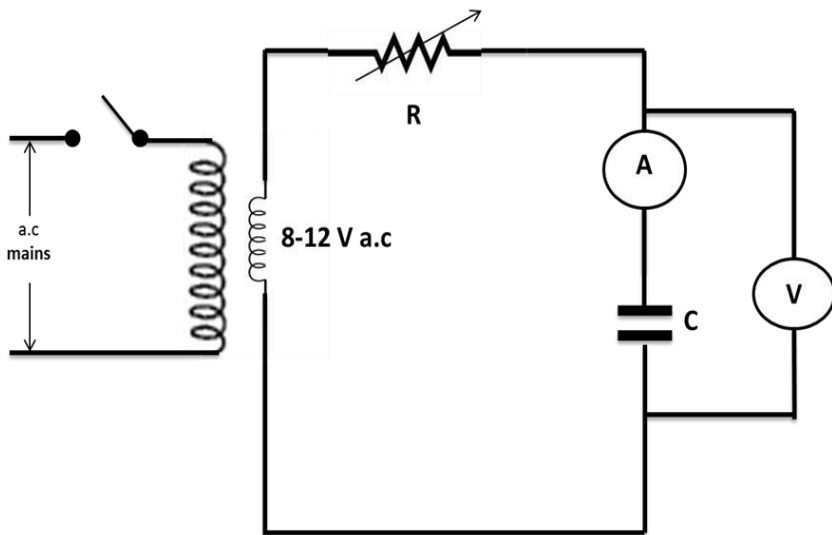To show that the behavior of an capacitance in an A.c. circuit is analogous to that of a resistor which obeys Ohm's law and hence to measure capacitance



A.C Circuit

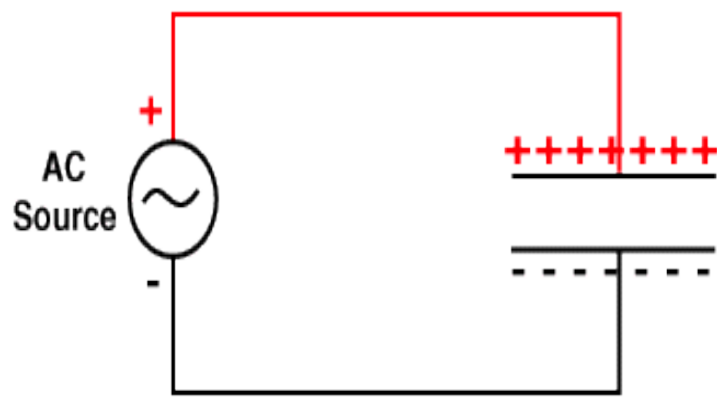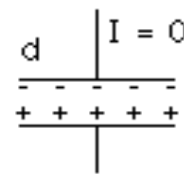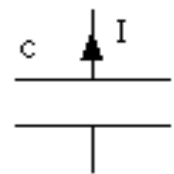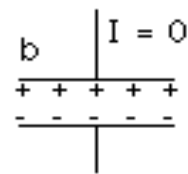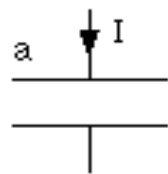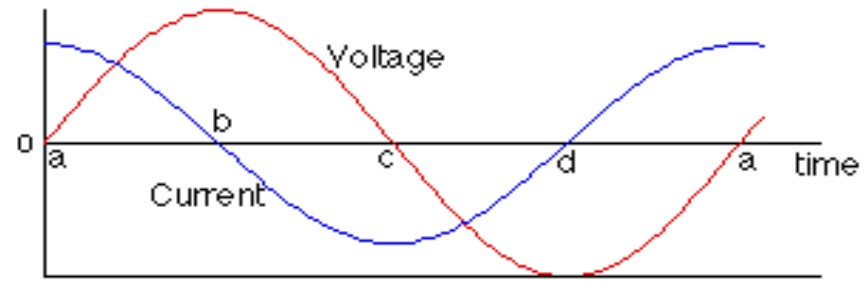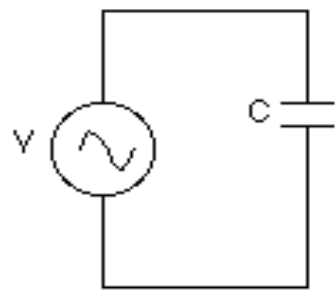

Experiment No. (2)

Data // part (1)

$$f = 50 \text{ Hz}$$

$$C = 2 \mu\text{F}$$

V/ volt	$I/A \times 10^{-3}$
1	
1.5	
2	
2.5	
3	
3.5	
4	
4.5	
5	
5.5	
6	

Experiment No. (2)

Data // part (1)

$$C = 2\mu F$$


Graph & Calculation // part (1)/ Practically

Theory value

$$X_C = \frac{1}{2\pi f C}, \text{ where } f = 50\text{Hz}$$

$$\text{slop} = \frac{V}{I} = X_C$$

Practically
value

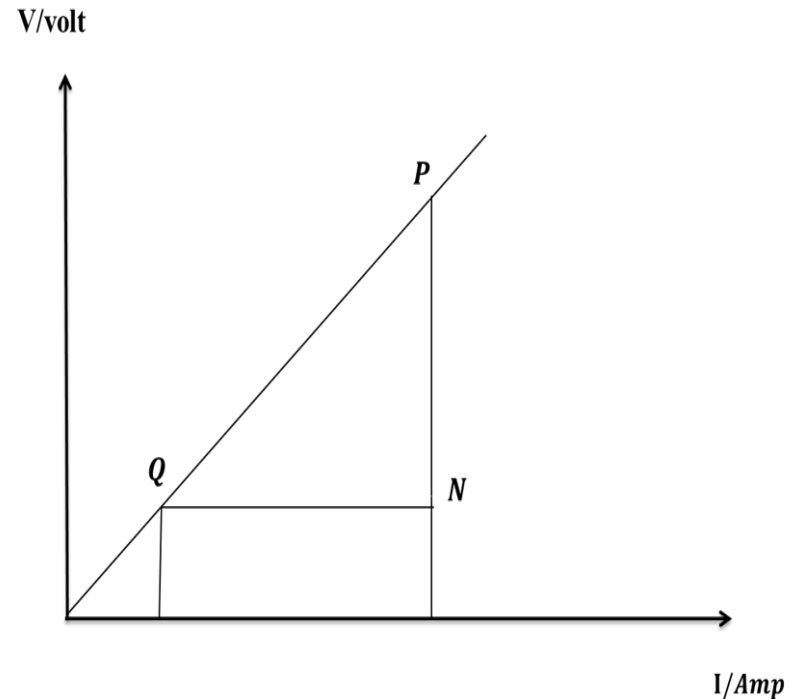

$$\text{Error ratio } (X_C) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

Experiment No. (2)

Data // part (2)

$$f = 50 \text{ Hz}$$

$$C = 4\mu\text{F}$$

V/ volt	$I/A \times 10^{-3}$
1	
1.5	
2	
2.5	
3	
3.5	
4	
4.5	
5	
5.5	
6	

Experiment No. (2)

Data // part (2)

$$C = 4\mu F$$


Graph & Calculation // part (2)/ Practically

Theory value

$$X_C = \frac{1}{2\pi f C}, \text{ where } f = 50\text{Hz}$$

$$\text{slop} = \frac{V}{I} = X_C$$

Practically
value

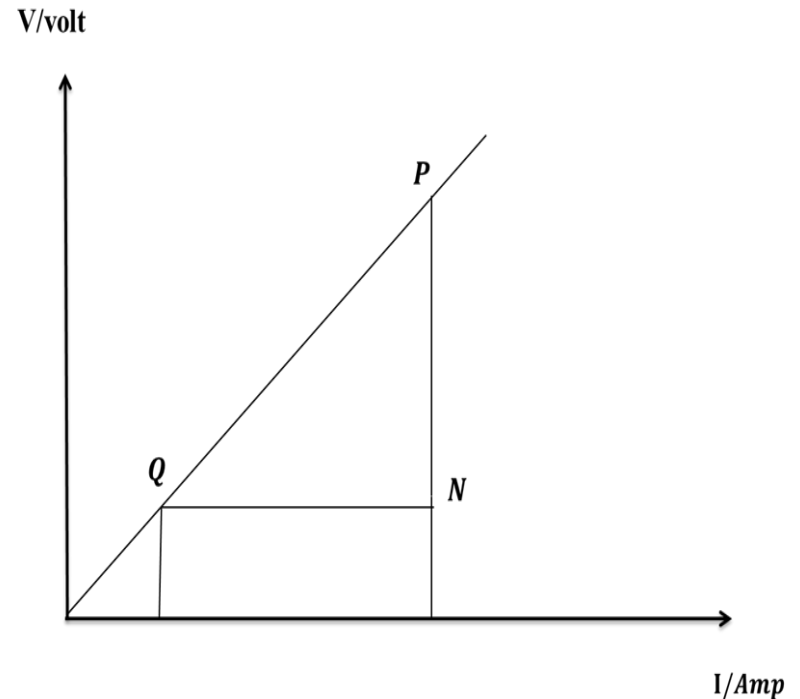

$$\text{Error ratio } (X_C) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

Experiment No. (2)

Data // part (3)

$$C = 2\mu F$$

f Hz	V/ volt	$I/A \times 10^{-3}$	$X_C = \frac{V}{I} / \Omega$	$1/f$ S
30	7.51	3.2		
40	6.8	4		
50	6.5	4.7		
60	6.2	5.3		
70	5.9	5.8		
80	5.6	6.2		
90	5.35	6.6		
100	5.1	6.9		

Experiment No. (2)

Data // part (3)

$$C = 2\mu F$$


Theory value

Graph & Calculation // part (2)/ Practically

$$\text{slop} = \frac{X_C}{1/f} = X_C f$$

Practically value

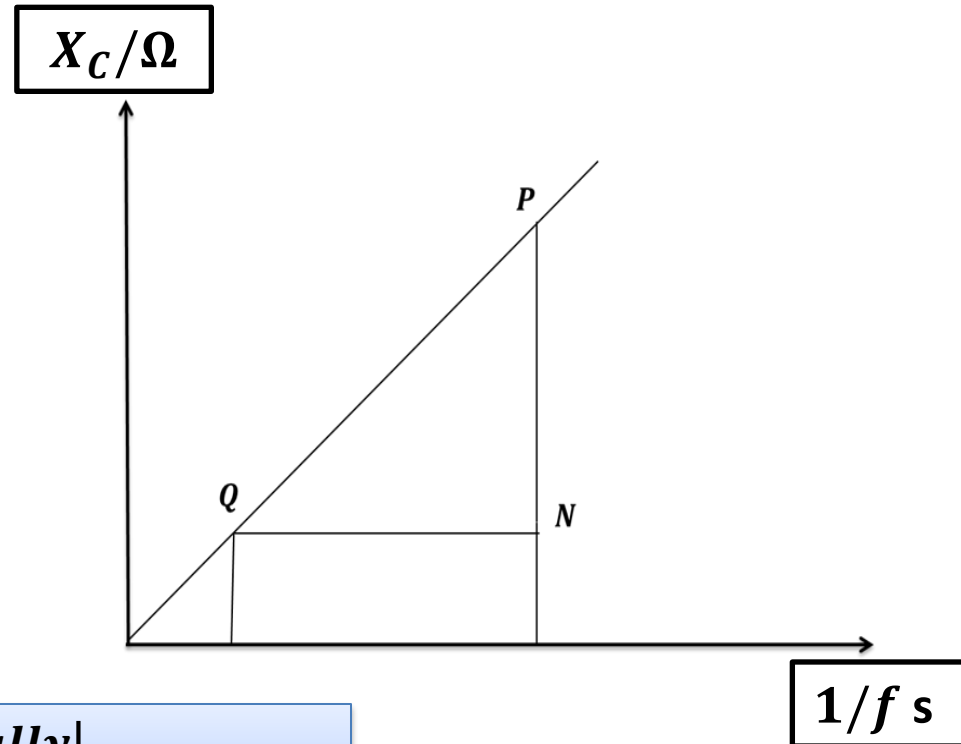
$$X_C = \frac{1}{2\pi f C}$$
$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \text{slop}}$$



$$\text{Error ratio } (C) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

Experiment No. (3)


L-C-R Series and Parallel Resonance

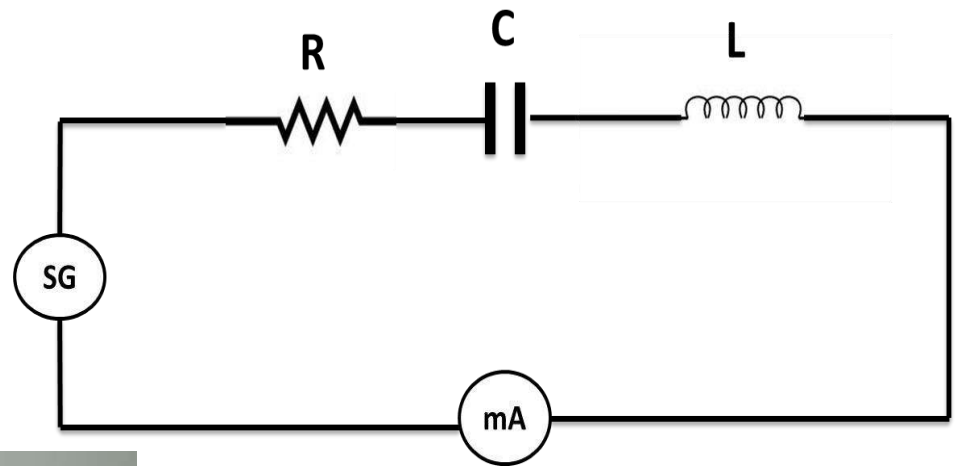


L-C-R Series




Inductive Reactance against Frequency

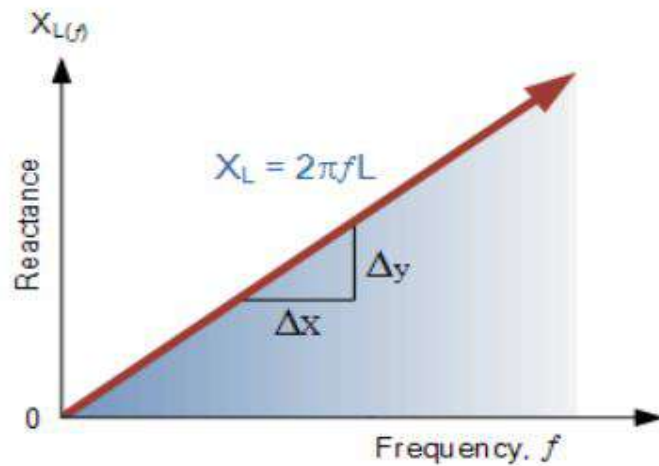

Capacitive Reactance against Frequency

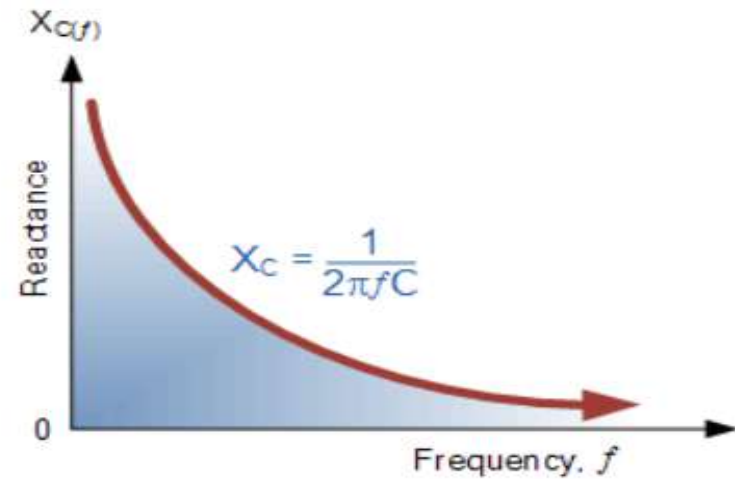

Series Resonance Frequency

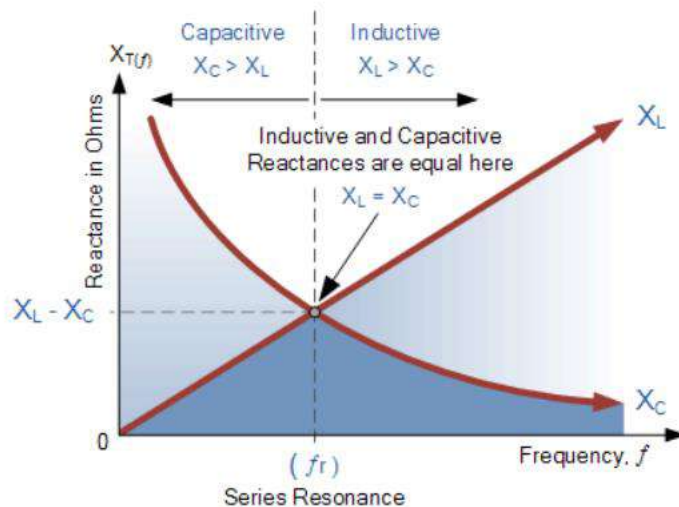


$$X_L = X_C \Rightarrow 2\pi fL = \frac{1}{2\pi fC}$$

$$f^2 = \frac{1}{2\pi L \times 2\pi C} = \frac{1}{4\pi^2 LC}$$


$$f = \sqrt{\frac{1}{4\pi^2 LC}}$$

$$\therefore f_r = \frac{1}{2\pi \sqrt{LC}} \text{ (Hz)} \quad \text{or} \quad \omega_r = \frac{1}{\sqrt{LC}} \text{ (rads)}$$


Series RLC Circuit at Resonance

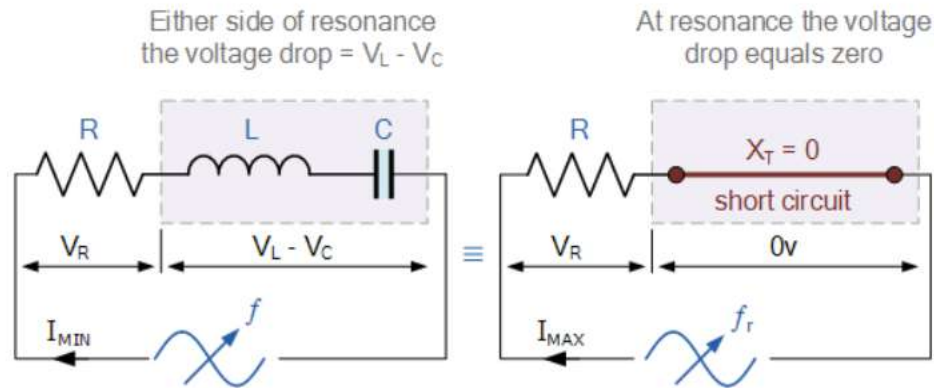

Series Circuit Current at Resonance

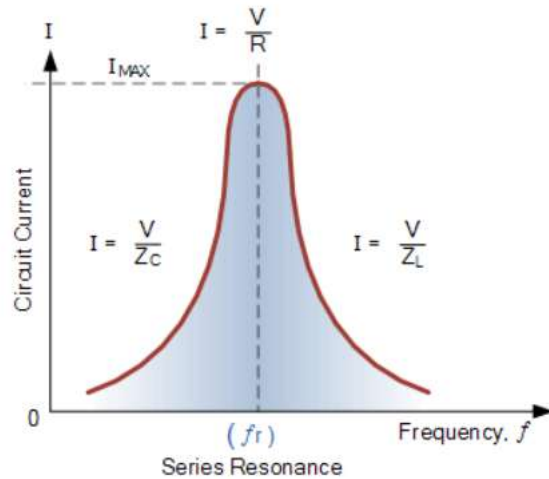

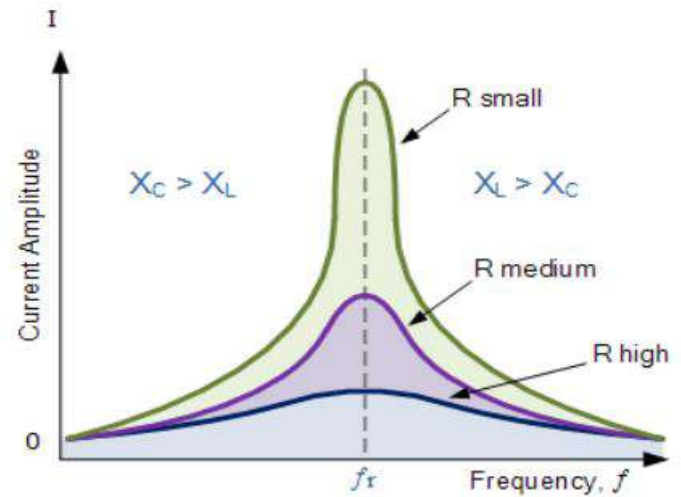Bandwidth of a Series RLC Resonance Circuit



Experiment No. (3)

Data

$$R = 5\Omega$$

$$L = 35\text{ mH}$$

$$C = 6\mu F$$

f / Hz	$I / \text{A} \times 10^{-3}$
50	
60	
70	
80	
90	
100	
150	
200	
300	
400	
500	

f / Hz	$I / \text{A} \times 10^{-3}$
600	
700	
800	
900	
1000	
1500	
2000	
3000	

Experiment No. (3)


$$Q = \frac{2\pi f_0 L}{R}$$

Theory value

Graph & Calculation /
Practically

Practically value


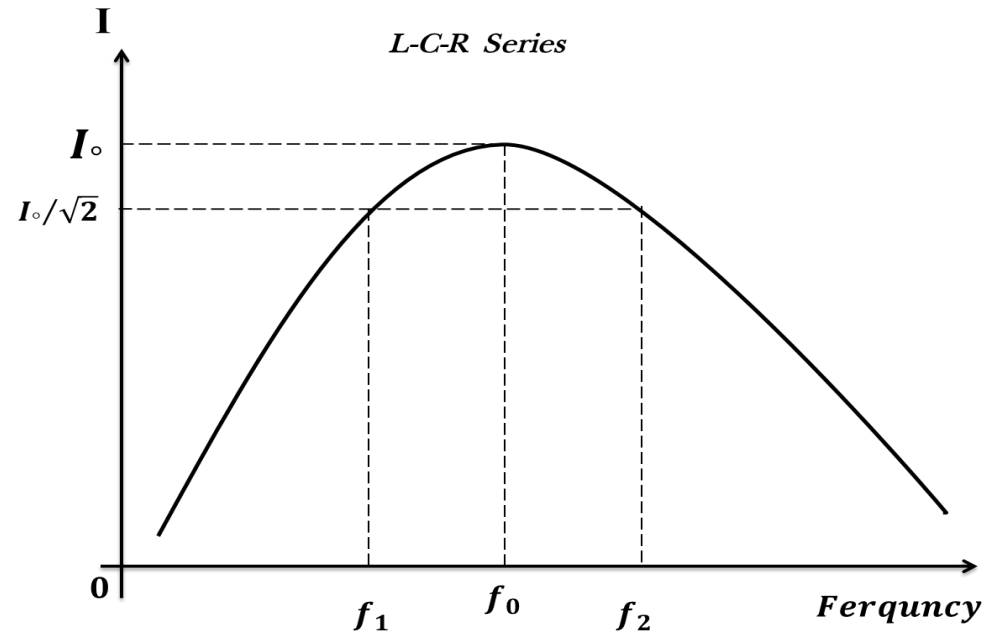
$$\text{slop} = Q = \frac{f_0}{f_2 - f_1}$$



$$\text{Error ratio (Q)} = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

Experiment No. (4)

Time constant for RC-Circuit

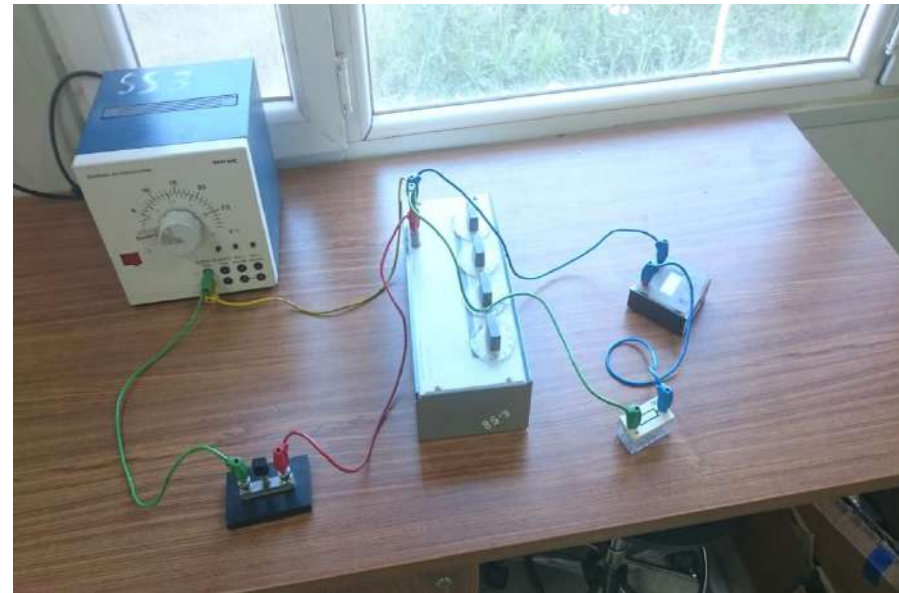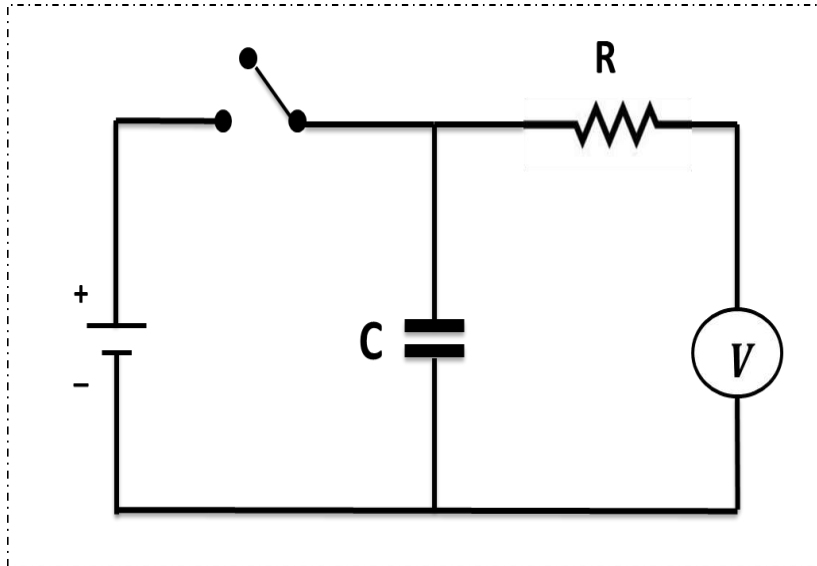

Circuit

Experiment No. (4)

Data

$R = 1M\Omega$

$V_0 = 7.04 v$

$C = 10\mu F$

$R_v = 10.04M\Omega$

T/sec	V/v
0	
10	
20	
30	
40	
50	
60	
70	
80	
90	
100	
110	

T/sec	V/v
120	
130	
140	
150	
160	
170	
180	
190	
200	
210	
220	

T/sec	V/v
230	
240	
250	

Experiment No. (4)


$$\tau = RC = (R + R_v) \times C = ??$$

Theory value

Graph & Calculation /
Practically

Practically value

$$\text{slop} = RC = \tau$$

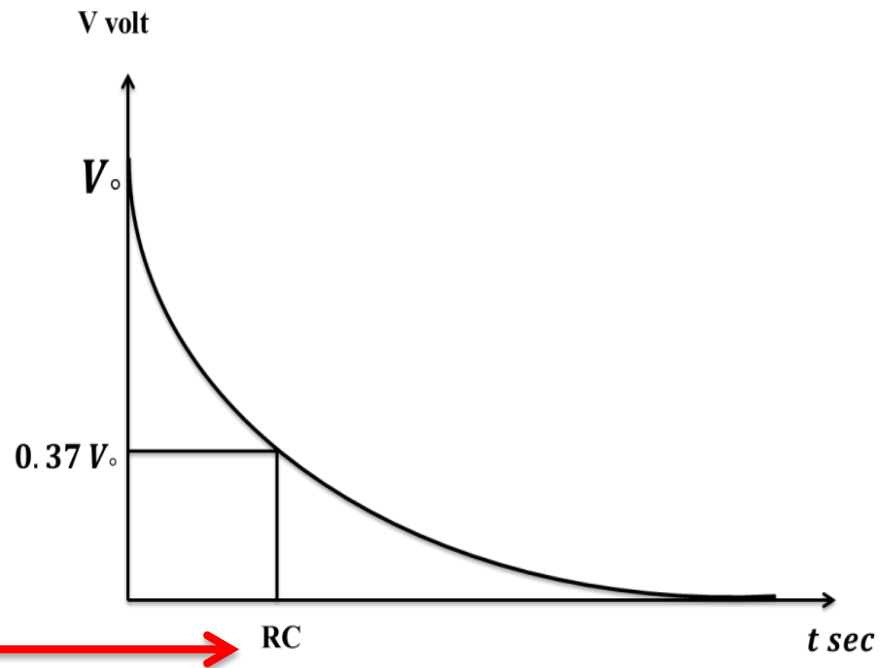

$$\text{Error ratio } (\tau) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

Experiment No. (4)

$$T_{1/2} = 0.693 RC$$


Theory value

Graph & Calculation /
Practically

Practically value

$$\text{slop} = RC = ??$$

$$T_{1/2} = 0.693 RC$$

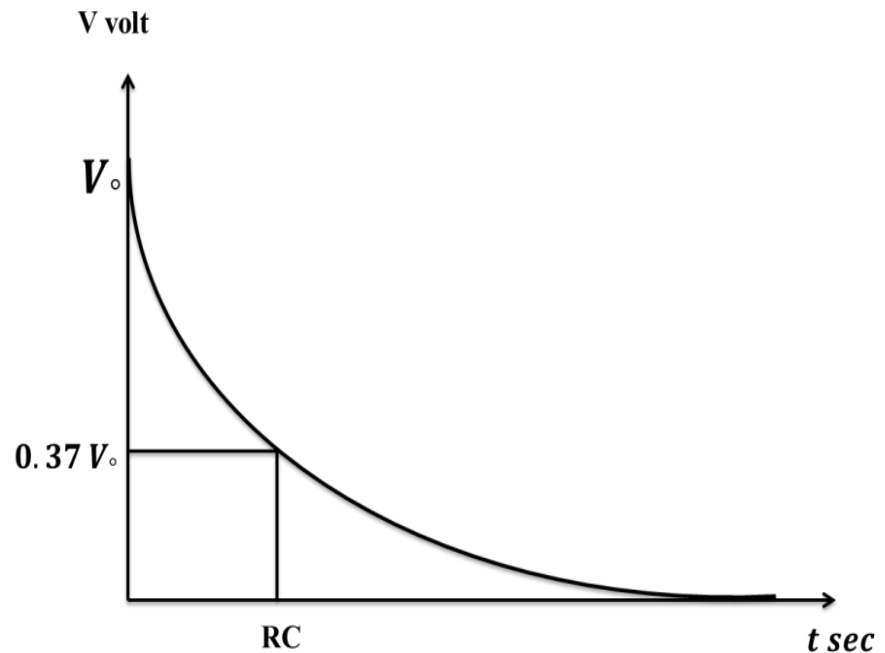

$$\text{Error ratio } (T_{1/2}) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

Experiment No. (5)

*Experiments with a deflection magnetometer:
To investigate how the magnetic flux density due
to the current in a long straight wire varies with*

- (a) the current in the wire*
- (b) the distance from the wire*



Experiment No. (5)

Data // part 1

D= 8 cm

Current I /Amp	Magnetometer deflections					$\tan \theta$
	θ_1	θ_2	θ_3	θ_4	Mean θ°	
0.3						
0.6						
0.9						
1.2						
1.5						
1.8						
2.1						
2.4						
2.7						

Experiment No. (5)

Graph & Calculation /
Practically


$$B_{E1} \tan \theta = \frac{\mu_0 I}{2\pi D}$$

slope 1

$$\text{slope} = \frac{\Delta \tan \theta}{\Delta I}$$

$$\text{slop1} = \frac{1}{\text{slope}}$$
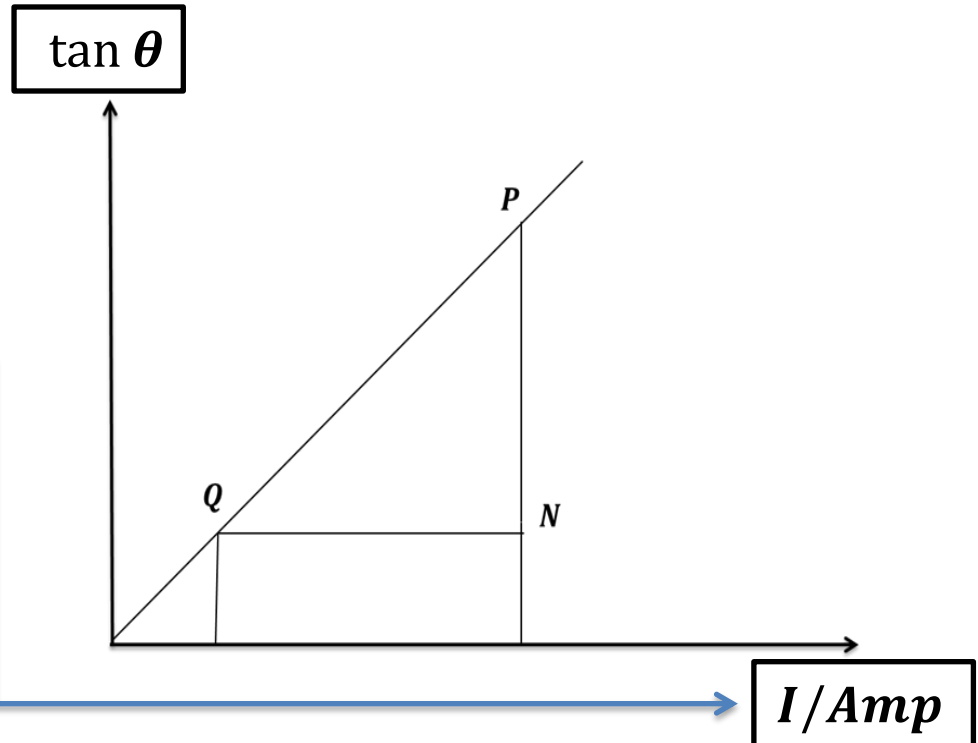
$$\therefore B_{E1} = \frac{\mu_0}{2\pi \times D} \times \text{slop1}$$



Experiment No. (5)

Data // part 2

$I = 2.6 \text{ Amp.}$

Distance D/cm	Magnetometer deflections					$\cot \theta$
	θ_1	θ_2	θ_3	θ_4	Mean θ°	
8						
10						
12						
14						
16						

Experiment No. (5)


slope 2

$$D = \frac{\mu_0 I}{2\pi B_{E2}} \cot \theta$$

Graph & Calculation /
Practically

$$\text{slope 2} = \frac{\Delta \cot \theta}{\Delta D}$$
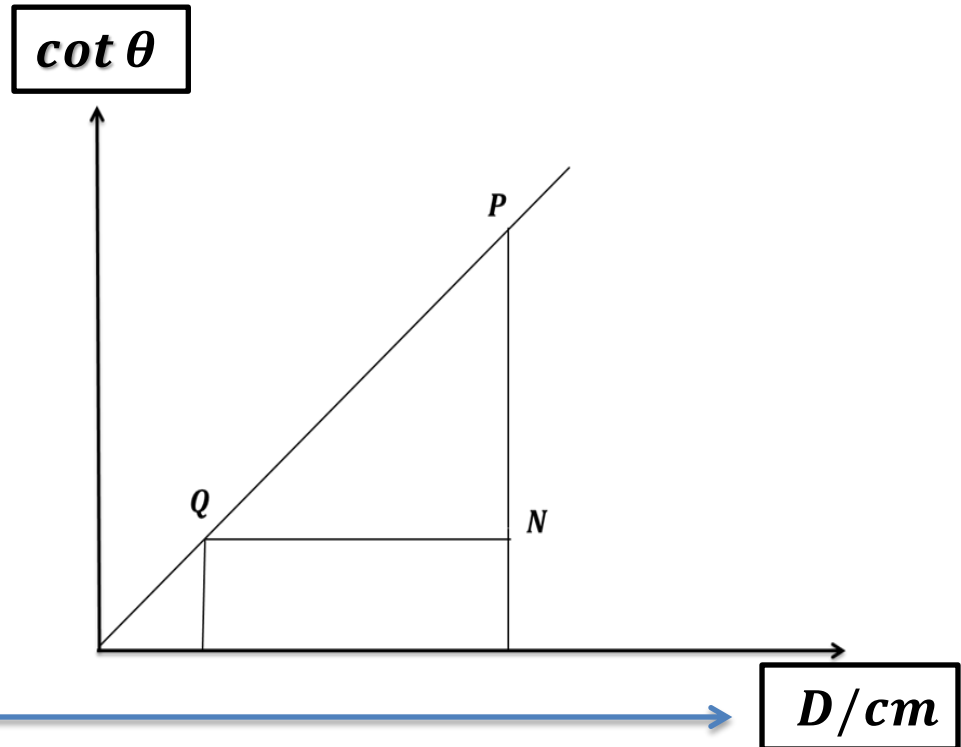
$$\therefore B_{E2} = \frac{\mu_0 \times I}{2\pi \times \text{slope 2}}$$



$$\text{Error ratio } (B_E) = \left| \frac{B_{E2} - B_{E1}}{B_{E2}} \right| \times 100\%$$

Thanks