

# Digital Magnitude Comparator






A comparator is a special combinational circuit designed primarily to compare the relative magnitude of two binary numbers .an n-bit comparator receives two n-bit numbers A and B as inputs and the outputs are:

- $A > B$  (G)
- $A < B$  (L)
- $A = B$  (E)

Inputs

A

B

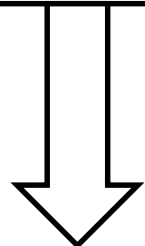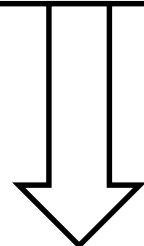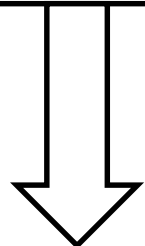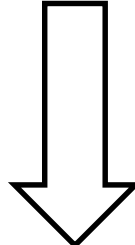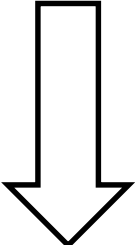

G

L

E

Outputs

# 1 bit Comparator

DEC.	A	B	G	L	E
0	0	0	0	0	1
1	1	0	1	0	0
2	0	1	0	1	0
3	1	1	0	0	1


# 1 bit Comparator


$$G = A\bar{B}$$

$$L = \bar{A}B$$


$$E = \bar{A}\bar{B} + AB$$

# 1 Bit Comparator

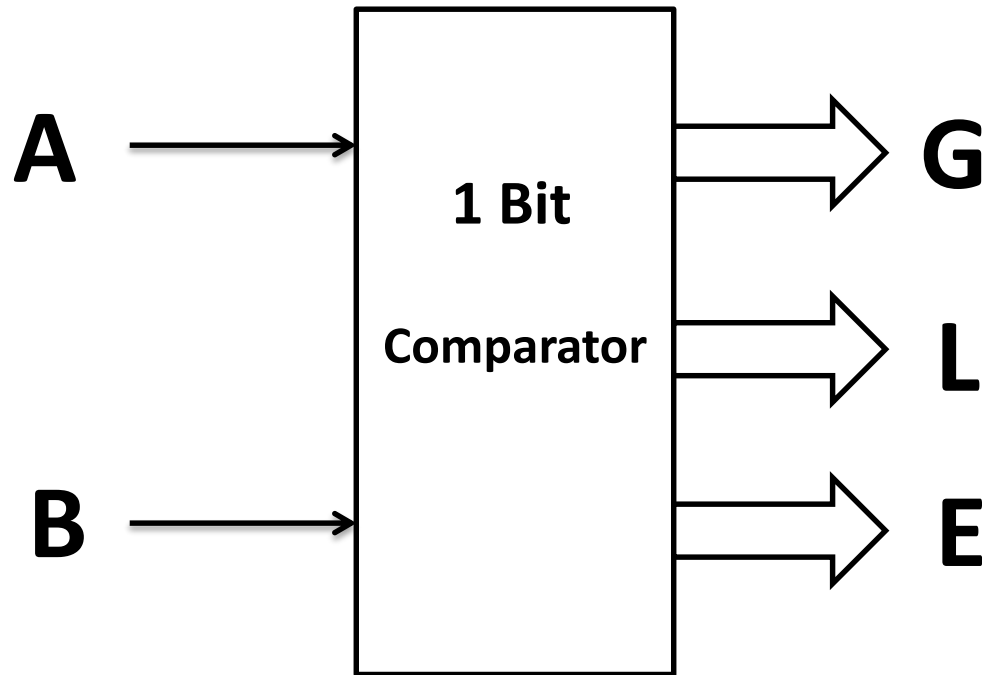

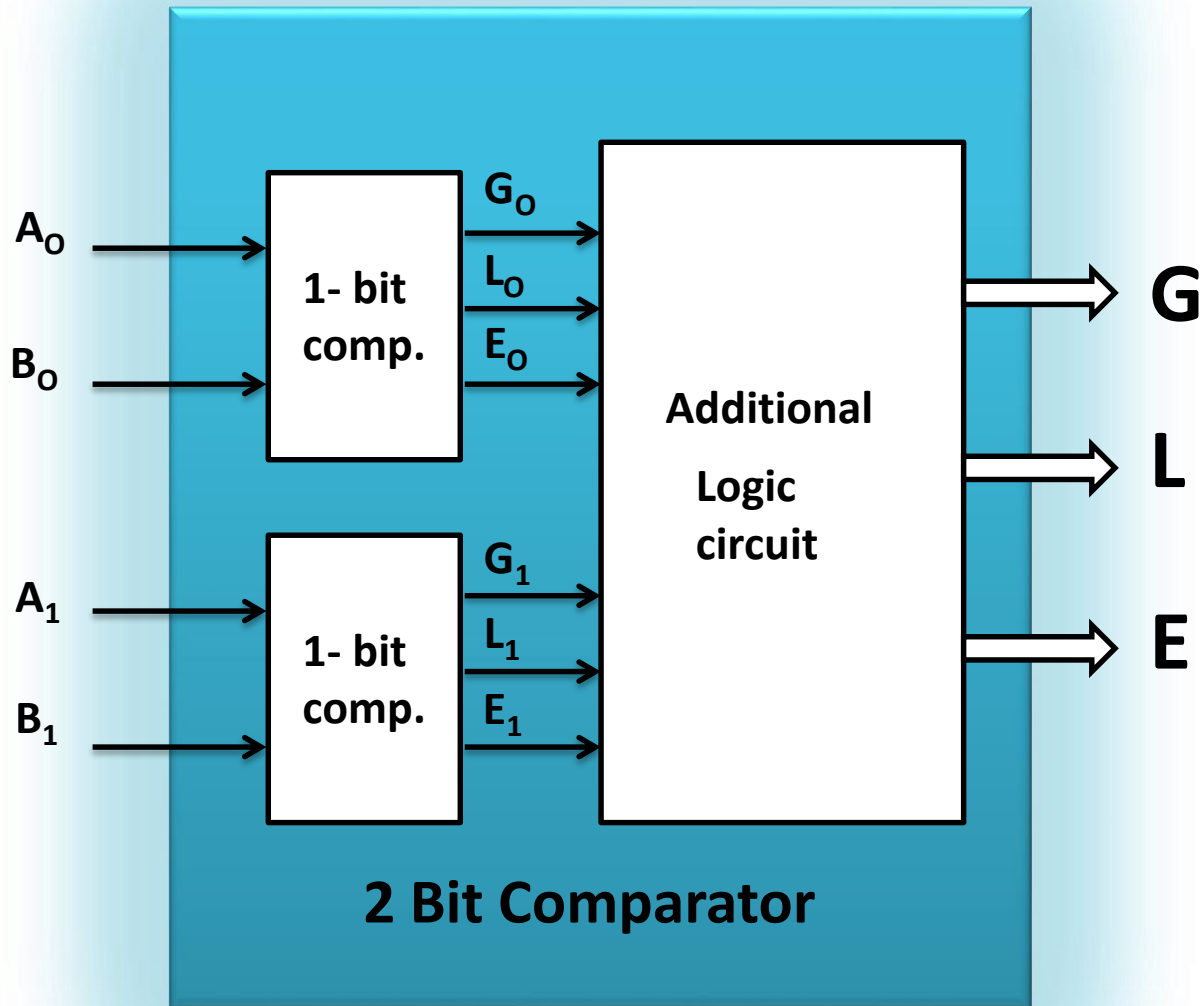

# 2 Bit Comparator

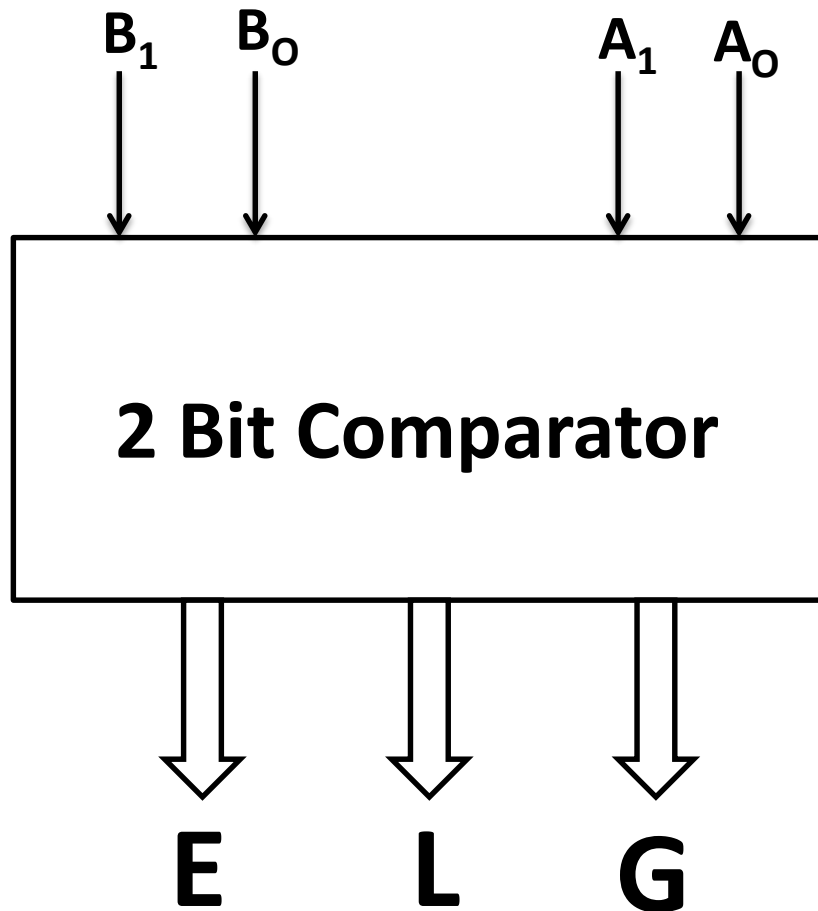

**If  $A_1 < B_1$  or  $A_1 = B_1$  And  $A_0 < B_0$**

$$\mathbf{G = G_1 + E_1 \cdot G_0}$$


**If  $A_1 > B_1$  or  $A_1 = B_1$  And  $A_0 > B_0$**

$$\mathbf{L = L_1 + E_1 \cdot L_0}$$

**If  $A_1 = B_1$  and  $A_0 = B_0$**

$$\mathbf{E = E_1 \cdot E_0}$$



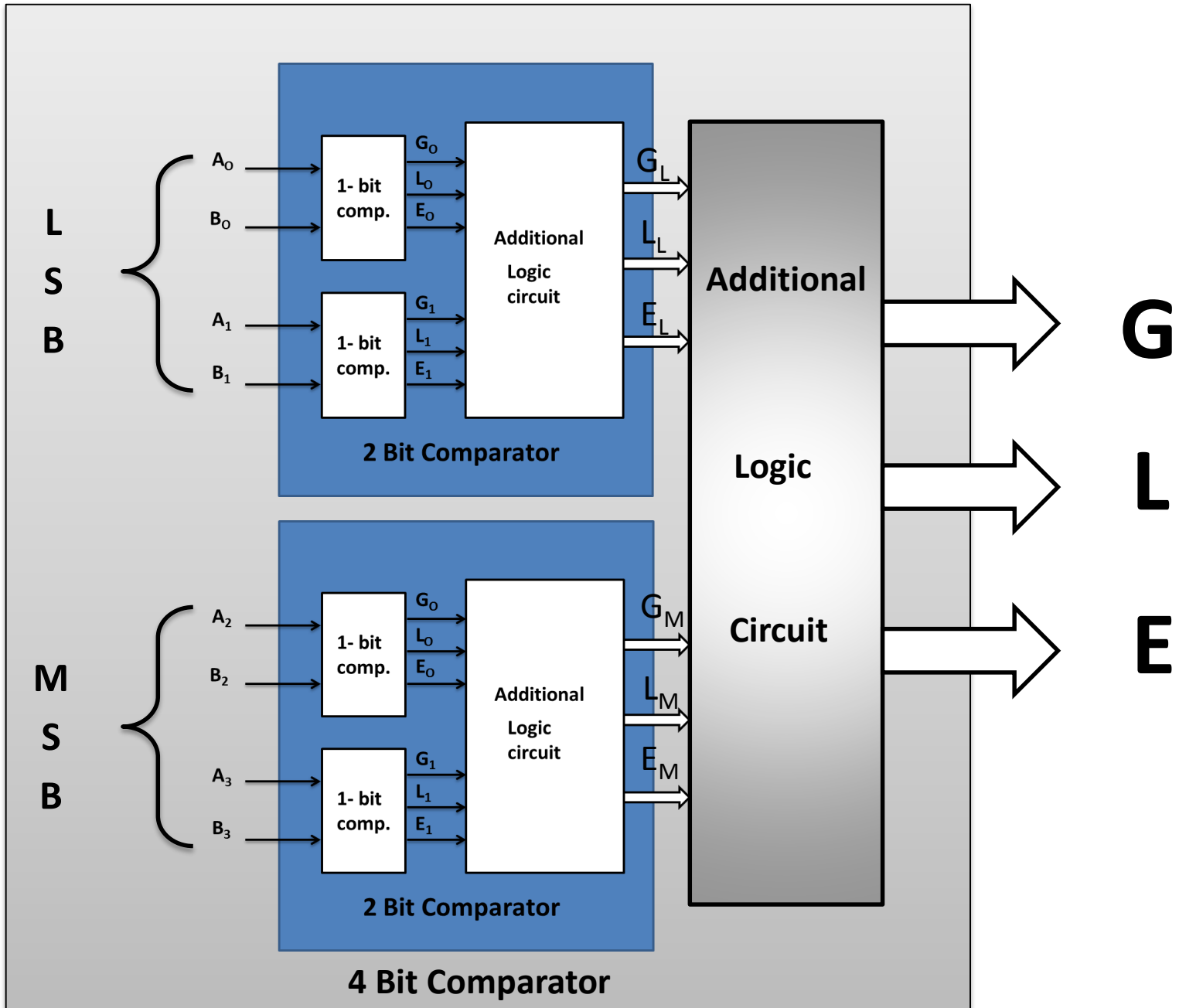

# 4 Bit Comparator

$$G = G_M + E_M \cdot G_L$$

$$L = L_M + E_M \cdot L_L$$

$$E = E_M \cdot E_L$$

