

University of Salahaddin – Erbil  
College of Science  
Physics Department



# Laboratory Manual

# Electricity and Magnetism

## 2<sup>nd</sup> Course

Assist. Lecturer. Safa Gh. Hameed


[Safa.hameed@su.edu.krd](mailto:Safa.hameed@su.edu.krd)

1Year – Physics  
2023-2024


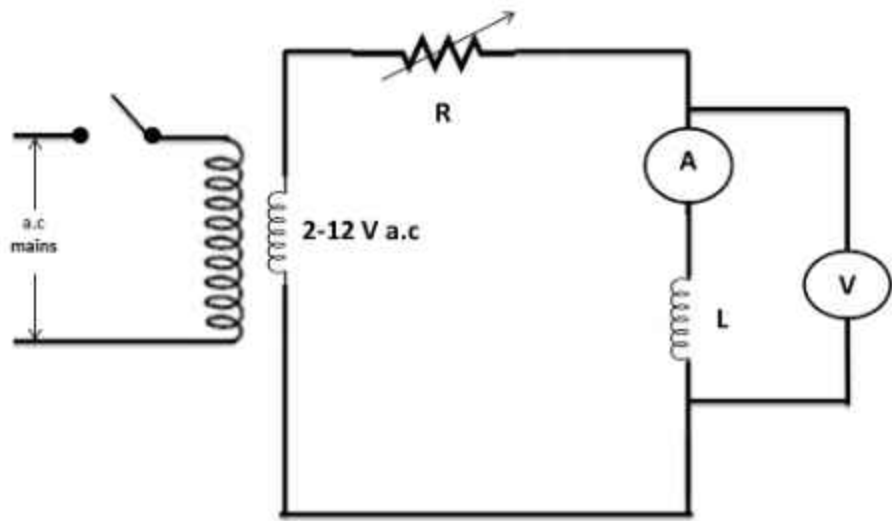
## *Experiment No. ( 1 )*

*To show that the behavior of an inductance in A.c. circuit is analogous to that of a resistor which obeys Ohm's law and hence to measure inductance*



**A.C Circuit**

# *Experiment No. ( 1 )*

**Data // part (1)**

$$f = 1500 \text{ Hz}$$

$$L = 35 \text{ mH}$$

<b><i>V/ volt</i></b>	<b><i>I/A × 10<sup>-3</sup></i></b>
<b><i>1</i></b>	
<b><i>1.5</i></b>	
<b><i>2</i></b>	
<b><i>2.5</i></b>	
<b><i>3</i></b>	
<b><i>3.5</i></b>	
<b><i>4</i></b>	
<b><i>4.5</i></b>	

## Experiment No. (1)

Data // part (1)

$$L = 35 \text{ mH}$$


Theory value

$$X_L = 2\pi fL, \text{ where } f = 1500 \text{ Hz}$$

Graph & Calculation // part (1)/ Practically

$$\text{slop} = \frac{\Delta V}{\Delta I} = X_L$$

Practically  
value

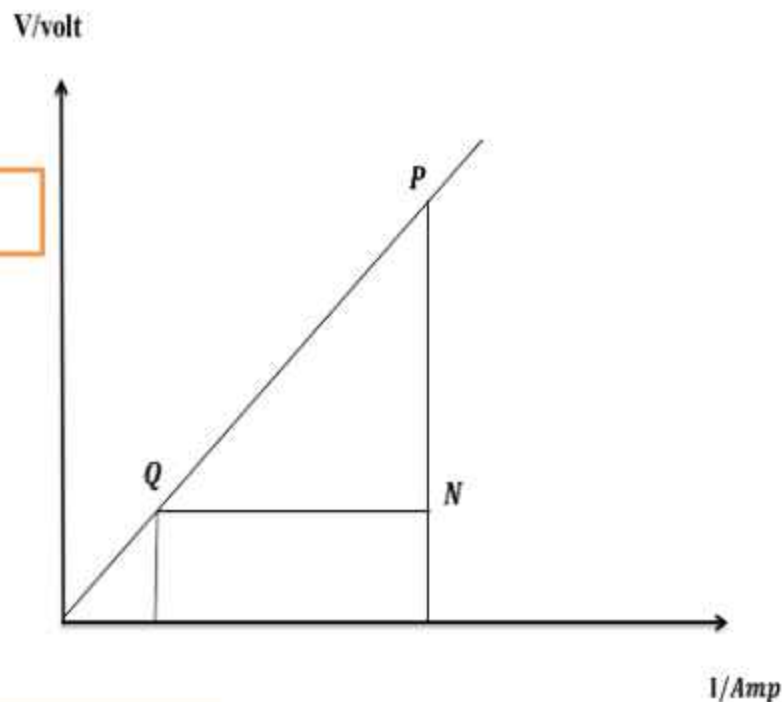

$$\text{Error ratio } (X_L) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

# Experiment No. (1)

Data // part (2)

$$L = 35 \text{ mH}$$

$f \text{ Hz}$	$V/ \text{ volt}$	$I/A \times 10^{-3}$	$X_L = \frac{V}{I} / \Omega$
1000			
2000			
3000			
4000			
5000			
6000			
7000			
8000			
9000			

# Experiment No. (1)

Data // part (2)

$L = 35 \text{ mH}$

Theory value


Graph & Calculation // part (2)/ Practically

$$\text{slop} = \frac{\Delta X_L}{\Delta f}$$

Practically value

$$X_L = 2\pi fL$$

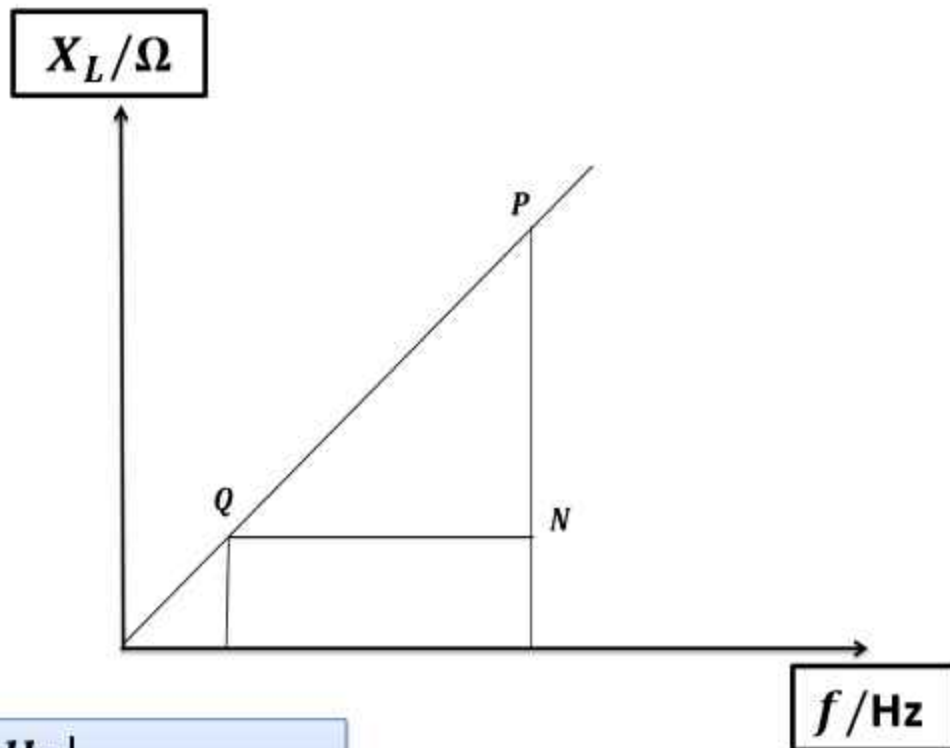
$$L = \frac{X_L}{2\pi f} = \frac{\text{slop}}{2\pi}$$










$$\text{Error ratio (L)} = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$
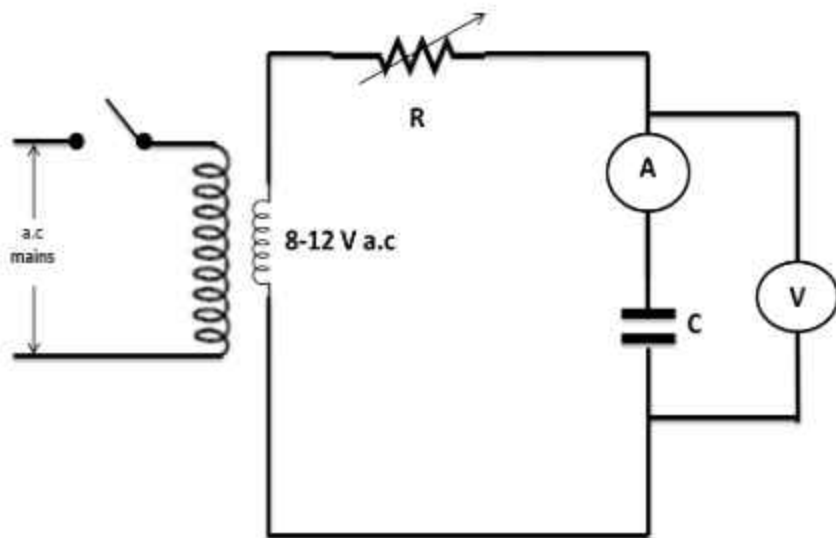
## *Experiment No. ( 2 )*

*To show that the behavior of an capacitance in an A.c. circuit is analogous to that of a resistor which obeys Ohm's law and hence to measure capacitance*



**A.C Circuit**

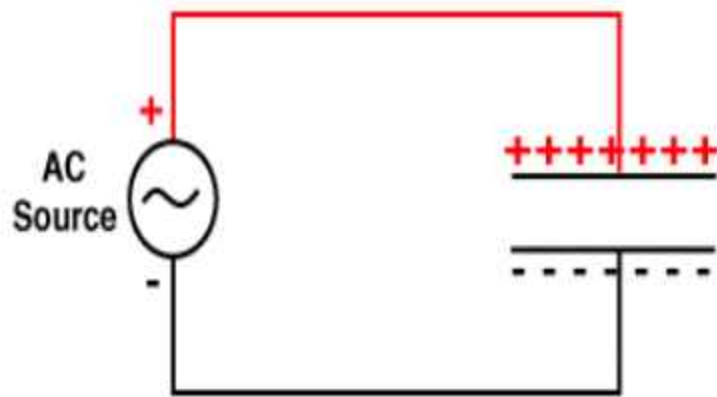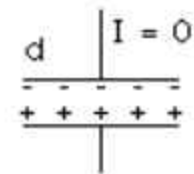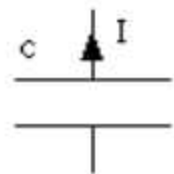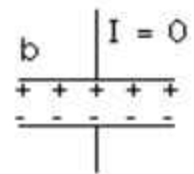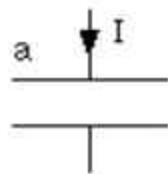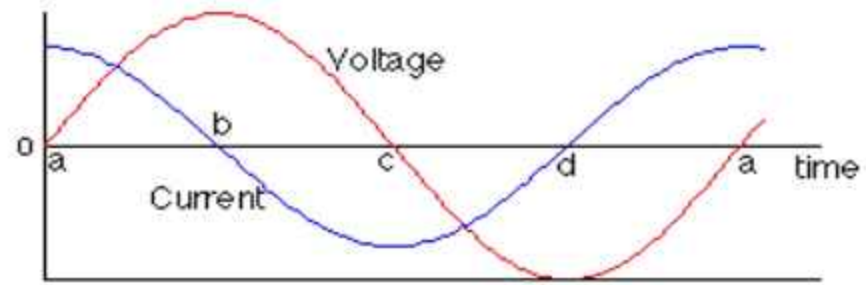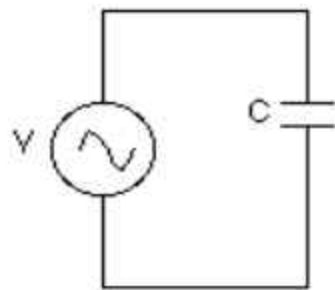



# Experiment No. ( 2 )

Data // part (1)

$$f = 50 \text{ Hz}$$

$$C = 2 \mu\text{F}$$

V/ volt	$I/A \times 10^{-3}$
1	
1.5	
2	
2.5	
3	
3.5	
4	
4.5	
5	
5.5	
6	

# Experiment No. ( 2 )

Data // part (1)

$$C = 2\mu F$$


Graph & Calculation // part (1)/ Practically

Theory value

$$X_C = \frac{1}{2\pi f C}, \text{ where } f = 50\text{Hz}$$

$$\text{slop} = \frac{V}{I} = X_C$$

Practically  
value

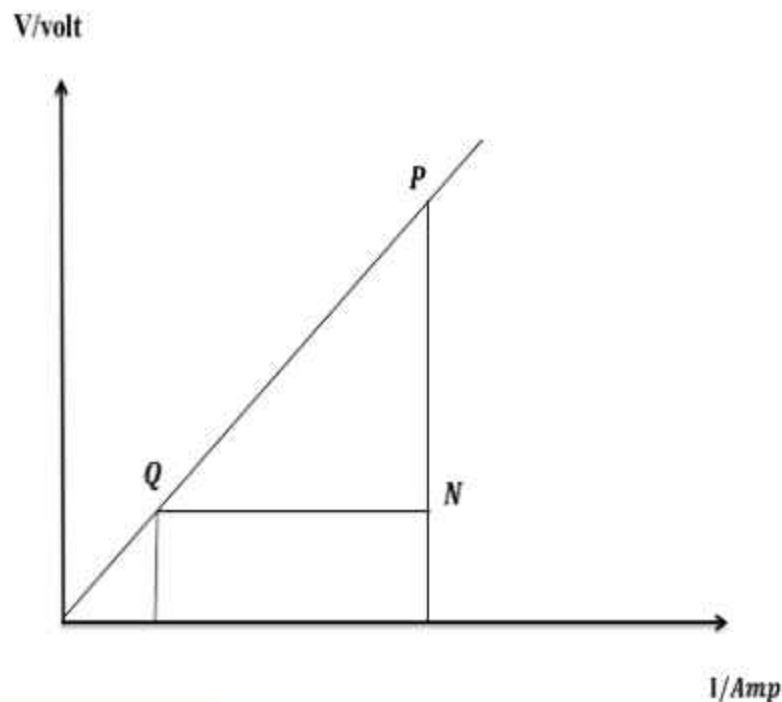

$$\text{Error ratio } (X_C) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

# Experiment No. ( 2 )

Data // part (2)

$$f = 50 \text{ Hz}$$

$$C = 4 \mu\text{F}$$

V/ volt	$I/A \times 10^{-3}$
1	
1.5	
2	
2.5	
3	
3.5	
4	
4.5	
5	
5.5	
6	

# Experiment No. ( 2 )

Data // part (2)

$$C = 4\mu F$$


Graph & Calculation // part (2)/ Practically

Theory value

$$X_C = \frac{1}{2\pi f C}, \text{ where } f = 50\text{Hz}$$

$$\text{slop} = \frac{V}{I} = X_C$$

Practically  
value

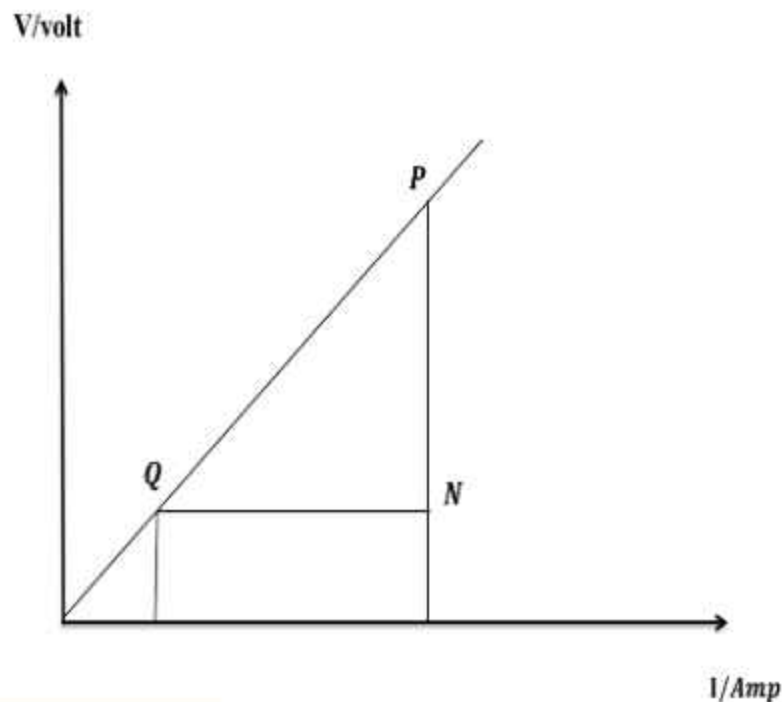

$$\text{Error ratio } (X_C) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

# Experiment No. ( 2 )

Data // part (3)

$$C = 2\mu F$$

$f$ Hz	V/ volt	$I/A \times 10^{-3}$	$X_C = \frac{V}{I} / \Omega$	$1/f$ s
30				
40				
50				
60				
70				
80				
90				
100				

# Experiment No. ( 2 )

Data // part (3)

$$C = 2\mu F$$


Theory value

Graph & Calculation // part (2)/ Practically

$$\text{slop} = \frac{X_C}{1/f} = X_C f$$

Practically value

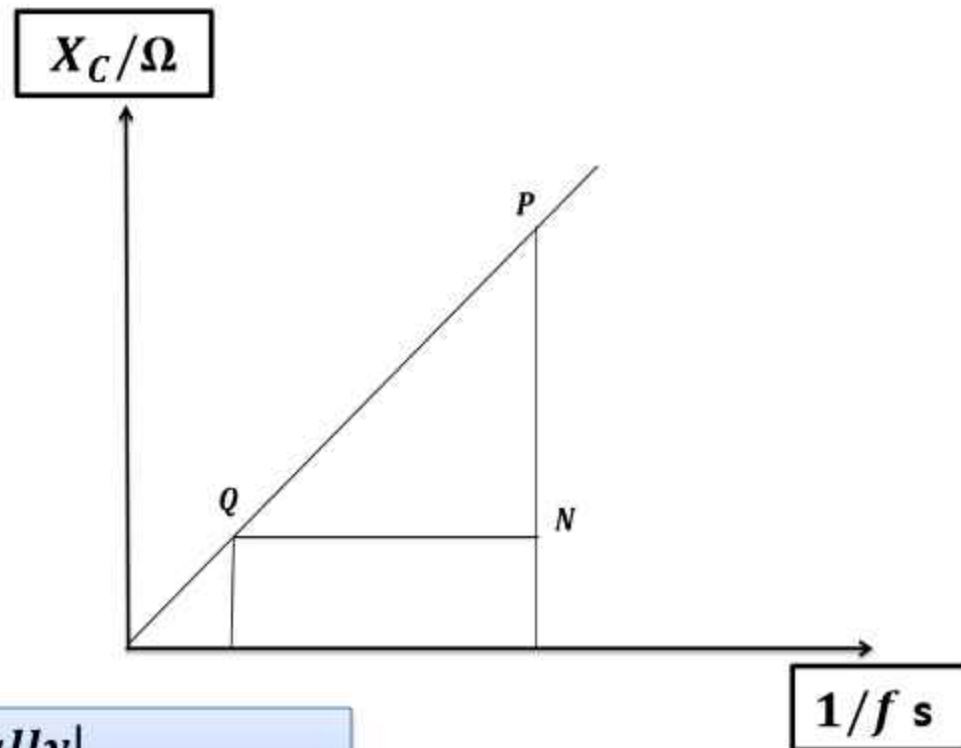
$$X_C = \frac{1}{2\pi f C}$$
$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \text{slop}}$$



$$\text{Error ratio (C)} = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

# *Experiment No. ( 3 )*


## *L-C-R Series and Parallel Resonance*

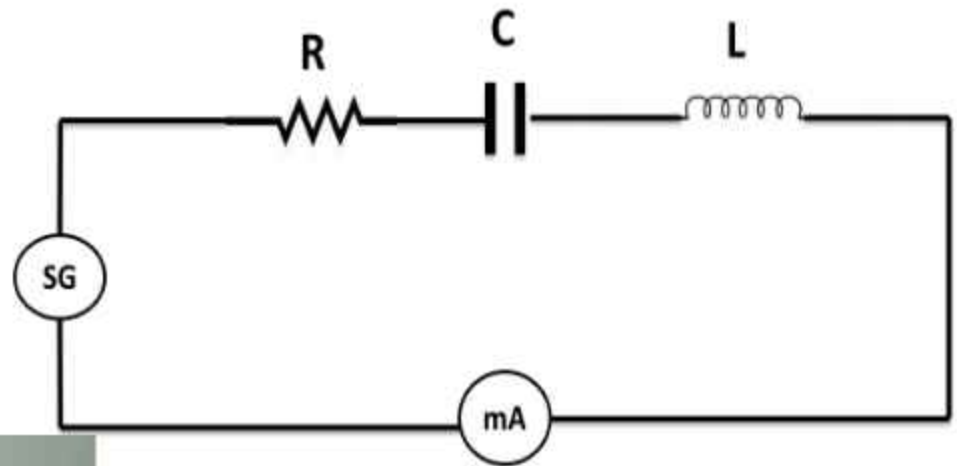


*L-C-R Series*




## Inductive Reactance against Frequency

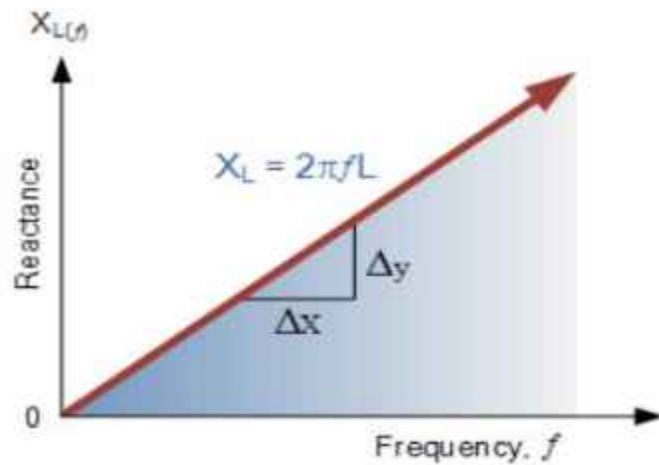
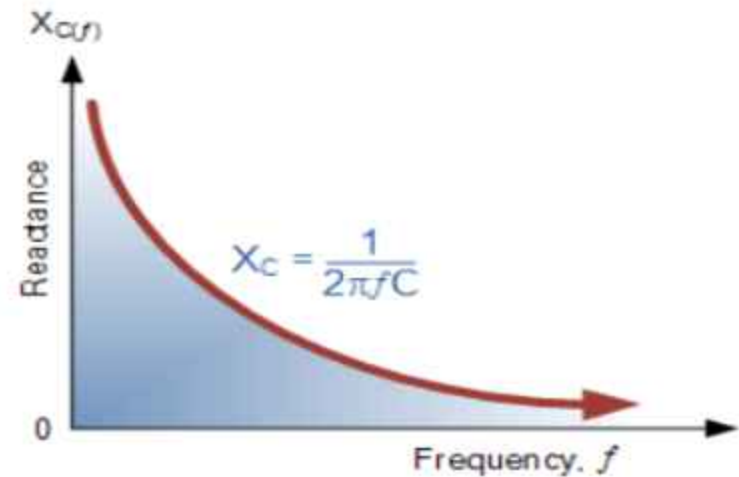
## Capacitive Reactance against Frequency



## Series Resonance Frequency

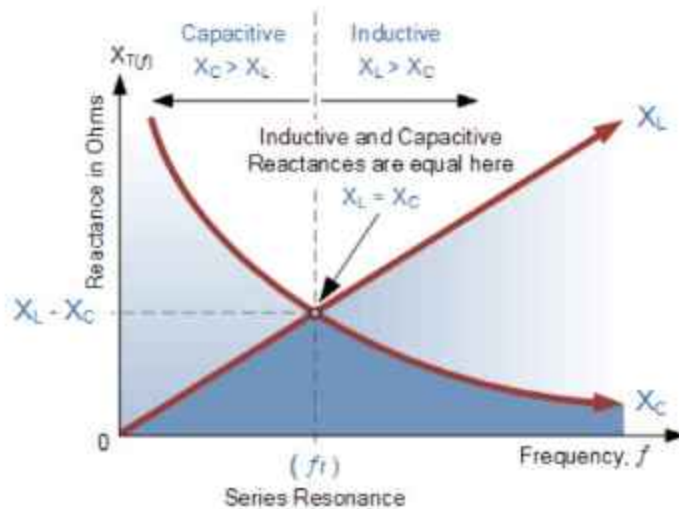

$$X_L = X_C \Rightarrow 2\pi fL = \frac{1}{2\pi fC}$$


$$f^2 = \frac{1}{2\pi L \times 2\pi C} = \frac{1}{4\pi^2 LC}$$

$$f = \sqrt{\frac{1}{4\pi^2 LC}}$$


$$\therefore f_r = \frac{1}{2\pi \sqrt{LC}} \text{ (Hz)} \quad \text{OR} \quad \omega_r = \frac{1}{\sqrt{LC}} \text{ (rads)}$$




## Series RLC Circuit at Resonance

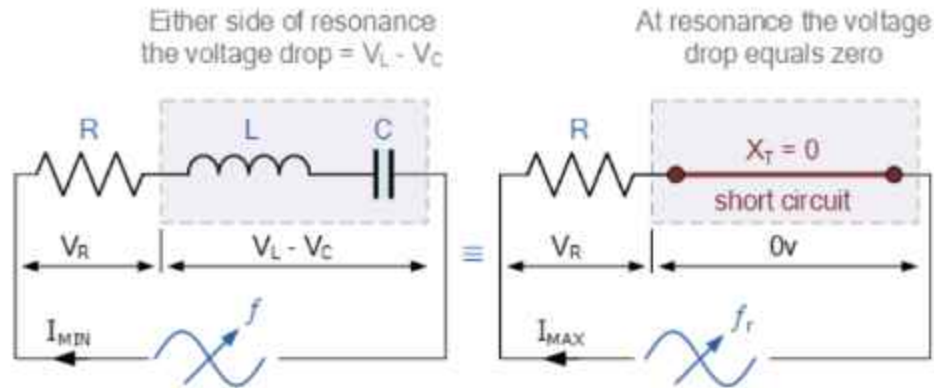

## Series Circuit Current at Resonance

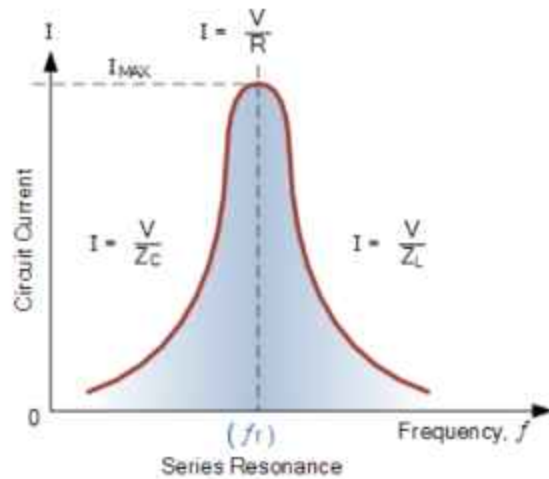
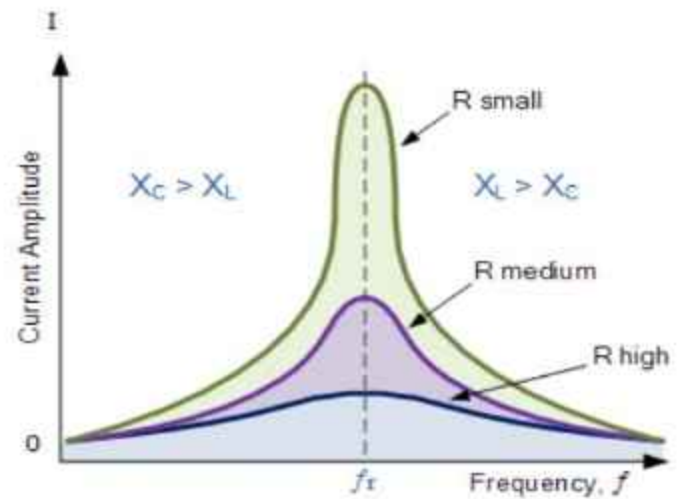
## Bandwidth of a Series RLC Resonance Circuit



# Experiment No. ( 3 )

Data

$R = 5\Omega$

$L = 35\text{ mH}$

$C = 6\mu F$

$f / \text{Hz}$	$I / \text{A} \times 10^{-3}$
50	
60	
70	
80	
90	
100	
150	
200	
300	
400	
500	

$f / \text{Hz}$	$I / \text{A} \times 10^{-3}$
600	
700	
800	
900	
1000	
1500	
2000	
3000	

# Experiment No. ( 3 )


$$Q = \frac{2\pi f_0 L}{R}$$

Theory value

Graph & Calculation /  
Practically

Practically value


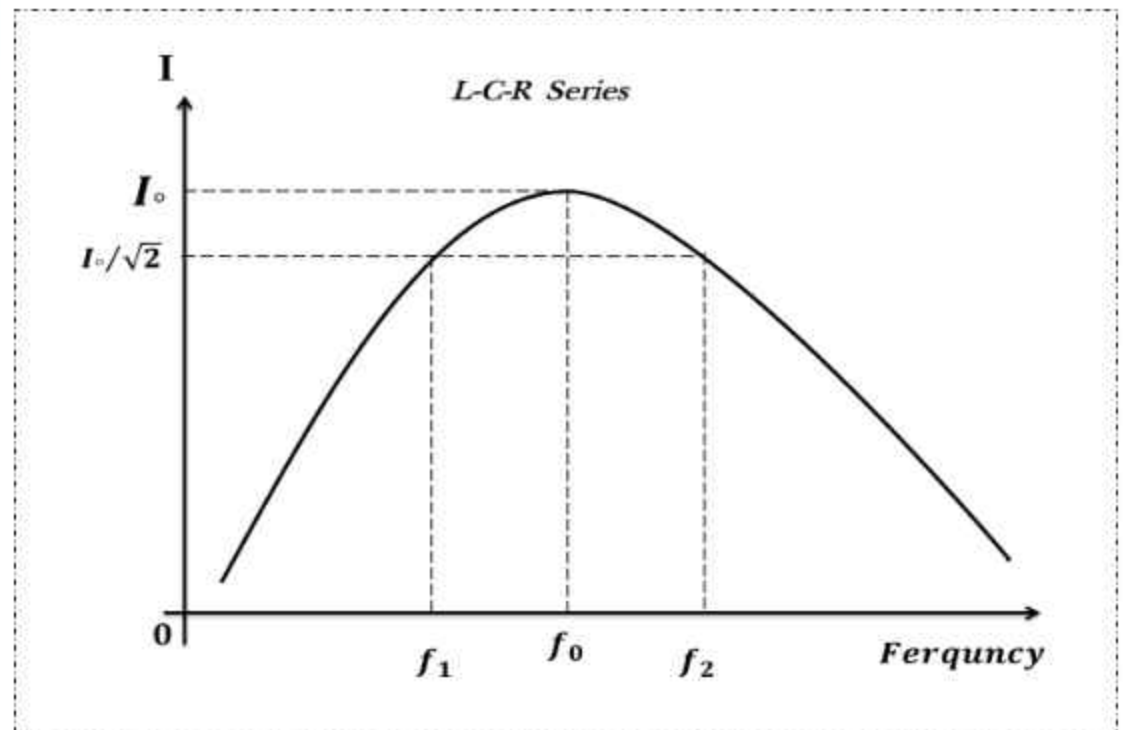
$$\text{slop} = Q = \frac{f_0}{f_2 - f_1}$$



$$\text{Error ratio } (f_0) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

# *Experiment No. ( 4 )*

## *Time constant for RC-Circuit*

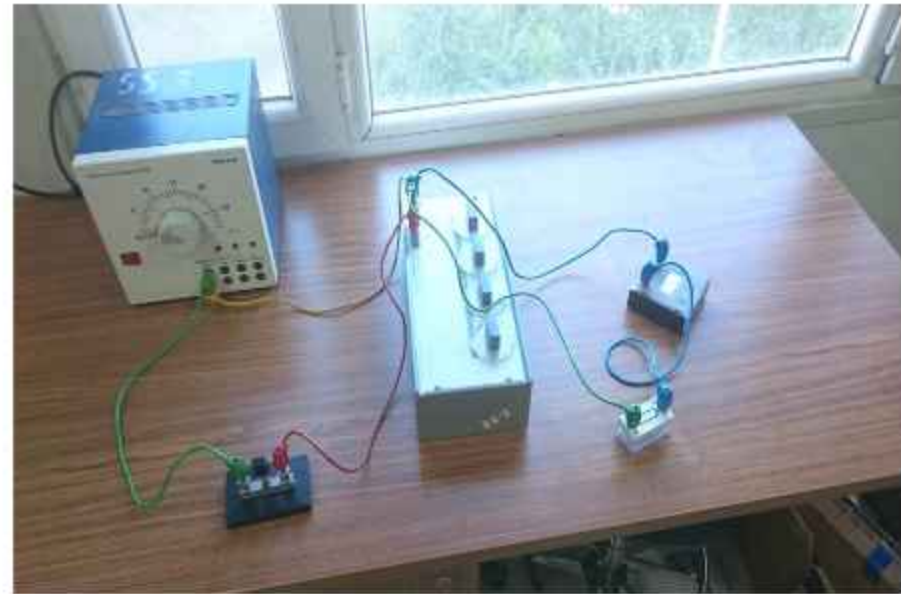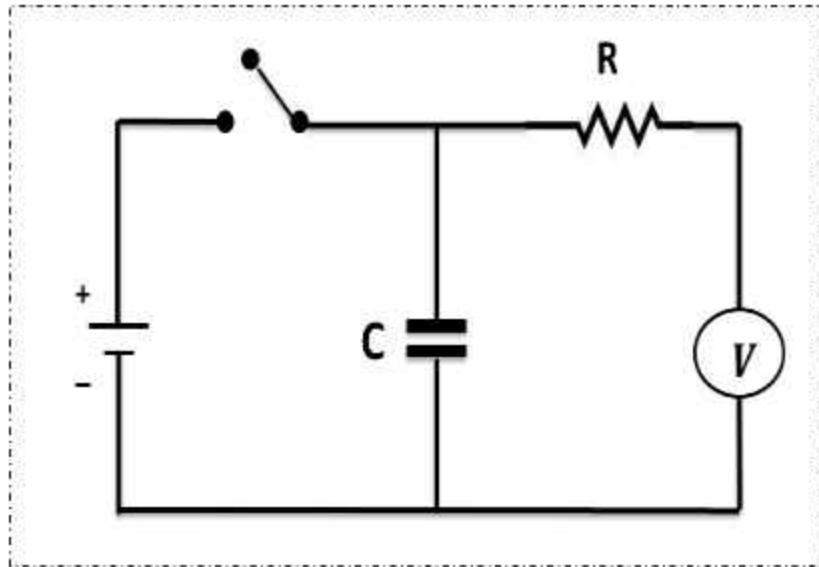

*Circuit*

# Experiment No. ( 4 )

Data

$R = 1M\Omega$

$V_0 = 7.04 v$

$C = 10\mu F$

$R_v = 10.04M\Omega$

$T/sec$	$V/v$
0	
10	
20	
30	
40	
50	
60	
70	
80	
90	
100	
110	

$T/sec$	$V/v$
120	
130	
140	
150	
160	
170	
180	
190	
200	
210	
220	

$T/sec$	$V/v$
230	
240	
250	

## Experiment No. (4)


$$\tau = RC = (R + R_v) \times C = ??$$

Theory value

Graph & Calculation /  
Practically

Practically value

$$\text{slop} = RC = \tau$$

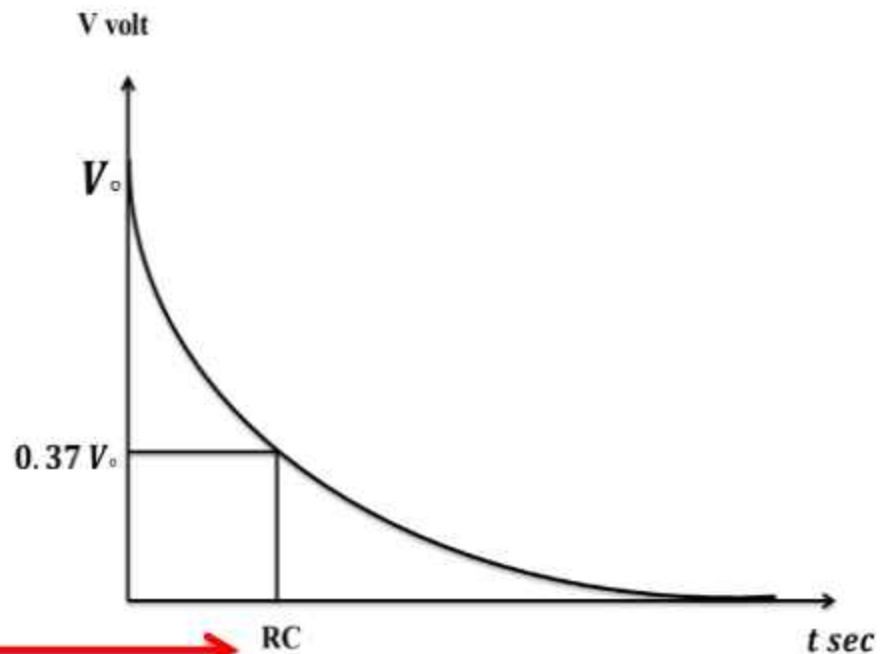

$$\text{Error ratio } (\tau) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

## Experiment No. (4)

$$T_{1/2} = 0.693 RC$$


Theory value

Graph & Calculation /  
Practically

Practically value

$$\text{slop} = RC = ??$$

$$T_{1/2} = 0.693 RC$$

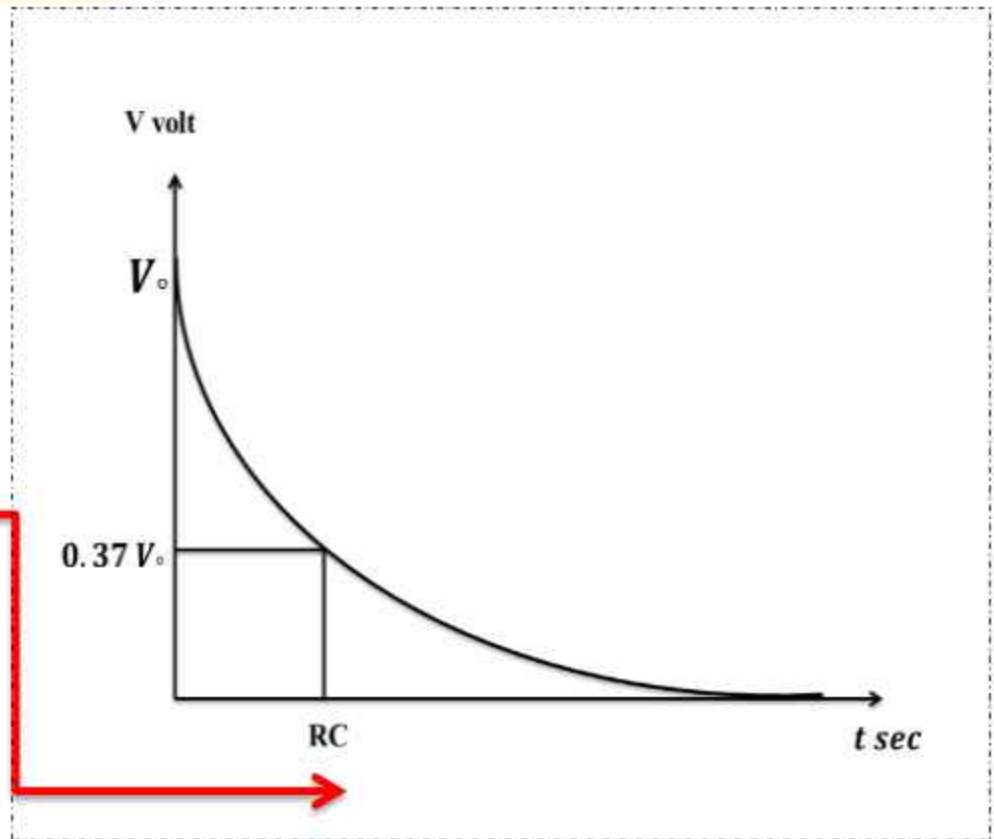

$$\text{Error ratio } (T_{1/2}) = \left| \frac{\text{theory} - \text{practically}}{\text{theory}} \right| \times 100\%$$

## ***Experiment No. ( 5 )***

***Experiments with a deflection magnetometer:  
To investigate how the magnetic flux density due  
to the current in a long straight wire varies with***

***(a) the current in the wire***

***(b) the distance from the wire***





# Experiment No. ( 5 )

Data // part 1

D= 8 cm

Current $I$ /Amp	Magnetometer deflections					$\tan \theta$
	$\theta_1$	$\theta_2$	$\theta_3$	$\theta_4$	Mean $\theta^\circ$	
0.3						
0.6						
0.9						
1.2						
1.5						
1.8						
2.1						
2.4						
2.7						

# Experiment No. ( 5 )

$$B_{E1} \tan \theta = \frac{\mu_0 I}{2\pi D}$$


Graph & Calculation /  
Practically

**slope 1**

$$\text{slope} = \frac{\Delta \tan \theta}{\Delta I}$$

$$\text{slop1} = \frac{1}{\text{slope}}$$
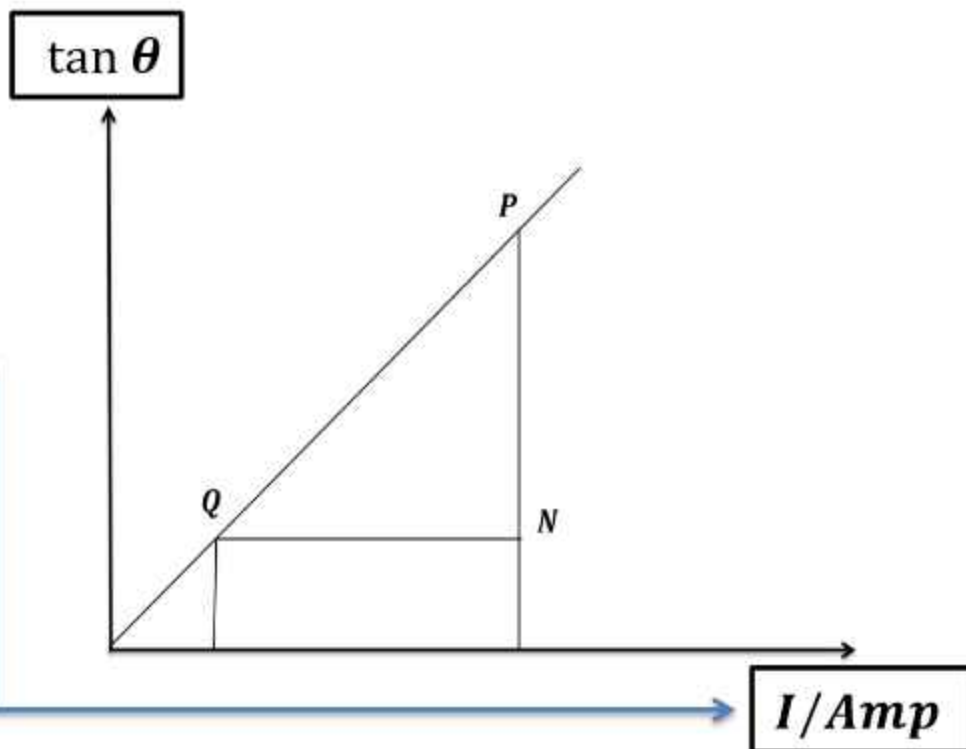
$$\therefore B_{E1} = \frac{\mu_0}{2\pi \times D} \times \text{slop1}$$



# Experiment No. ( 5 )

## Data // part 2

$I = 2.6 \text{ Amp.}$

Distance $D/cm$	Magnetometer deflections					$\cot \theta$
	$\theta_1$	$\theta_2$	$\theta_3$	$\theta_4$	Mean $\theta^\circ$	
8						
10						
12						
14						
16						

## Experiment No. ( 5 )

**slope 2**


$$D = \frac{\mu_0 I}{2\pi B_{E2}} \cot \theta$$

Graph & Calculation /  
Practically

$\cot \theta$

$$\text{slope 2} = \frac{\Delta \cot \theta}{\Delta D}$$
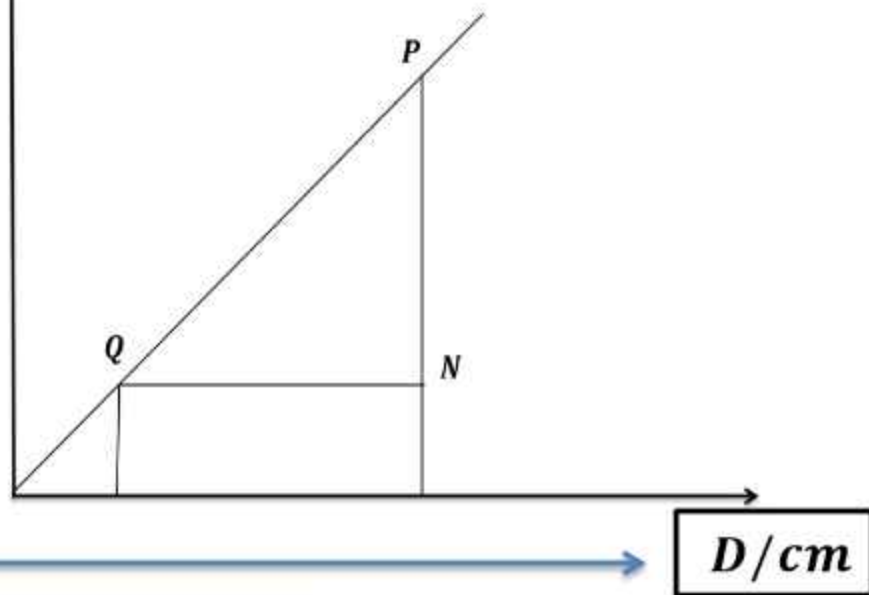
$$\therefore B_{E2} = \frac{\mu_0 \times I}{2\pi} \times \text{slope 2}$$



$$\text{Error ratio } (B_E) = \left| \frac{B_{E2} - B_{E1}}{B_{E2}} \right| \times 100\%$$

**Thanks**