# Chapter Seven (2<sup>nd</sup> Semester) Transistor Biasing

# 7.1: Introduction

A transistor is operated (used) by selecting an appropriate Q - point in the active region of its output characteristics. This is achieved by establishing suitable dc voltages and currents at different terminals of the transistor by using external batteries and circuits. The choice of an appropriate Q - point depends on:

- > The amplitude of the *ac* input signal
- Supply voltages
- > Load resistance
- > Permissible distortion in the output

<u>In</u> spite of the given values of these parameters, the **operating point** <u>may not be</u> **stable** and may shift as a result of a **change in temperature** or **transistor characteristics**.

This is mainly because of the **temperature** dependence of the transistor parameters like  $I_{CO}$ ,  $\beta$ , and  $V_{BE}$ . The **parameter**  $\beta$  changes considerably with temperature it doubles for every 10 °C rises in temperature for Ge transistors while for silicon transistors, the change is much less. Therefore, the differential coefficient  $\frac{\partial I_C}{\partial I_{CO}}$  can be used as a measure of the temperature stability of a transistor provided the change in  $\beta$  and  $V_{BE}$  is insignificant. Thus, the stability S of a transistor can be approximately expressed as:

$$\boldsymbol{S} = \frac{\partial I_C}{\partial I_{CO}} \quad \dots \quad (1)$$

The lower the value of S more stable the Q - point. The lowest value of S is unity since  $I_C$  must contain  $I_{CO}$ . In actual transistor circuits, S is greater than unity.

The increase in  $I_{CO}$  with temperature may eventually cause the burning out of the transistor, a condition known as *thermal runaway*.

<u>As</u>  $I_{co}$  increases <u>due to</u> a rise in temperature, there is a corresponding increase in  $I_c$ .

An excessive amount of **heat** is, therefore, evolved at the collector junction, the **temperature** of which **rises** further.

This, in turn, **increases**  $I_{CO}$  and the cycle repeats itself. As the process is cumulative, the temperature of the collector junction may increase so much that it exceeds the rated value of the transistor, thereby **burning out the transistor**.

We describe below some biasing circuits for the common-emitter *npn* transistor as it is preferred in most applications.

#### 2022-2023

### 7.2: Base Bias (Fixed Bias)

In this type of bias, the same power supply is used to forward-bias the emitter-base junction and reverse-bias the collector-base junction as shown in figure (1b).



Figure (1): (a): Base bias. (b): Common emitter *npn* transistor with fixed bias.

This method of biasing is common in switching circuits. Figure (1a) shows a base-biased transistor. The analysis of this circuit for the linear region shows that it is directly dependent on  $\beta_{DC}$ .

Starting with **Kirchhoff's voltage law** around the base circuit:  $V_{CC} - V_{R_B} - V_{BE} = 0$ Substituting  $V_{R_B} = I_B R_B$ , you get:  $V_{CC} - I_B R_B - V_{BE} = 0 \rightarrow I_B R_B = V_{CC} - V_{BE}$ 

The resistances  $R_B$  and  $R_c$  (or  $R_L$ ) are <u>used to establish</u> the quiescent (no signal) base  $I_B$  and collector  $I_C$  currents respectively.

The quiescent **base current**  $I_B$  is:

$$\boldsymbol{I}_{\boldsymbol{B}} = \frac{V_{CC} - V_{BE}}{R_B} \dots (2)$$

The voltage  $V_{BE}$  is about 0.7 V for silicon transistors and may be neglected in comparison with  $V_{CC}$  therefore, we have:  $I_B \cong \frac{V_{CC}}{R_B}$ 

**Kirchhoff's voltage law** applied around the collector circuit in Figure (1a) gives the following equation:  $V_{CC} - I_C R_C - V_{CE} = 0$ Solving for  $V_{CE}$ :  $V_{CE} = V_{CC} - I_C R_C$  ... (3) Substituting the expression for  $I_B$  into the formula  $I_C = \beta_{DC} I_B$  yields:

$$I_{C} = \beta_{DC} \left( \frac{V_{CC} - V_{BE}}{R_{B}} \right) \dots (4)$$

Thus, the base current is independent of the quiescent collector current and is constant for the given values of  $V_{CC}$  and  $R_B$ , hence this circuit is called the fixed bias circuit. If the Q - point is chosen in the region of the output characteristics, then  $\alpha$  is a constant independent of the collector voltage. The current  $I_C (I_C = \beta I_B + \gamma I_{CO})$  as given by equation (5) is:

 $I_{C} = \frac{\alpha}{1-\alpha}I_{B} + \frac{1}{1-\alpha}I_{CO} \dots (5)$ where  $\beta = \frac{\Delta I_{C}}{\Delta I_{B}} = \frac{\alpha}{1-\alpha}$  (have in Page 155) and  $\gamma = \frac{\Delta I_{E}}{\Delta I_{B}} = \frac{1}{1-\alpha}$  (have in Page 157)

Therefore, the stability factor **S** is:  $S = \frac{\partial I_C}{\partial I_{CO}} = \frac{1}{1-\alpha}$  ... (6)

Taking  $\alpha = 0.98$ , we obtain S = 50. This indicates that Ic increases fifty times as fast as  $I_{CO}$ , i.e., the circuit cannot provide a stable operating point and there exists a good probability of thermal runaway occurs. Another disadvantage of this circuit is that if the transistor is replaced by another similar transistor, the quiescent current and voltage may change markedly resulting in a shift of the Q - point.

In the circuit of figure (1b) the capacitors C1 and C2 are the coupling capacitors which are used to connect the transistor with some input and output devices. They allow the passage of *ac* signal but block the dc currents and voltages which might be present along with the ac signal.  $\frac{V_{CC}}{+12V}$ 

**Example 1:** Determine how much the Q - point ( $I_C$ ,  $V_{CE}$ ) for the circuit in this figure will change over a temperature range where  $\beta_{DC}$  increases from 100 to 200.

#### **Solution:**

For 
$$\beta_{DC} = 100$$
, and  $V_{BE} = 0.7 V$ .  
 $I_{C} = \beta_{DC} \left( \frac{V_{CC} - V_{BE}}{R_{B}} \right) \rightarrow I_{C(1)} = 100 \left( \frac{12 - 0.7}{330 \times 10^{3}} \right) = 3.42 \ mA$   
 $V_{CE} = V_{CC} - I_{C}R_{C} \rightarrow V_{CE(1)} = 12 - (3.42 \times 10^{-3} \times 560) = 10.1 \ V$   
For  $\beta_{DC} = 200$ , and  $V_{BE} = 0.7 \ V$ .  
 $I_{C} = \beta_{DC} \left( \frac{V_{CC} - V_{BE}}{R_{B}} \right) \rightarrow I_{C(2)} = 200 \left( \frac{12 - 0.7}{330 \times 10^{3}} \right) = 6.84 \ mA$   
 $V_{CE} = V_{CC} - I_{C}R_{C} \rightarrow V_{CE(2)} = 12 - (6.84 \times 10^{-3} \times 560) = 8.17 \ V$ 

 $\begin{cases} R_{\rm C} \\ 560 \Omega \end{cases}$ 

RB

330 kO

$$\% \Delta I_{C} = \left(\frac{I_{C(2)} - I_{C(1)}}{I_{C(1)}}\right) \times 100\% = \left(\frac{6.84 - 3.42}{3.42}\right) \times 100\% = 100\% \text{ (an increase)}$$

The percent change in  $V_{CE}$  is:

$$\% \Delta V_{CE} = \left(\frac{V_{CE(2)} - V_{CE(1)}}{V_{CE(1)}}\right) \times 100\% = \left(\frac{8.17 - 10.1}{10.1}\right) \times 100\% = -19.1\% (a \ decrease)$$

As you can see, the Q - point is very dependent on  $\beta_{DC}$  in this circuit and therefor makes the base bias arrangement very unreliable. Consequently, base bias is not normally used if linear operation is required. However, it can be used in switching applications

**H.W: Q1:** Determine how much the  $Q - point (I_C, V_{CE})$  for the circuit in this figure will change over a temperature range where  $\beta_{DC}$  increases from 85 to 100 and  $V_{BE}$  decreases from 0.7 V to 0.6 V. **Solution:** 



**H.W:** Q2: If  $\beta_{DC} = 50$  at 0°C and 125 at 100°C for the circuit in figure above, determine the percent change in the Q - point values over the temperature range. Assume no change in  $V_{BE}$ .

Page 187

### 7.3: Collector-Feedback Bias

Collector feedback bias is created by connecting a single resistance  $R_B$  between the collector and the base as shown in figure (2b). the forward base bias is provided by collector voltage  $V_{CE}$  rather than the collector supply voltage  $V_{CC}$ . It is, therefore, also known as collector-tobase bias. This circuit has better stability than the previous one.



Figure (2): (a): Collector-feedback bias. (b): Common emitter *npn* transistor with collector-feedback bias.

If  $I_C$  increases because of a change in temperature or replacement of the transistor by another one of the same types, the drop across  $R_C$  increases. Since  $V_{CC}$  is fixed, there is a corresponding decrease in  $V_{CE}$ .

This causes  $I_B$  to decrease which, in turn, decreases  $I_C$ . Thus, the initial increases in  $I_C$  are automatically compensated for in this circuit. From figure (3), it follows that:

$$V_{CC} = (I_C + I_B)R_C + V_{CE}$$

By **Ohm's law**, the base current can be expressed as:  $I_B = \frac{V_{CE} - V_{BE}}{R_B} \rightarrow V_{CE} = I_B R_B + V_{BE}$ 

$$V_{CC} = I_C R_C + I_B R_C + I_B R_B + V_{BE}$$
  
Neglecting  $I_B R_C$  and  $I_C = \beta_{DC} I_B \rightarrow I_B = \frac{I_C}{\beta_{DC}}$  we get:  $I_C R_C + \frac{I_C}{\beta_{DC}} R_B = V_{CC} - V_{BE} \rightarrow I_C = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta_{DC}}} \dots (7)$ 

Neglecting  $V_{BE}$  we get:

$$V_{CC} = I_C R_C + I_B (R_C + R_B)$$
$$I_B = \frac{V_{CC} - I_C R_C}{R_C + R_B} \dots (8)$$

In indicates the decrease in  $I_B$  with an increase in  $I_C$  as explained above. From equation (5), we have:

$$I_{C} = \frac{\alpha}{1-\alpha}I_{B} + \frac{1}{1-\alpha}I_{CO}$$

Using equation (8) we obtain:

$$I_{C} = \frac{\alpha}{1-\alpha} \left( \frac{V_{CC} - I_{C}R_{C}}{R_{C} + R_{B}} \right) + \frac{1}{1-\alpha} I_{CO}$$

Or

$$I_{C}(1-\alpha) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} - \frac{\alpha I_{C}R_{C}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO} \rightarrow I_{C}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}} + I_{CO}\left(1-\alpha + \frac{\alpha R_{C}}{R_{C}+R_{B}}\right) = \frac{\alpha V_{CC}}{R_{C}+R_{B}}$$

Therefore, the stability factor **S** is:

$$\boldsymbol{S} = \frac{\partial I_C}{\partial I_{CO}} = \frac{1}{1 - \boldsymbol{\alpha} + \frac{\boldsymbol{\alpha} R_C}{R_C + R_B}} \rightarrow \boldsymbol{S} = \frac{1}{1 - \frac{\boldsymbol{\alpha} R_C + \boldsymbol{\alpha} R_B}{R_C + R_B} + \frac{\boldsymbol{\alpha} R_C}{R_C + R_B}} \rightarrow \boldsymbol{S} = \frac{1}{1 - \frac{\boldsymbol{\alpha} R_B}{R_C + R_B}} \dots (9)$$

Using equation  $(\beta = \frac{\alpha}{1-\alpha} \rightarrow \alpha = \frac{\beta}{1+\beta})$ , it becomes:

$$\boldsymbol{S} = \frac{1}{1 - \boldsymbol{\alpha} + \frac{\boldsymbol{\alpha}R_{C}}{R_{C} + R_{B}}} = \frac{1}{\frac{\boldsymbol{\alpha}}{\boldsymbol{\beta}} + \frac{\boldsymbol{\alpha}R_{C}}{R_{C} + R_{B}}} = \frac{1 \times \frac{\boldsymbol{\beta}}{\boldsymbol{\alpha}}}{\left(\frac{\boldsymbol{\alpha}}{\boldsymbol{\beta}} + \frac{\boldsymbol{\alpha}R_{C}}{R_{C} + R_{B}}\right) \times \frac{\boldsymbol{\beta}}{\boldsymbol{\alpha}}} = \frac{1 + \boldsymbol{\beta}}{\left(1 + \frac{\boldsymbol{\beta}R_{C}}{R_{C} + R_{B}}\right)} \dots (10)$$

Comparing equation (9) with (6), we find that the stability is better in this case than in the previous case. However, for the improvement is only marginal.

**Example 2:** Calculate the Q – *point* value ( $I_C$  and  $V_{CE}$ ) for the circuit in this figure. Solution:

$$I_{\rm C} = \frac{V_{\rm CC} - V_{\rm BE}}{R_{\rm C} + R_{\rm B}/\beta_{\rm DC}} = \frac{10 \,{\rm V} - 0.7 \,{\rm V}}{10 \,{\rm k}\Omega + 180 \,{\rm k}\Omega/100} = 788 \,\mu{\rm A}$$

$$V_{\rm CE} = V_{\rm CC} - I_{\rm C}R_{\rm C} = 10 \,{\rm V} - (788 \,\mu{\rm A})(10 \,{\rm k}\Omega) = 2.12 \,{\rm V}$$

**H.W: Q3:** Calculate the Q - point values in figure above for  $\beta_{DC} = 200$  and determine the percent change in the Q - point in this figure from  $\beta_{DC} = 100$  to  $\beta_{DC} = 200$ .

**H.W: Q4:** Determine the percent change in the Q - point in this figure from  $\beta_{DC} = 100$  to  $\beta_{DC} = 85$ .



## 7.4: Emitter–Feedback Bias

To calculate  $I_E$ , you can write Kirchhoff's voltage law (KVL) around the base circuit.

$$-V_{CC} + I_B R_B + V_{BE} + I_E R_E = 0 \rightarrow I_E R_E + I_B R_B = V_{CC} - V_{BE}$$
  
Substituting  $I_E / \beta_{DC}$  for  $I_B$ , you can see that  $I_E$  is still dependent on  $\beta_{DC}$ :

$$I_{E}R_{E} + \frac{I_{E}}{\beta_{DC}}R_{B} = V_{CC} - V_{BE} \rightarrow I_{E} = \frac{V_{CC} - V_{BE}}{R_{E} + \frac{R_{B}}{\beta_{DC}}} \dots (11)$$

Kirchhoff's voltage law applied around the collector circuit in Figure (3a) gives the following equation:  $V_{CC} - I_C R_C - I_C R_E - V_{CE} = 0$ Solving for  $V_{CE}$ :  $V_{CE} = V_{CC} - I_C (R_C + R_E)$  ... (12)

As described above, the collector feedback circuit results in poor stabilization if the collector or load resistance  $R_c$  is small compared with the base resistance  $R_B$ .

The emitter feedback bias shown in figure (3) proves promising in such a case and leads to good stabilization even for  $R_c$  equal to zero.



Figure (3): (a): Emitter-feedback bias. (b): Common emitter *npn* transistor with emitter-feedback bias.

The circuit consists of a network of four resistance  $R_1$ ,  $R_2$ ,  $R_E$  and  $R_C$ .

The *dc* voltage drops across  $R_E$  reverse biases the emitter base junction. However, a suitable parallel combination of resistance  $R_1$  and  $R_2$  produces a voltage drop  $V_B$  across  $R_2$  which is greater than the drop across  $R_E$  and has opposite polarity this makes the emitter base junction forward biased. The resistance  $R_C$  reverse biases the collector base junction.

Page 191

2022-2023

R<sub>C</sub> 560 Ω

330 kO

As  $I_C$  tends to increase owing to increase in  $I_{CO}$  which is caused by rise in temperature the current  $I_E$  increases. This increases the voltage drop across  $R_E$  which makes the base terminal less positive with respect to the emitter terminal. Hence the base current decreases which, in turn, decreases the collector current thus, we find that the emitter resistor  $R_E$  provides negative current feedback to the base that tends to maintain  $I_E$  at a constant value. Hence this bias is called the emitter feedback bias.

**Example 3:** Determine how much the  $Q - point (I_C, V_{CE})$  for the circuit in this figure will change over a temperature range where  $\beta_{DC}$  increases from 100 to 200.

#### **Solution:**

For  $\beta_{\rm DC} = 100$ ,

 $I_{\rm C(1)} = I_{\rm E} = \frac{V_{\rm CC} - V_{\rm BE}}{R_{\rm E} + R_{\rm B}/\beta_{\rm DC}} = \frac{12\,{\rm V} - 0.7\,{\rm V}}{1\,{\rm k}\Omega + 330\,{\rm k}\Omega/100} = 2.63\,{\rm mA}$  $V_{\rm CE(1)} = V_{\rm CC} - I_{\rm C(1)}(R_{\rm C} + R_{\rm E}) = 12\,{\rm V} - (2.63\,{\rm mA})(560\,\Omega + 1\,{\rm k}\Omega) = 7.90\,{\rm V}$ For  $\beta_{\rm DC} = 200$ ,

$$I_{C(2)} = I_{E} = \frac{V_{CC} - V_{BE}}{R_{E} + R_{B}/\beta_{DC}} = \frac{12 \text{ V} - 0.7 \text{ V}}{1 \text{ k}\Omega + 330 \text{ k}\Omega/200} = 4.26 \text{ mA}$$
$$V_{CE(2)} = V_{CC} - I_{C(2)}(R_{C} + R_{E}) = 12 \text{ V} - (4.26 \text{ mA})(560 \Omega + 1 \text{ k}\Omega) = 5.35 \text{ V}$$

The percent change in  $I_{\rm C}$  is

$$\%\Delta I_{\rm C} = \left(\frac{I_{\rm C(2)} - I_{\rm C(1)}}{I_{\rm C(1)}}\right) 100\% = \left(\frac{4.26 \text{ mA} - 2.63 \text{ mA}}{2.63 \text{ mA}}\right) 100\% = 62.0\%$$
  
$$\%\Delta V_{\rm CE} = \left(\frac{V_{\rm CE(2)} - V_{\rm CE(1)}}{V_{\rm CE(1)}}\right) 100\% = \left(\frac{7.90 \text{ V} - 5.35 \text{ V}}{7.90 \text{ V}}\right) 100\% = -32.3\%$$

## 7.5: Voltage-Divider Bias

You will now study a method of biasing a transistor for linear operation using a single source resistive voltage divider. This is the most widely used biasing method.

Generally, voltage-divider bias circuits are designed so that the base current  $(I_B)$  is much smaller than the current  $(I_2)$  through  $R_2$  in Figure (4).

In this case, the **voltage-divider circuit** *is very straightforward* to analyse because the loading effect of the base current ( $I_{B(BASE)}$ ) can be ignored.

A voltage divider in which the base current  $(I_B)$  is small compared to the current  $(I_2)$  in  $R_2$  is said to be a stiff voltage divider because the base voltage is relatively independent of different transistors and temperature effects.



Figure (4): Voltage-divider bias.

To analyse a voltage-divider circuit in which  $I_B$  is small compared to  $I_2$ , first calculate the voltage on the base using the unloaded voltage-divider rule:

$$\boldsymbol{V}_{\boldsymbol{B}} = \frac{R_2}{R_1 + R_2} V_{CC} \quad \dots (13)$$

Once you know the base voltage, you can find the voltages and currents in the circuit, as follows:  $V_E = V_B - V_{BE}$  ... (14) and  $I_C \cong I_E = \frac{V_E}{R_E}$  ... (15) Then:  $V_C = V_{CC} - I_C R_C$  ... (16) Once you know  $V_C$  and  $V_E$ , you can determine VCE.  $V_{CE} = V_C - V_E$  ... (17)

# Voltage Divider with Load:



Stiff:  $R_{IN(BASE)} \ge 10R_2$   $V_B \equiv \left(\frac{R_2}{R_1 + R_2}\right) V_{CC}$ Not stiff:  $R_{IN(BASE)} < 10R_2$  $V_B = \left(\frac{R_2 || R_{IN(BASE)}}{R_1 + R_2 || R_{IN(BASE)}}\right) V_{CC}$ 

# Loading Effects of Voltage-Divider Bias:

$$\mathbf{R}_{IN (BASE)} = \frac{\beta_{DC} V_B}{I_E} \dots (18)$$

**Example 4:** Determine  $V_{CE}$  and  $I_C$  in the stiff voltage-divider biased transistor circuit of this figure if  $\beta_{DC} = 100$ .

#### **Solution:**

The base voltage is:

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{5.6 \times 10^3}{10 \times 10^3 + 5.6 \times 10^3} 10 = 3.59 V$$
  
So,  $V_E = V_B - V_{BE} = 3.59 - 0.7 = 2.89 V$   
and  $I_C \cong I_E = \frac{V_E}{R_E} = \frac{2.89}{560} = 5.16 mA$   
and  $V_C = V_{CC} - I_C R_C = 10 - (5.16 \times 10^{-3} \times 1 \times 10^3) = 4.84 V$   
Therefore;  $V_{CE} = V_C - V_E = 4.84 - 2.89 = 1.95 V$ 



**H.W: Q5:** If the voltage divider in figure above was not stiff, how would  $V_B$  be affected?

2022-2023

**Example 5:** Determine the *dc* input resistance looking in at the base of the transistor in this figure.  $\beta_{DC} = 125$  and  $V_B = 4$  V.

#### **Solution:**

$$I_E = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E} = \frac{4 - 0.7}{1 \times 10^3} = 3.3 \ mA$$
$$R_{IN \ (BASE)} = \frac{\beta_{DC} V_B}{I_E} = \frac{125 \times 4}{3.3 \times 10^{-3}} = 152 \ K\Omega$$

**H.W: Q6:** What is  $R_{IN (BASE)}$  in figure above if  $\beta_{DC} = 60$  and  $V_B = 2$  V? **Solution:** 

### 7.6: Thevenin's Theorem Applied to Voltage-Divider Bias

The equivalent circuit of figurer (3) obtained by applying the Thevenin's theorem to the left of the terminals BG is shown in figurer (5) the input and output voltage and the capacitor  $C_E$  are not shown.



Figure (5): Equivalent circuit of figure (3).



The **Thevenin of equivalent base voltage**  $V_B$  is given by:

$$V_{TH} = V_B = \frac{R_2}{R_1 + R_2} V_{CC} \dots (19)$$

The **Thevenin or equivalent base resistance** *R*<sub>*B*</sub> is given by:

$$\mathbf{R}_{TH} = \mathbf{R}_{B} = \frac{R_{1}R_{2}}{R_{1} + R_{2}} \dots (20)$$

Appling the Kirchhoff's voltage law to input circuit of figure (5), we get:

$$V_{TH} - V_{R_{TH}} - V_{BE} + V_{R_E} = 0$$

Substituting, using Ohm's law, and solving for  $V_{TH}$ ,

$$\boldsymbol{V}_{\boldsymbol{B}} = I_B R_B + V_{BE} - I_E R_E$$

The voltage  $V_{BE}$  can be neglected in comparison to  $V_B$  since in an *npn* transistor amplifier. Substituting  $-(I_B + I_C)$  for  $I_E$  i.e.;  $(I_E = -(I_B + I_C))$ 

 $V_B = I_B R_B + (I_B + I_C) R_E = I_B R_B + I_B R_E + I_C R_E = I_B (R_B + R_E) + I_C R_E$ Then solving for  $I_B$ :

$$I_{B} = \frac{V_{B} - I_{C}R_{E}}{R_{B} + R_{E}} \dots (21)$$

Substituting it in equation (5)  $(I_{C} = \frac{\alpha}{1-\alpha}I_{B} + \frac{1}{1-\alpha}I_{CO})$ , we obtain:

$$(1 - \alpha)I_{C} = \alpha \frac{V_{B} - I_{C}R_{E}}{R_{B} + R_{E}} + I_{CO} \rightarrow (1 - \alpha)I_{C} = \frac{\alpha V_{B}}{R_{B} + R_{E}} - \frac{\alpha R_{E}I_{C}}{R_{B} + R_{E}} + I_{CO}$$
$$\left(1 - \alpha + \frac{\alpha R_{E}}{R_{B} + R_{E}}\right)I_{C} = \frac{\alpha V_{B}}{R_{B} + R_{E}} + I_{CO} \rightarrow I_{C} = \frac{\frac{\alpha V_{B}}{R_{B} + R_{E}}}{1 - \alpha + \frac{\alpha R_{E}}{R_{B} + R_{E}}} + \frac{I_{CO}}{1 - \alpha + \frac{\alpha R_{E}}{R_{B} + R_{E}}}$$

The stability factor **S** is calculated as:

$$\boldsymbol{S} = \frac{\partial I_C}{\partial I_{CO}} = \frac{1}{1 - \boldsymbol{\alpha} + \frac{\boldsymbol{\alpha} R_E}{R_B + R_E}} \rightarrow \boldsymbol{S} = \frac{1}{1 - \frac{\boldsymbol{\alpha} R_E + \boldsymbol{\alpha} R_B}{R_B + R_E} + \frac{\boldsymbol{\alpha} R_E}{R_B + R_E}} \rightarrow \boldsymbol{S} = \frac{1}{1 - \frac{\boldsymbol{\alpha} R_B}{R_B + R_E}} \dots (22)$$

Using equation  $(\beta = \frac{\alpha}{1-\alpha} \rightarrow \alpha = \frac{\beta}{1+\beta})$ , it becomes:

$$S = \frac{1}{1 - \alpha + \frac{\alpha R_E}{R_B + R_E}} = \frac{1}{\frac{\alpha}{\beta} + \frac{\alpha R_E}{R_B + R_E}} = \frac{1 \times \frac{\beta}{\alpha}}{\left(\frac{\alpha}{\beta} + \frac{\alpha R_E}{R_B + R_E}\right) \times \frac{\beta}{\alpha}} = \frac{1 + \beta}{\left(1 + \frac{\beta R_E}{R_B + R_E}\right)} \dots (23)$$
  
Equation (23) indicates that as  $\frac{R_B}{R_E} \to 0, S \to 1$  and  $\frac{R_B}{R_E} \to \infty, S \to 1 + \beta$ .

n

 $R_E$   $R_E$   $R_E$   $R_E$ 

Hence smaller the  $R_B$  or larger the  $R_E$ , better is the stabilization. For finite values of  $R_B$ , is always exceeds 1 which means  $I_C$  always increases faster than  $I_{CO}$ . keeping the Q – point fixed, the stability can be improved by either decreasing  $R_B$  or increasing  $R_E$ . If  $R_B$  is reduced the  $R_1R_2$  network draws more current from the supply which causes greater power loss. The increase in  $R_E$  (with fixed  $R_B$ ), on the other hand, requires higher  $V_{CC}$  to maintain the same quiescent currents which again increases the power loss or decreases in efficiency of the device.

When this circuit is used for amplification of ac signals, the ac voltage drops across  $R_E$  produces unwanted negative feedback which reduces the gain of the amplifier. This is avoided by connecting a large bypass capacitor  $C_E$  across  $R_E$  which has very small reactance at the lowest frequency of the input signal.

### 7.6.1: Voltage-Divider Biased NPN Transistor



Figure (6): Thevenizing the bias circuit.

The Thevenin equivalent of the bias circuit, connected to the transistor base, is shown in the beige box in Figure (6c). Applying Kirchhoff's voltage law around the equivalent base-emitter loop gives:

$$V_{TH}-V_{R_{TH}}-V_{BE}-V_{R_E}=0$$

Substituting, using Ohm's law, and solving for  $V_{TH}$ ,

$$\boldsymbol{V}_{\boldsymbol{B}} = I_B R_B + V_{BE} + I_E R_E$$

Substituting  $I_E / \beta_{DC}$  for  $I_B$ :

$$\boldsymbol{V}_{\boldsymbol{B}} = \frac{I_E}{\beta_{DC}} R_B + V_{BE} + I_E R_E$$

$$I_E = \frac{V_B - V_{BE}}{R_E + \frac{R_B}{\beta_{DC}}} \dots (24)$$

If  $\frac{R_B}{\beta_{DC}}$  is small compared to  $R_E$ , the result is the same as for an unloaded voltage divider. Voltage-divider bias is widely used because reasonably good bias stability is achieved with a single supply voltage.

### 7.6.2: Voltage-Divider Biased PNP Transistor



Figure (7): Voltage-divider biased pnp transistor.

The analysis procedure is the same as for an *npn* transistor circuit using Thevenin's theorem and Kirchhoff's voltage law, as demonstrated in the following steps with reference to Figure (7). For Figure (7a), applying Kirchhoff's voltage law around the base-emitter circuit gives

$$V_{TH} + V_{R_{TH}} - V_{BE} + V_{R_E} = 0$$

Substituting, using Ohm's law, and solving for  $V_{TH}$ ,

$$\boldsymbol{V}_{\boldsymbol{B}} = V_{BE} - I_B R_B - I_E R_E$$

The base current is:  $I_B = I_E / \beta_{DC}$ 

$$\boldsymbol{V}_{\boldsymbol{B}} = V_{BE} - \frac{I_E}{\beta_{DC}} R_B - I_E R_E \rightarrow \frac{I_E}{\beta_{DC}} R_B + I_E R_E = -V_B + V_{BE}$$

The equation for  $I_E$  is:

$$I_{E} = \frac{-V_{B} + V_{BE}}{R_{E} + \frac{R_{B}}{\beta_{DC}}} \dots (25)$$

By Thevenin's theorem:  $V_{TH} = V_B = \frac{R_2}{R_1 + R_2} V_{CC}$  and  $R_{TH} = R_B = \frac{R_1 R_2}{R_1 + R_2}$ 

For Figure (7b), the analysis is as follows:

$$-V_{TH} + V_{R_{TH}} - V_{BE} + V_{R_E} + V_{EE} = 0$$

Substituting, using Ohm's law, and solving for  $V_{TH}$ ,

$$\boldsymbol{V}_{\boldsymbol{B}} = \boldsymbol{I}_{B}\boldsymbol{R}_{B} + \boldsymbol{I}_{E}\boldsymbol{R}_{E} - \boldsymbol{V}_{BE} + \boldsymbol{V}_{EE}$$

The base current is:  $I_B = I_E / \beta_{DC}$ 

$$\boldsymbol{V}_{\boldsymbol{B}} = \frac{I_E}{\beta_{DC}} R_B + I_E R_E - V_{BE} + V_{EE} \rightarrow \frac{I_E}{\beta_{DC}} R_B + I_E R_E = V_B + V_{BE} - V_{EE}$$

The equation for  $I_E$  is:

$$I_{E} = \frac{V_{B} + V_{BE} - V_{EE}}{R_{E} + \frac{R_{B}}{\beta_{DC}}} \dots (26)$$

By Thevenin's theorem:  $V_{TH} = V_B = \frac{R_1}{R_1 + R_2} V_{EE}$  and  $R_{TH} = R_B = \frac{R_1 R_2}{R_1 + R_2}$ 

**Example 6:** Find  $I_c$  and  $V_{Ec}$  for the *pnp* transistor circuit in this figure.

### **Solution:**

Apply Thevenin's theorem.  

$$V_{\text{TH}} = \left(\frac{R_1}{R_1 + R_2}\right) V_{\text{EE}} = \left(\frac{22 \,\text{k}\Omega}{22 \,\text{k}\Omega + 10 \,\text{k}\Omega}\right) 10 \,\text{V} = (0.688) 10 \,\text{V} = 6.88 \,\text{V}$$

$$R_{\text{TH}} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(22 \,\text{k}\Omega)(10 \,\text{k}\Omega)}{22 \,\text{k}\Omega + 10 \,\text{k}\Omega} = 6.88 \,\text{k}\Omega$$

$$I_{\text{E}} = \frac{V_{\text{TH}} + V_{\text{BE}} - V_{\text{EE}}}{R_{\text{E}} + R_{\text{TH}}/\beta_{\text{DC}}} = \frac{6.88 \,\text{V} + 0.7 \,\text{V} - 10 \,\text{V}}{1.0 \,\text{k}\Omega + 45.9 \,\Omega} = \frac{-2.42 \,\text{V}}{1.0459 \,\text{k}\Omega} = -2.31 \,\text{mA}$$

$$I_{\text{C}} = I_{\text{E}} = 2.31 \,\text{mA}$$

$$V_{\text{C}} = I_{\text{C}} R_{\text{C}} = (2.31 \,\text{mA})(2.2 \,\text{k}\Omega) = 5.08 \,\text{V}$$

$$V_{\text{E}} = V_{\text{EE}} - I_{\text{E}} R_{\text{E}} = 10 \,\text{V} - (2.31 \,\text{mA})(1.0 \,\text{k}\Omega) = 7.68 \,\text{V}$$

$$V_{\text{EC}} = V_{\text{E}} - V_{\text{C}} = 7.68 \,\text{V} - 5.08 \,\text{V} = 2.6 \,\text{V}$$

$$R_{2}$$

$$R_{E}$$

$$R_{E}$$

$$R_{C}$$

$$R_{1}$$

$$R_{C}$$

$$R_{C$$

V

**Example 7:** Find  $I_c$  and  $V_{CE}$  for a *pnp* transistor circuit with these values:  $R_1 = 68K\Omega$ ,  $R_2 = 47K\Omega$ ,  $R_c = 1.8K\Omega$ ,  $R_E = 2.2K\Omega$ ,  $V_{CC} = -6V$ , and  $\beta_{DC} = 75$ . Refer to this figure, which shows the schematic with a negative supply voltage.

#### **Solution:**

Apply Thevenin's theorem.

$$V_{TH} = V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{47 \times 10^3}{68 \times 10^3 + 47 \times 10^3} (-6) = -2.45 V$$

$$R_{TH} = R_B = \frac{R_1 R_2}{R_1 + R_2} = \frac{68 \times 10^3 \times 47 \times 10^3}{68 \times 10^3 + 47 \times 10^3} = 27.8 K\Omega$$

$$I_C \approx I_E = \frac{-V_B + V_{BE}}{R_E + \frac{R_B}{\beta_{DC}}} = -\frac{-(-2.45) + 0.7}{2.2 \times 10^3 + \frac{27.8 \times 10^3}{75}} = \frac{3.15}{2571} = 1.23 mA$$

$$I_C \approx -I_E = -1.23 mA$$
So,  $V_E = -I_E R_E = -1.23 \times 10^{-3} \times 2.2 \times 10^3 = -2.71 V$ 
and  $V_C = V_{CC} - I_C R_C = -6 - (-1.23 \times 10^{-3} \times 1.8 \times 10^3) = -3.79 V$ 
Therefore;  $V_{CE} = V_C - V_E = -3.79 - (-2.71) = -1.08 V$ 



# **SUMMARY:**

- Loading effects are neglected for a stiff voltage divider.
- The dc input resistance at the base of a BJT is approximately  $\beta_{DC}R_E$ .
- Voltage-divider bias provides good Q point stability with a single-polarity supply voltage. It is the most common bias circuit.
- Emitter bias generally provides good Q point stability but requires both positive and negative supply voltages.
- The base bias circuit arrangement has poor stability because its Q point varies widely with  $\beta_{DC}$ .
- Emitter-feedback bias combines base bias with the addition of an emitter resistor.
- Collector-feedback bias provides good stability using negative feedback from collector to base.

# **KEY TERMS:**

**Feedback**: The process of returning a portion of a circuit's output back to the input in such a way as to oppose or aid a change in the output.

**Q-point**: The dc operating (bias) point of an amplifier specified by voltage and current values.

Stiff Voltage Divider: A voltage divider for which loading effects can be neglected.

#### **SELF-TEST:** <u>https://quizlet.com/520347124/chapter-5-transistor-bias-circuits-flash-cards/</u>

1. The input resistance at the base of a biased transistor depends mainly on

(a)  $\beta_{DC}$  (b)  $R_B$  (c)  $R_E$  (d)  $\beta_{DC}$  and  $R_E$ 2. In a voltage-divider biased transistor circuit such as in Figure (6),  $R_{IN (BASE)}$  can generally be neglected in calculations when

(a)  $R_{IN (BASE)} > R_2$  (b)  $R_2 > 10R_{IN (BASE)}$  (c)  $R_{IN (BASE)} > 10R_2$  (d)  $R_1 \ll R_2$ 

3. In a certain voltage-divider biased *npn* transistor,  $V_B$  is 2.95 V. The *dc* emitter voltage is approximately

(a) 2.25 V (b) 2.95 V (c) 3.65 V (d) 0.7 V

- 4. Voltage-divider bias
  - (a) cannot be independent of  $\beta_{DC}$  (b) can be essentially independent of  $\beta_{DC}$
- (c) is not widely used (d) requires fewer components than all the other methods 5. Emitter bias is
  - (a) essentially independent of  $\beta_{DC}$  (b) very dependent on  $\beta_{DC}$
  - (c) provides a stable bias point (d) answer (a) and (c)

6. In an emitter bias circuit,  $R_E = 2.7 K\Omega$  and  $V_{EE} = 15 V$ . The emitter current

(a) is 5.3 mA (b) is 2.7 mA (c) is 180 mA (d) cannot be determined

7. The disadvantage of base bias is that

- (a) it is very complex (b) it produces low gain
- (c) it is too beta dependent (d) it produces high leakage current
- 8. Collector-feedback bias is
  - (a) based on the principle of positive feedback (b) based on b
  - (c) based on the principle of negative feedback
- (b) based on beta multiplication

(d) not very stable